



SUMMER- 18 EXAMINATION

Subject Name: Electronic Devices & Circuits Model Answer

Subject Code: **17319**

Important Instructions to examiners:



- 1) The answers should be examined by key words and not as word-to-word as given in the model answer scheme.
- 2) The model answer and the answer written by candidate may vary but the examiner may try to assess the understanding level of the candidate.
- 3) The language errors such as grammatical, spelling errors should not be given more importance (Not applicable for subject English and Communication Skills).
- 4) While assessing figures, examiner may give credit for principal components indicated in the figure. The figures drawn by candidate and model answer may vary. The examiner may give credit for any equivalent figure drawn.
- 5) Credits may be given step wise for numerical problems. In some cases, the assumed constant values may vary and there may be some difference in the candidate's answers and model answer.
- 6) In case of some questions credit may be given by judgement on part of examiner of relevant answer based on candidate's understanding.
- 7) For programming language papers, credit may be given to any other program based on equivalent concept.

Q. No.	Sub Q. N.	Answers	Marking Scheme																
1	A	Attempt any SIX:	12- Total Marks																
	a	List different operating regions of transistor.	2M																
	Ans:	<p>Operating regions of transistor:-</p> <table border="1"> <thead> <tr> <th>Operating Region</th> <th>I_B or V_{CE}</th> <th>BC and BE junctions</th> <th>Mode</th> </tr> </thead> <tbody> <tr> <td>Cut off</td> <td>I_B = very small</td> <td>Reverse biased and Reverse biased</td> <td>Open switch</td> </tr> <tr> <td>Saturation</td> <td>V_{CE} = Very small</td> <td>Forward biased and Forward biased</td> <td>Closed switch</td> </tr> <tr> <td>Active</td> <td>V_{CE} = Moderate</td> <td>Reverse biased and Forward biased</td> <td>Amplifier</td> </tr> </tbody> </table>	Operating Region	I _B or V _{CE}	BC and BE junctions	Mode	Cut off	I _B = very small	Reverse biased and Reverse biased	Open switch	Saturation	V _{CE} = Very small	Forward biased and Forward biased	Closed switch	Active	V _{CE} = Moderate	Reverse biased and Forward biased	Amplifier	2M
Operating Region	I _B or V _{CE}	BC and BE junctions	Mode																
Cut off	I _B = very small	Reverse biased and Reverse biased	Open switch																
Saturation	V _{CE} = Very small	Forward biased and Forward biased	Closed switch																
Active	V _{CE} = Moderate	Reverse biased and Forward biased	Amplifier																
	b	Define the term stability factor.	2M																
	Ans:	<p>Stability factor It is defined as the rate of change of collector current I_C with respect to the collector base leakage current I_{CO}, keeping both the current I_B and the current gain β constant.</p> $S = \frac{\partial I_C}{\partial I_{CO}} = \frac{dI_C}{dI_{CO}} = \frac{\Delta I_C}{\Delta I_{CO}}$	2M																

SUMMER- 18 EXAMINATION

Subject Name: Electronic Devices & Circuits Model Answer

Subject Code: 17319

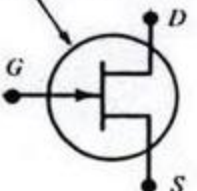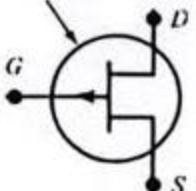c	Draw the symbol of n-channel and p-channel JFET.	2M
Ans:	<p>Symbol of n-channel and p-channel JFET:-</p> <div style="display: flex; justify-content: space-around; align-items: center;"> <div style="text-align: center;"> <p>Schematic Symbol of an n-Channel JFET</p>  </div> <div style="text-align: center;"> <p>Schematic Symbol of a p-Channel JFET</p>  </div> </div>	1M each
d	List the types of amplifier coupling.	2M
Ans:	<p>Types of amplifier coupling: (ANY TWO)</p> <ol style="list-style-type: none"> 1. Resistance – capacitance (RC) coupling. 2. Transformer coupling 3. Direct coupling 	1M each
e	Define intrinsic stand-off ratio of UJT.	2M
Ans:	<p>Intrinsic standoff ratio:</p> <p>It is defined as the ratio of the R_{B1} (base resistance 1) to the inter-base resistance R_{BB}.</p> $\eta = \frac{R_{B1}}{R_{BB}} = \frac{R_{B1}}{R_{B1} + R_{B2}}$	<p>(Definition</p> <p>:1M,</p> <p>Equation</p> <p>:1M)</p>
f	State the need of voltage regulator.	2M
Ans:	<p>NEED OF VOLTAGE REGULATORS:-</p> <p>DC voltage obtained by using rectifier and filter is not constant and may vary depending upon supply variations. This DC voltage may result in an error or may damage other electronic devices or circuits</p> <p>e.g.</p> <ol style="list-style-type: none"> 1. In oscillators it may lead to phase shift. 2. In amplifiers it may lead to change in voltage gain or power gain. 	2M



SUMMER- 18 EXAMINATION

Subject Name: Electronic Devices & Circuits Model Answer


Subject Code: **17319**

	<p>3. It may lead to calibration error in measuring instruments.</p> <p>4. It may produce distortions in output of audio and video amplifiers.</p> <p>Hence to avoid these errors DC voltage regulators are necessary to keep the output DC voltage constant.</p>	
g	Define efficiency of power amplifier.	2M
Ans:	<p>Definition:-</p> <p>Efficiency of power amplifier is defined as the ratio of r. m. s. output power dissipated in the load to the total DC power taken from the supply source.</p> <p>Formula:-</p> $\eta\% = \frac{P_{OUT}}{P_{DC}} \times 100$ <p>Where:</p> <p>$\eta\%$ - is the efficiency of the amplifier.</p> <p>P_{out} - is the amplifiers output power delivered to the load.</p> <p>P_{dc} - is the DC power taken from the supply.</p>	<p>1M</p> <p>1M</p>
h	State the condition for sustained oscillations.	2M
Ans:	<p>Conditions for sustained oscillations:-</p> <ol style="list-style-type: none"> 1. The total shift introduced, as the signal proceeds from input terminals through the amplifier and feedback network & back again to the input is precisely 0° or 360°. 2. The magnitude of the loop gain $A_v\beta$ must be equal to 1 at the frequency of oscillations. $ A_v\beta = 1 \ \& \ \theta = 0^\circ \ \text{or} \ 360^\circ.$	1M each
B	Attempt any TWO:	8- Total Marks
a	Draw the circuit diagram for Common Base (CB) configuration and draw its input and output characteristics.	4M
Ans:	Circuit diagram for Common Base (CB) configuration:-	2M

SUMMER- 18 EXAMINATION


Subject Name: Electronic Devices & Circuits Model Answer

Subject Code: **17319**

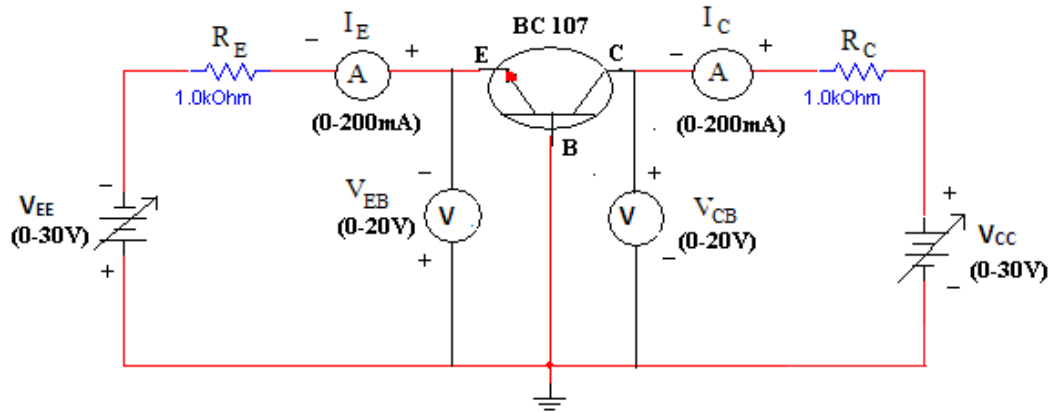

1M each

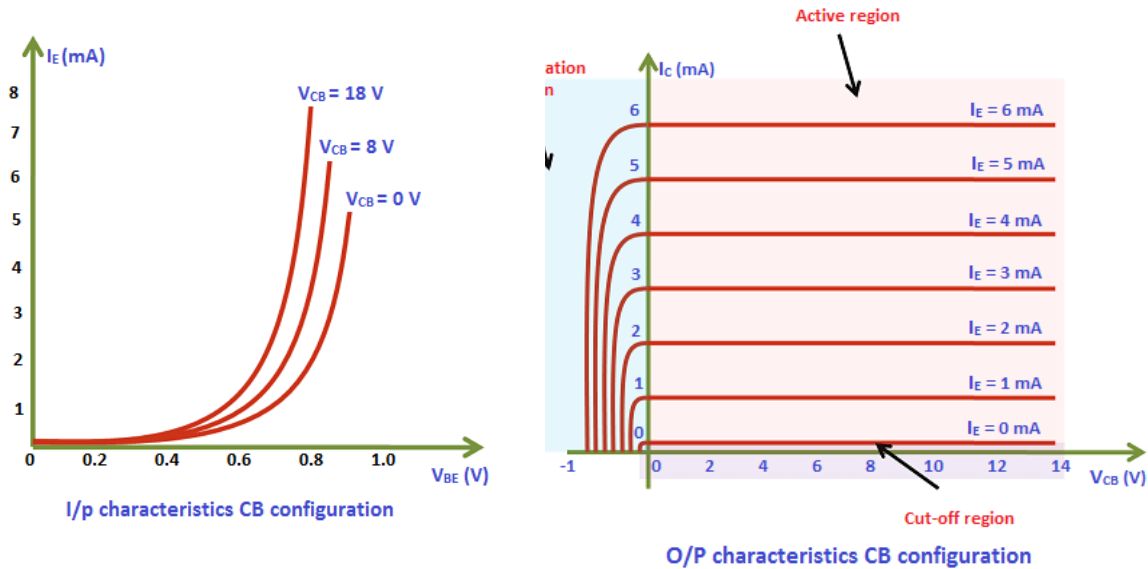Input - output characteristics of Common Base (CB) configuration:-



b List the types of transistor biasing. Draw neat circuit diagram of voltage divider biasing. **4M**

Ans: **Transistor biasing methods:-**

1. Base bias / Fixed Bias
2. Base bias with emitter feedback
3. Voltage divider bias/ Self bias
4. Emitter bias


Circuit diagram of voltage divider biasing:- **2M**



SUMMER- 18 EXAMINATION

Subject Name: Electronic Devices & Circuits Model Answer


Subject Code: **17319**

 

c Draw and explain zener diode as a voltage regulator.

4M

Ans: Circuit diagram:-

 

Part I: REGULATION BY VARYING INPUT VOLTAGE: -

A resistance (R_s) is connected in series with the zener diode to limit current in the circuit. For proper operation, the input voltage (V_s) must be greater than the zener voltage (V_z). Where, R_z = zener resistance

$$I_s = I_z + I_L$$

Here the load resistance is kept fixed and input voltage is varied within the limits

Case1:- WHEN INPUT VOLTAGE IS INCREASED

When input voltage is increased the input current (I_s) also increases. Thus current through zener diode gets increased without affecting the load current (I_L). The increase in input voltage also increases the voltage drop across the resistance R_s thereby keeping the V_L constant.

Case 2:- WHEN INPUT VOLTAGE IS DECREASED

1M
diagram,
1M
Explanation



SUMMER- 18 EXAMINATION


Subject Name: Electronic Devices & Circuits Model Answer

Subject Code: 17319

When input voltage is decreased, the input current gets reduced, as a result of this I_z also decreases. The voltage drop across R_s will be reduced and thus the load voltage V_L equal to V_z and load current (I_L) remains constant.

Part II: REGULATION BY VARYING LOAD RESISTANCE:-

In this method the input voltage is kept constant whereas load resistance R_L is varied.

 

Case 1:- WHEN LOAD RESISTANCE IS INCREASED

When load resistance is increased, the load current reduces, due to which the zener current I_z increases. Thus the value of input current and voltage drop across series resistance is kept constant. Hence the load voltage remains constant.

Case 2:- WHEN LOAD RESISTANCE IS REDUCED

When load resistance is decreased, the load current increases. This leads to decrease in I_z . Because of this the input current and the voltage drop across series resistance remains constant. Hence the load voltage is also kept constant.

1M
diagram,
1M
Explanation



SUMMER- 18 EXAMINATION

Subject Name: Electronic Devices & Circuits Model Answer



Subject Code: **17319**

Q. No .	Sub Q. N.	Answers	Marking Scheme
2		Attempt any FOUR:	16- Total Marks
	a	Describe the concept of thermal runaway. How it should be avoided?	4M
	Ans :	<p>Concept of thermal Runaway:-</p> <p>We know that $I_c = \beta I_B + (1 + \beta) I_{CO}$, where I_{CO} is the leakage current.</p> <p>I_{CO} is strongly dependent on temperature.</p> <p>The flow of collector current produces heat within the transistor.</p> <p>This raises the transistor temperature.</p> <p>If no stabilization is done, I_{CO} further increases.</p> <p>If I_{CO} increases, I_c increases by $(1 + \beta) I_{CO}$</p> <p>The increased I_c will raise the temperature of the transistor which in-turn will increase the I_{CO}. This effect is cumulative and in a fraction of a second I_c becomes so large causing transistor to burn up. This self-destruction of an unstabilized transistor is known as Thermal Runaway.</p> <div style="text-align: center;"> </div> <p>Thermal Runaway can be avoided :</p> <ol style="list-style-type: none"> 1. By keeping I_c constant. This is done by causing I_B to decrease automatically with temperature increase. 2. By using heat sink. 	3M
			1M

SUMMER- 18 EXAMINATION

Subject Name: Electronic Devices & Circuits Model Answer

Subject Code: **17319**

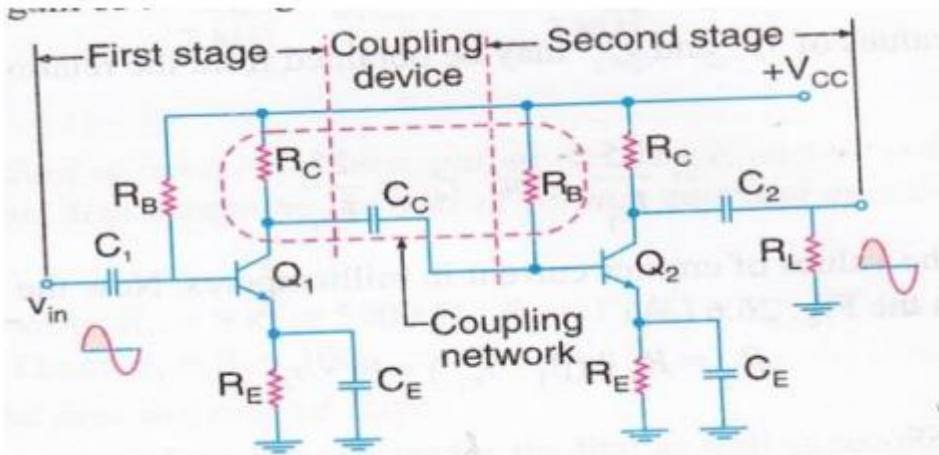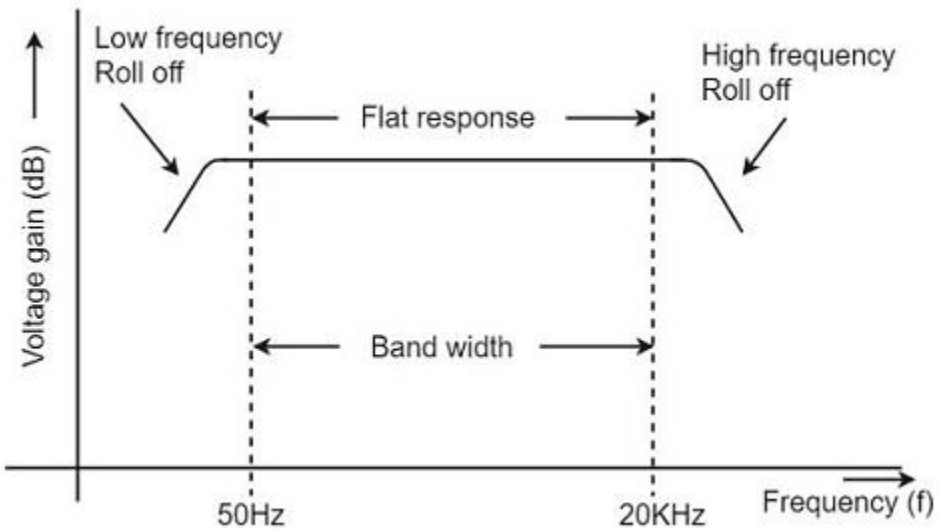
b	Draw the circuit diagram of two stage RC coupled amplifier. Draw its frequency response.	4M
Ans :	<p>Circuit diagram of two stage RC coupled amplifier:-</p>  <p>Frequency response:-</p> 	2M 2M



SUMMER- 18 EXAMINATION

Subject Name: Electronic Devices & Circuits Model Answer

Subject Code: **17319**

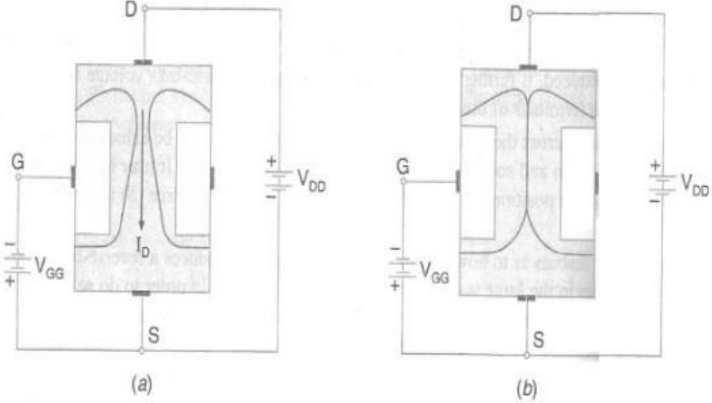c	Explain the working of N-channel JFET with neat diagram.	4M
Ans :	<p>N-Channel JFET:-</p>  <p>Working:</p> <ol style="list-style-type: none">1. The application of negative gate voltage or positive drain voltage with respect to source, reverse biases the gate- source junction of an N-channel JFET. The effect of reverse bias voltage is to form depletion regions within the channel.2. When a voltage is applied between the drain & source with dc supply voltage (V_{DD}), the electrons flows from source to drain through the narrow channel existing between the depletion regions. This constitutes the drain current (I_D) & its conventional direction is from drain to source. The value of drain current is maximum, when no external voltage is applied between the gate & source & is designated by the symbol I_{DSS}.3. When V_{GG} is increased, the reverse bias voltage across gate-source junction is increased. As a result of this depletion regions are widened. This reduces the effective width of the channel & therefore controls the flow of drain current through the channel.4. When gate to source voltage (V_{GG}) is increased further, a stage is reached at which both depletion regions touch each other as shown in fig (b).5. At this value of V_{GG}, channel is completely blocked or pinched off & drain current is reduced to zero. The value of V_{GS} at which drain current becomes zero is called pinch	2M

SUMMER- 18 EXAMINATION

Subject Name: Electronic Devices & Circuits Model Answer

Subject Code: **17319**


off voltage designated by the symbol V_P or $V_{GS(OFF)}$. The value of V_P is negative for N-channel JFET.

d List the types of feedback connection. Draw block diagram representation of them.

4M


Ans : **Types of feedback connection:-**

1. Positive Feedback

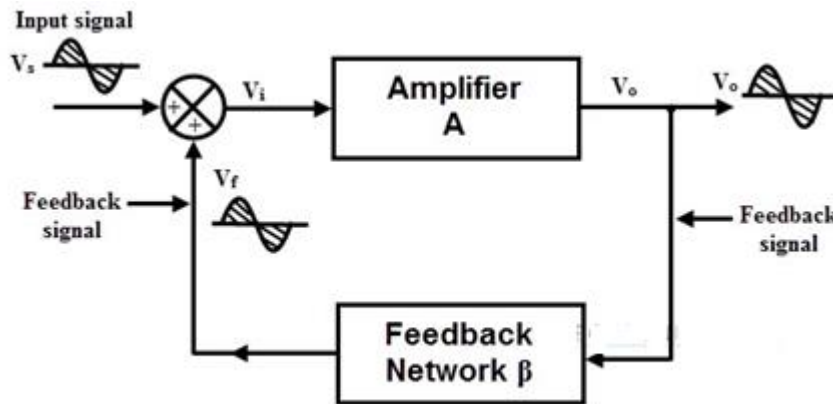

2M

2. Negative Feedback

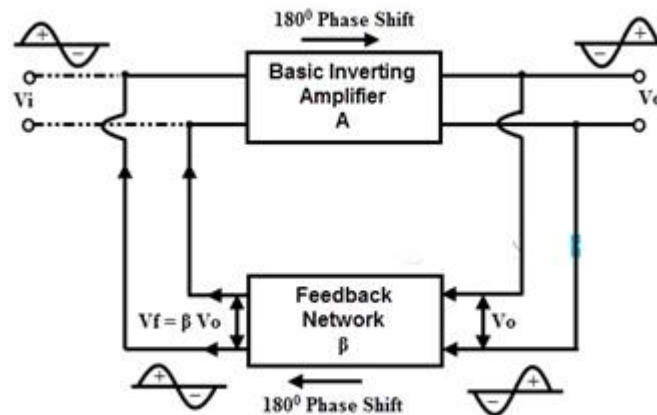

2M

(OR)

Types of negative Feedback:-

1. Voltage Series Negative feedback amplifier
2. Voltage Shunt Negative feedback amplifier
3. Current series Negative feedback amplifier
4. Current shunt Negative feedback amplifier

e Draw and explain UJT relaxation oscillator with input and output waveforms.

4M

SUMMER- 18 EXAMINATION

Subject Name: Electronic Devices & Circuits Model Answer

Subject Code: **17319**



SUMMER- 18 EXAMINATION

Subject Name: Electronic Devices & Circuits Model Answer

Subject Code: **17319**


		<p>WORKING:-</p> <p>In above figure, transistor is connected in series with load, therefore the circuit is known as a series regulator.</p> <p>The transistor behaves as variable resistance whose value is determined by the amount of base current.</p> $V_L = V_Z - V_{BE}$ <p style="text-align: center;">(OR)</p> $V_{BE} = V_Z - V_L \dots\dots\dots\text{Equation 1}$ <p>Suppose that value of load resistance is increased. Because of this, the load current decreases and load voltage (V_L) tend to increase. From equation (1) that any increase in V_L will decrease V_{BE} because V_Z value is fixed.</p> <p>As a result of this, forward bias of the transistor is reduced. This reduces its level of conduction. This increases V_{CE} of transistor which will slightly decrease the input current for the increase in the value of load resistance so that load voltage remains constant.</p> <p>If the output voltage decreases, then exactly opposite action will take place and output voltage is regulated.</p> <p>The output of a transistor series regulator is approximately equal to zener voltage (V_Z) This regulator can also be used for larger load currents.</p>	2M
Q. No.	Sub Q. N.	Answers	Marking Scheme
3		Attempt any FOUR:	16- Total Marks
	a	<p>Compare CB, CE and CC configuration on the basis of,</p> <ul style="list-style-type: none"> (i) Input Impedance (R_i) (ii) Output Impedance (R_o) (iii) Voltage gain (A_v) (iv) Current gain (A_i) 	4M



SUMMER- 18 EXAMINATION

Subject Name: Electronic Devices & Circuits Model Answer

Subject Code: **17319**
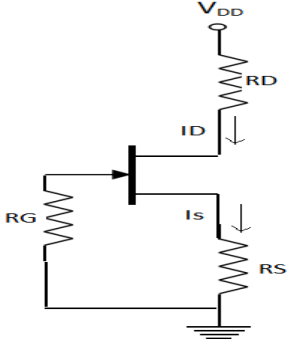
<p>Ans :</p>	<table border="1"> <thead> <tr> <th>Parameter</th> <th>Common Base</th> <th>Common Emitter</th> <th>Common Collector</th> </tr> </thead> <tbody> <tr> <td>Input Impedance</td> <td>Low (50 Ohm)</td> <td>Moderate (1 KOhm)</td> <td>High (300 KOhm)</td> </tr> <tr> <td>Output Impedance</td> <td>High (1 M Ohm)</td> <td>Moderate (50 K)</td> <td>Low (300 Ohm)</td> </tr> <tr> <td>Voltage Gain</td> <td>High</td> <td>Higher than CB</td> <td>Less than Unity</td> </tr> <tr> <td>Current Gain</td> <td>Less than Unity</td> <td>High</td> <td>Very High</td> </tr> </tbody> </table>	Parameter	Common Base	Common Emitter	Common Collector	Input Impedance	Low (50 Ohm)	Moderate (1 KOhm)	High (300 KOhm)	Output Impedance	High (1 M Ohm)	Moderate (50 K)	Low (300 Ohm)	Voltage Gain	High	Higher than CB	Less than Unity	Current Gain	Less than Unity	High	Very High	<p>1M each (numerical values for parameters are optional)</p>
Parameter	Common Base	Common Emitter	Common Collector																			
Input Impedance	Low (50 Ohm)	Moderate (1 KOhm)	High (300 KOhm)																			
Output Impedance	High (1 M Ohm)	Moderate (50 K)	Low (300 Ohm)																			
Voltage Gain	High	Higher than CB	Less than Unity																			
Current Gain	Less than Unity	High	Very High																			
<p>b</p>	<p>Draw the circuit diagram of self-bias method of JFET and describe its working.</p>	<p>4M</p>																				
<p>Ans :</p>	<p>Self Biasing Method:-</p> <p>The self-bias configuration for FET(dc equivalent circuit) is as shown in fig. This configuration eliminates the need of two dc power supplies.</p>  <p>JFET must be operated such that the gate source junction is always reverse biased. This condition requires a negative V_{GS} for n channel JFET. This can be achieved using the self bias arrangement as above –</p> <p>The resistor R_G does not affect the bias because it has essentially no voltage drop across it and therefore gate remains at 0V. R_G is necessary only to isolate an ac signal from ground in amplifier application.</p> <p>From above diagram $I_S = I_D$ & $V_G = 0$ \therefore voltage across $R_S = V_{RS} = I_S \cdot R_S = I_D \cdot R_S$</p> <div style="border: 1px solid black; padding: 5px; display: inline-block;"> $\therefore V_S = I_D \cdot R_S$ </div> $V_{GS} = V_G - V_S$ $= 0 - I_D \cdot R_S$	<p>Diagram-2M Working-2M</p>																				



SUMMER- 18 EXAMINATION

Subject Name: Electronic Devices & Circuits Model Answer

Subject Code: **17319**

$$V_{GS} = - I_D \cdot R_S$$

From Shockley's equation the drain current is:

$$I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_{GS(off)}} \right]^2$$

Substitute the value of $V_{GS} = - I_D \cdot R_S$

$$I_D = I_{DSS} \left[1 - \frac{I_D \cdot R_S}{V_{GS(off)}} \right]^2$$

$$I_D = I_{DSS} \left[1 + \frac{I_D R_S}{V_{GS(off)}} \right]^2$$

The drain voltage with respect to ground is determined as follows –

$$V_D = V_{DD} - I_D R_D$$

$$V_S = I_D R_S$$

The drain to source voltage is –

$$V_{DS} = V_D - V_S.$$

$$V_{DS} = (V_{DD} - I_D R_D) - I_D R_S$$

$$V_{DS} = V_{DD} - I_D R_D - I_D R_S$$

Q point of self Bias circuit is located as –

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

$$V_{GS} = - I_D R_S$$



$$I_D = I_{DS} \left[1 + \frac{I_D R_S}{V_{GS(off)}} \right]^2$$

$$V_{DS} = V_{DD} - I_D R_D - I_D R_S$$

SUMMER- 18 EXAMINATION

Subject Name: Electronic Devices & Circuits Model Answer

Subject Code: 17319

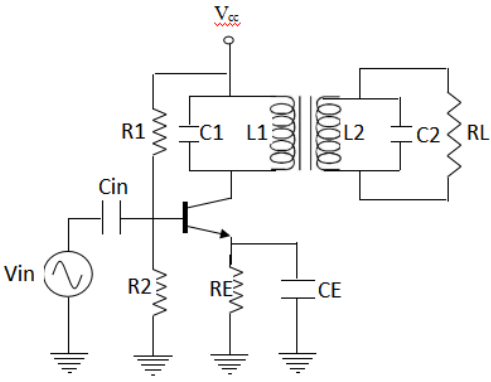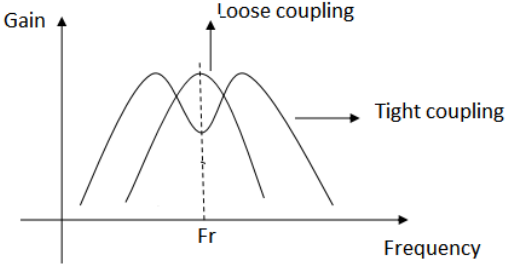c	Draw the circuit diagram of double tuned amplifier and describe its working.	4M
Ans :	<p>Circuit diagram:-</p>  <p>Working:-</p> <p>When a signal containing many frequencies is applied at the input, the frequency corresponding to the resonant freq. of tuned circuit comprising of C_1 & L_1 is selected, and other frequencies are rejected. The tuned circuit offers very high impedance to this signal frequency. Amplified output appears across the tuned circuit $L_1 C_1$. The output from this tuned circuit is transferred to the second tuned circuit $L_2 C_2$ through mutual induction. Frequency response of doubled tuned circuit depends upon the magnetic coupling of L_1 & L_2.</p> <p>A frequency response curve of a typical doubled tuned circuit at different coupling condition is shown –</p>  <p>From above it is seen that most suitable curve is one when optimum coefficient of coupling exists between the tuned circuits. In this condition, the circuit is highly selective & also provides sufficient amount of gain for a particular band of freq.</p> <p>Thus by adjusting coupling between two coils the required result can be obtained.</p>	Diagram-2M Working-2M



SUMMER- 18 EXAMINATION

Subject Name: Electronic Devices & Circuits Model Answer


Subject Code: **17319**

(frequency response curve is optional. Marks may be awarded even if it is not drawn.)

d Draw pin diagram of IC 723. Give any four important features of IC 723.

4M

Ans :
Pin diagram of IC 723:

 

Important features of 723:

The important features of IC 723 regulator is as given below:

- It is small in size and less in cost.
- Positive or negative supply operation.
- Unregulated dc supply voltage at the input between 9.5V and 40V
- Output voltage adjustable from 2 V to 37 V.
- Maximum load current of 150 mA
- With additional transistor used, I_{Lmax} upto 10A is available
- Internal power dissipation of 800mW
- Wide variety of applications such as series, shunt, switching and floating regulators.
- Relative simplicity with power supply can be designed.
- Low standby current gain.
- Very low temperature drift
- High ripple rejection.
- Built in fold back current limiting.
- Built in short circuit protection.
- Load and line regulations of 0.03%

Any four features-

1/2 M each

e Draw and explain transistorized crystal oscillator.

4M

SUMMER- 18 EXAMINATION

Subject Name: Electronic Devices & Circuits Model Answer

Subject Code: **17319**

Ans :	<p>Circuit Diagram:</p> <div style="text-align: center;"> </div> <p>Working:-</p> <p>When the power is turned on, capacitor C_1 is charged. When this capacitor discharges, it sets up oscillations. The voltage across L_1 is applied to coil L_2 due to mutual inductance. This positive feedback causes the oscillator to produce oscillations. The frequency of oscillations in the circuit is controlled by the crystal. As the crystal is connected in the base circuit its influence on the frequency of the circuit is much more than LC circuit. The entire circuit vibrates at the natural frequency of the crystal. As the frequency of the crystal is independent of temperature, the circuit generates a constant frequency.</p>	Circuit Diagram-2M Explanation-2M
f	Draw and explain class-B push pull amplifier.	4M
Ans :	<div style="text-align: center;"> </div> <p>Circuit operation:-</p> <p>When there is no signal, both the transistor Q_1 and Q_2 are cut off. Hence no current is drawn from the V_{CC} supply. Thus there is no power wasted.</p> <p>Consider positive half cycle of the input signal the base of Q_1 becomes positive and the base of Q_2</p>	Diagram-2M Explanation-2M



SUMMER- 18 EXAMINATION

Subject Name: **Electronic Devices & Circuits Model Answer**

Subject Code: **17319**

negative. Therefore Q₁ conducts (ON) and Q₂ is OFF

When negative half cycle is applied across input, the base of Q₁ becomes negative and the base of Q₂ is positive. Therefore Q₁ is OFF and Q₂ conducts. only i_{c2} flows and i_{c1} = 0. A negative sinusoidal voltage will appear across load.

Thus at any instant only one transistor will conduct. When Q₁ conducts, only i_{c1} flows and i_{c2} = 0. A positive sinusoidal voltage will appear across load.

Q. No.	Sub Q. N.	Answers	Marking Scheme
4		Attempt any FOUR:	12- Total Marks
	a	Define α and β of the transistor. Derive the relationship between α and β.	4M
	Ans :	<p>Alpha(α) :It is a large signal current gain in common base configuration. It is the ratio of collector current (output current) to the emitter current (input current).</p> <p>Beta (β):It is a current gain in the common emitter configuration. It is the ratio of collector current (output current) to base current (output current).</p> <p>Relation between α& β:</p> <p>Current gain (α) of CB configuration = $\frac{I_C}{I_E}$</p> <p>Current gain of (β) of CE configuration = $\frac{I_C}{I_B}$</p> <p>We know that ;</p> $I_E = I_B + I_C \dots\dots\dots(1)$ <p>Dividing equation (1) by I_C</p> $\frac{I_E}{I_C} = \frac{I_B}{I_C} + \frac{I_C}{I_C}$ <p>Therefore $\frac{1}{\alpha} = \frac{1}{\beta} + 1$ [since $\alpha = \frac{I_C}{I_E}$, $\beta = \frac{I_C}{I_B}$]</p> <p>Therefore $\frac{1}{\alpha} = \frac{1+\beta}{\beta}$</p> <p>$\alpha (1 + \beta) = \beta$</p> <p>$\alpha + \alpha \beta = \beta$</p> <p>$\alpha = \beta - \alpha \beta$</p> <p>$\alpha = \beta(1 - \alpha)$</p>	<p>Definition α and β-1M each</p> <p>Derivation- 2M</p>



SUMMER- 18 EXAMINATION

Subject Name: **Electronic Devices & Circuits Model Answer**

Subject Code: **17319**

Therefore $\beta = \frac{\alpha}{1-\alpha}$ OR $\alpha = \frac{\beta}{1+\beta}$

Note: Any other appropriate method for derivation can also be considered and marks awarded.

b Compare Class A, Class B, Class C & Class AB power amplifier.

4M

Ans :

Class A	Class B	Class C	Class AB
Conducts for (360°) full cycle of input signal	(180°) half cycle of input signal	Less than 180° of input signal.	Greater than 180° and less than 360°
Q point is at the centre of load line	On X axis	Below X axis	Just above X axis
No distortion	More than class A	More than A, B, AB	Less distortion.
lowest efficiency 25% to 50%	Above 78.5%	Above 95%	Between 50 to 78.5%
Power dissipation very high	low	Very low	Moderate.

Any 4 point-1m each

c Explain the working of N-channel D-MOSFET.

4M

Ans : **Circuit Operation:-**

 


Diagram-2m

Working-2M



SUMMER- 18 EXAMINATION

Subject Name: **Electronic Devices & Circuits Model Answer**

Subject Code: **17319**

The gate to source voltage is set to zero volts by the direct connection from one terminal to the other. & voltage V_{DS} is applied across the drain to source terminals. This results the attraction by the free electrons of the n channel due to positive drain & I_{DSS} establish in the circuit.

For negative voltage at gate, the gate will tend to repel free electrons towards P type substrate and attract holes toward insulated layer. Recombination occurs between electron & holes that will reduce the number of free electron in the channel for conduction. So drain current reduces. The value of voltage of V_{GS} at which drain current nearly becomes zero is called cut off voltage.

When gate is positive with respect to source then positive V_{GS} draws additional electrons from the P type substrate. Thus drain current (I_D) increases as increase in positive value.

d Draw and explain transistor as a switch with neat input and output waveforms.

4M

Ans
:


 


Diagram-1
Explanation-
2M
Waveform-
1M

When a sufficient voltage ($V_{in} > 0.7 V$) is applied between the base and emitter, collector to emitter voltage is approximately equal to 0. Therefore, the transistor acts as a short circuit. The collector current V_{cc}/R_c flows through the transistor. Therefore switch is ON.

Similarly, when no voltage or zero voltage is applied at the input, transistor operates in cutoff region and acts as an open circuit. Therefore switch is OFF.

Waveform:

 



SUMMER- 18 EXAMINATION

Subject Name: Electronic Devices & Circuits Model Answer

Subject Code: **17319**

e	<p>In UJT sweep circuit, calculate time period and frequency of oscillation if $\eta = 0.65$ and $R = 2 \text{ k}\Omega$</p>	4M
Ans :	$t = 2.3RC \log_{10} \left(\frac{1}{1-\eta} \right)$ <p>Assume $C = 0.1 \mu F$</p> $t = 2.3 \times 2 \times 10^3 \times 0.1 \times 10^{-6} \times \log_{10} \left(\frac{1}{1-0.65} \right)$ $t = 0.2097 \text{ ms}$ $f = \frac{1}{t}$ $f = \frac{1}{0.2097 \times 10^{-3}}$ $f = 4.7687 \text{ kHz}$	<p>Time period and frequency of oscillation - 2M each</p> <p>(marks may be given if any other value of C is assumed and calculation done accordingly)</p>
f	<p>Draw the block diagram of regulated power supply. State the function of each block.</p>	4M
Ans :	<p>Block Diagram of Regulated power supply:</p> <p>Block diagram of a regulated Dc power supply consist of the following blocks namely:</p> <ol style="list-style-type: none"> 1) Transformer 2) Rectifier 3) Filter 4) Voltage regulator. <ol style="list-style-type: none"> 1. Transformer:- The AC main voltage is applied to a step down transformer. It reduces the amplitude of ac voltage and applies it to a rectifier. 2. Rectifier: The rectifier is usually centre tapped or bridge type full wave rectifier. It converts the ac voltage into a pulsating dc voltage. 3. Filter: The pulsating dc (or rectified ac) voltage contains large ripple. This voltage is applied to the filter circuit and it removes the ripple. The function of a filter is to remove 	<p>Block Diagram-2M</p> <p>Function-2M</p>



SUMMER- 18 EXAMINATION

Subject Name: **Electronic Devices & Circuits Model Answer**

Subject Code: **17319**

the ripples to provide pure DC voltage at its output.

This DC output voltage is not a steady DC voltage but it changes with the change in load current. It has poor load and line regulation. The voltage obtained is unregulated DC voltage.

4. Voltage Regulator: The unregulated DC voltage is applied to a voltage regulator which makes this DC voltage steady and independent of variation in load and mains AC voltage .This improves the load and line regulation and provides the regulated DC voltage across the load.

Q. No .	Sub Q. N.	Answers	Marking Scheme
5		Attempt any FOUR:	16- Total Marks

a	Explain the concept of dc load line analysis.	4M
----------	--	-----------

Ans :	<p>Concept of DC load line:-</p> <p>For proper operation of a transistor a fixed level of certain currents and voltage in a transistor are set. These values of current and voltage define the point at which the transistor operates. This point is called operating point. It is also known as quiescent point or simply Q-point.</p> <p>Consider the transistor circuit shown in the figure above for this circuit we know that the value of collector current is given by the relation.</p> $I_C = \frac{V_{CC} - V_{CE}}{R_C} \dots \dots \dots \text{Equation (i)}$	<p>1 Mark for Concept</p> <p>2 Mark for Explanation</p>
-------	--	---



SUMMER- 18 EXAMINATION

Subject Name: Electronic Devices & Circuits Model Answer

Subject Code: **17319**

Where ,

V_{CC} = The value of DC supply voltage in the collector circuit.


V_{CE} = The value of collector to emitter, and

R_C = The Value of collector resistance

The value of collector to emitter voltage (V_{CE}) at saturation point, is very small as compared to V_{CC} supply. Therefore the collector current at saturation point is

$$I_C = \frac{V_{CC}}{R_C} \dots\dots\dots \text{Equation(ii)}$$

 The value of collector current at saturation point designated as $I_{C(sat)}$ may be obtained by dividing the value of V_{CC} supply by the value of collector resistance R_C . This value gives us upper end of the load line as shown in the figure.



1 Mark for Load line

At cut off point, the value of collector current is zero.

substituting $I_C = 0$ in equation(i)

$$0 = \frac{V_{CC} - V_{CE}}{R_C}$$

(OR)

$$V_{CE} = V_{CC} = V_{CE(cut\ off)} \dots\dots\dots \text{Equation (iii)}$$

Equation (iii) gives us the lower end of the load line as shown in the above figure.

The region lying in between saturation and cutoff points of the load line is called active region of the transistor operation. Equation (i),(iii) are the Q point coordinates of DC load line.

SUMMER- 18 EXAMINATION


Subject Name: Electronic Devices & Circuits Model Answer

Subject Code: **17319**


b Draw the circuit diagram of single stage CE amplifier. State the function of each component.

4M

 Ans : Single stage CE amplifier Circuit diagram:



(OR)

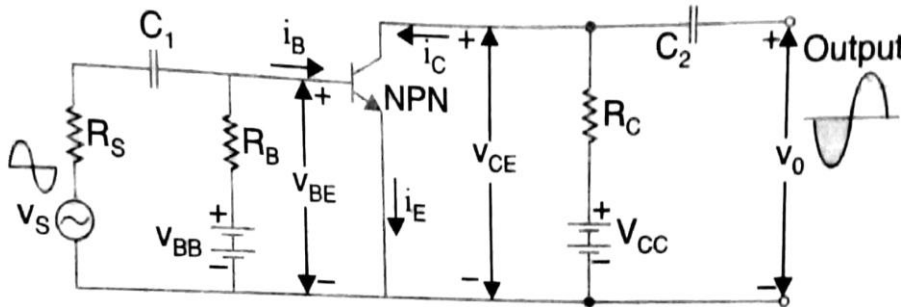

Function of each component:

- The potential divider biasing is provided by resistors R_1 , R_2 and R_E . It provides good stabilization of the operating point.
- The capacitors C_1 and C_2 are called the coupling capacitors and are used to pass the AC voltage signals from one side to the other. At the same time, they do not allow the DC voltage to pass through. Hence they are also known as blocking

2 Marks for any Circuit diagram

2 Marks for Function of each component



SUMMER- 18 EXAMINATION

Subject Name: Electronic Devices & Circuits Model Answer


Subject Code: **17319**

capacitors.

- The capacitor C_E works as a bypass capacitor. It bypasses all the AC currents from the emitter to the ground and avoids the negative current feedback. It increases the output AC voltage.
- The resistance R_L represents the resistance of whatever is connected at the output. It may be load resistance or input resistance of the next stage.

c Draw drain characteristics of JFET and explain ohmic and pinch-off region. **4M**

Ans : Drain characteristics of JFET :

 

Ohmic Region : This regions is shown as a curve OA in the figure. In this region, the drain current increases linearly with the increase in drain-to-source voltage, obeying Ohm's law. The linear increase in drain current is due to the fact that N-type semiconductor bar acts like a simple resistor.

Pinch off region: This regions is shown by the curve BC. It is also called **saturation region** or constant current region. This means the drain current remains constant at its maximum value (i.e. I_{DSS}). The drain current in the pinch off region, depends upon the gate-to-source voltage and is given by the relation

2 Marks for Drain characteristic

2 Marks for explanation of regions

SUMMER- 18 EXAMINATION

Subject Name: Electronic Devices & Circuits Model Answer

Subject Code: **17319**

<p>Ans : :</p>		<p>4 Marks</p>
<p>f</p>	<p>Draw Bootstrap amplifier and describe its working.</p>	<p>4M</p>
<p>Ans : :</p>	<p>Bootstrap amplifier:</p> <p>Here transistor Q_1 acts as a switch and transistor Q_2 acts as an emitter follower (i.e. a unit gain amplifier).</p> <p>Circuit Operation:</p>	<p>2 Marks for diagram</p> <p>2 Marks for working</p>



SUMMER- 18 EXAMINATION

Subject Name: Electronic Devices & Circuits Model Answer

Subject Code: **17319**

Initially transistor Q_1 is ON and Q_2 is OFF. Therefore capacitor C_1 is charged to V_{CC} through the diode forward resistance (R_F). At this instance output voltage is zero.

When negative pulse is applied to the base of transistor Q_1 , it turns OFF. Since transistor Q_2 is an emitter follower, therefore the output voltage V_0 is same as base voltage of transistor Q_2 .

When Q_1 turns OFF, the capacitor C_1 starts charging capacitor C through resistor (R). As a result of these both the base voltage of Q_2 and output voltage begins to increase from zero.

As the output voltage increases diode D becomes reverse biased, because of the fact that the output voltage is coupled through the capacitor (C_1) to the diode.

Since the value of capacitor (C_1) is much larger than that of capacitor (C), the voltage across capacitor (C_1) practically remains constant.

Thus voltage drop across resistor (R) and hence current (IR) remains constant, means capacitor C is charged with constant current.

This causes voltage across capacitor C (and hence the output voltage) to increase linearly with time.

The circuit pulls itself up by its own bootstrap and hence it is known as bootstrap sweep circuit.

Q. No.	Sub Q. N.	Answers	Marking Scheme										
6		Attempt any FOUR:	16- Total Marks										
	a	Compare RC coupled, direct coupled and transformer coupled amplifier.	4M										
	Ans :	<table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 8%;">Sr.No</th> <th style="width: 20%;">Particulars</th> <th style="width: 20%;">RC coupled</th> <th style="width: 20%;">Direct coupled</th> <th style="width: 20%;">Transformer coupled</th> </tr> </thead> <tbody> <tr> <td style="text-align: center;">1</td> <td>Frequency Response</td> <td>Excellent in the audio frequency range</td> <td style="text-align: center;">Best</td> <td style="text-align: center;">Poor</td> </tr> </tbody> </table>	Sr.No	Particulars	RC coupled	Direct coupled	Transformer coupled	1	Frequency Response	Excellent in the audio frequency range	Best	Poor	4Marks (any four points each carry one mark)
Sr.No	Particulars	RC coupled	Direct coupled	Transformer coupled									
1	Frequency Response	Excellent in the audio frequency range	Best	Poor									



SUMMER- 18 EXAMINATION

Subject Name: Electronic Devices & Circuits Model Answer

Subject Code: **17319**

2	Cost	Less	Least	More
3	Space and weight	Less	Least	More
4	Impedance matching	Not good	Good	Excellent
5	Coupling elements	R and C	No element	Transformer
6	Distortion	Amplitude	No distortion	Frequency
7	Voltage gain	Least	Less	More
8	Use	For voltage amplification	For amplifying extremely low frequencies	For power amplification

b State the meaning of positive and negative feedback. State four advantages of negative feedback.

4M

Ans :

Positive feedback :If the feedback signal (voltage or current) is applied in such a way that it is in phase with the input signal and thus increases it, then it is called a positive feedback. It is also known as regenerative feedback or direct feedback.

Negative feedback: If the feedback signal (voltage or current) is applied in such a way that it is out of phase with the input signal and thus decreases it, then it is called a negative feedback. It is also known as degenerative feedback or inverse feedback.

Advantages of negative feedback :

1. Bandwidth is increased.
2. Noise is decreased
3. Stability is increased
4. Less amplitude and harmonic distortion
5. Less frequency distortion.

2 Marks for meaning of positive and negative feedback

2 Marks for any four advantages



SUMMER- 18 EXAMINATION

Subject Name: Electronic Devices & Circuits Model Answer


Subject Code: **17319**

	6. Input and output resistance can be modified as desired. 7. Less phase distortion	
c	Define the terms Line and Load regulation.	4M
Ans :	<p>Line Regulation: The line regulation rating of a voltage regulator indicates the change in output voltage that will occur per unit change in the input voltage.</p> <p>Mathematically,</p> $\text{Line Regulation} = \frac{\Delta V_L}{\Delta V_S}$ <p>Where ΔV_L = the change in output voltage and ΔV_S = the change in input voltage</p> <p>Load Regulation:</p> <p>The load regulation indicates the change in output voltage that will occur per unit change in load current.</p> <p>Mathematically,</p> $\text{Load Regulation} = \frac{V_{NL} - V_{FL}}{\Delta I_L}$ <p>Where V_{NL} = No load output voltage V_{FL} = Full load output voltage ΔI_L = Change in load current demand</p>	2 Marks for Line regulation 2 Marks for Load regulation
d	Draw I-V characteristics of UJT and label different regions on it.	4M
Ans :		2 Marks for Characteristic

SUMMER- 18 EXAMINATION

Subject Name: Electronic Devices & Circuits Model Answer

Subject Code: **17319**

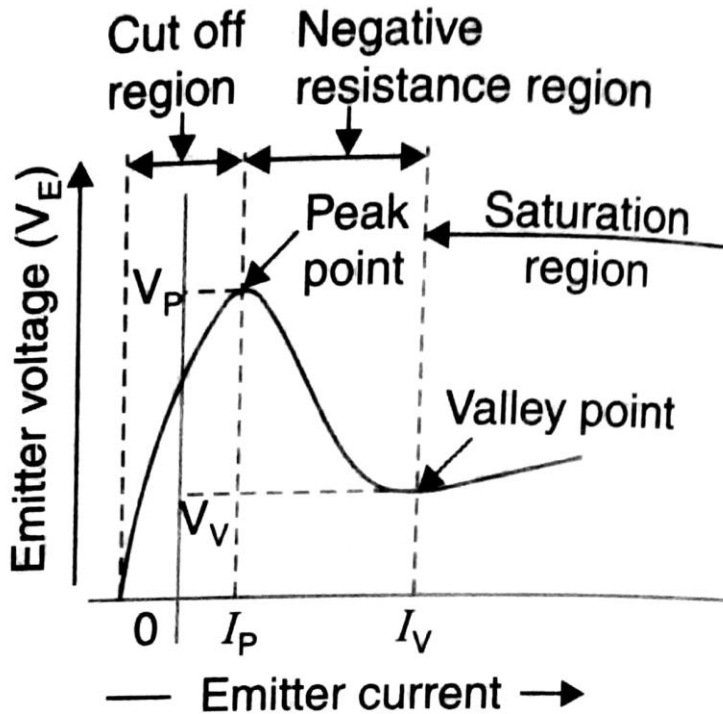


s

2 Marks for labeling

e Draw the circuit diagram of fixed bias circuit. Write its working.

4M

Ans :

 

2 Marks for Diagram

Applying KVL for the given loop

$$I_B \cdot R_B + V_{BE} - V_{CC} = 0$$

or the base current,

2 Marks for working



SUMMER- 18 EXAMINATION

Subject Name: **Electronic Devices & Circuits Model Answer**

Subject Code: **17319**

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} \dots\dots\dots \text{Equation (i)}$$

Since the supply voltage V_{CC} and the base emitter voltage V_{BE} have fixed values of voltage, the selection of base bias resistor R_B fixes the value of base current. Thus the equation (i) may be simplified as

$$I_B = \frac{V_{CC}}{R_B} \dots\dots\dots \text{(Since } V_{CC} \text{ is much greater than } V_{BE}\text{)}$$

Now consider the collector emitter circuit loop in the base bias circuit and applying the KVL for this loop,

$$I_C \cdot R_C + V_{CE} = V_{CC}$$

$$V_{CE} = V_{CC} - I_C \cdot R_C \dots\dots\dots \text{Equation (ii)}$$

The above equation gives the voltage drop across the collector emitter terminals of the transistor. The value of collector current is given by

$$I_C = \beta \cdot \frac{V_{CC}}{R_B} = \frac{V_{CC}}{R_B/\beta} \dots\dots\dots \text{Equation (iii)}$$

From above, collector current I_C is β times greater than base current and is not dependent on resistance of collector circuit (R_C).

I_{CE} and V_{CE} are dependent on β . But β is dependent on temperature.

It is impossible to obtain a stable 'Q' point in a fixed bias circuit.

Because of this fact, base bias is never used in amplifier circuit.

f Compare BJT and FET (any four points)

4M

Ans
:

Sr.No	Bipolar Junction Transistor(BJT)	Field Effect Transistor(FET)
1	It is bipolar device i.e. current in the device is carried either by both electrons & holes	It is unipolar device i.e. current in the device is carried either by electrons or holes



4 Marks for any four points



SUMMER- 18 EXAMINATION

Subject Name: **Electronic Devices & Circuits Model Answer**

Subject Code: **17319**

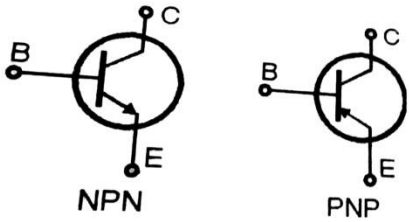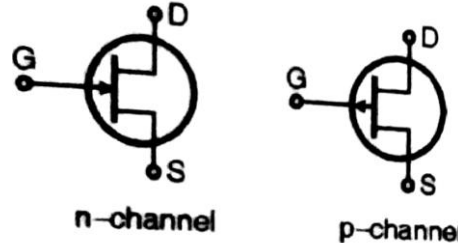2	It is a current controlled device i.e. the base current controls the amount of collector current.	It is a voltage controlled device i.e. voltage at the gate (or drain) terminal controls amount of current flowing through the device.
3	Input resistance is very low compared to FET.	Input resistance is very high
4	It has a positive temperature coefficient at high current levels. It means that current increases as temperature increases.	It has a negative temperature coefficient at high current levels. It means that current decreases as temperature increases.
5	It is more noisy.	It is less noisy.
6	It has higher gain bandwidth product as compared to FET	It has lower gain bandwidth product as compared to BJT.
7	It is comparatively difficult to fabricate on IC & occupies more space on chip compared to FET.	It is simpler to fabricate on IC & occupies less space on chip compared to BJT.
8	Transfer characteristics are linear	Transfer characteristics are non-linear
9	Thermal runaway can damage the BJT	Thermal runaway does not take place
10	Symbol:  NPN PNP	Symbol:  n-channel p-channel