



WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

1

Important Instructions to examiners:

- 1) The answers should be examined by key words and not as word-to-word as given in the model answer scheme.
- 2) The model answer and the answer written by candidate may vary but the examiner may try to assess the understanding level of the candidate.
- 3) The language errors such as grammatical, spelling errors should not be given more importance (Not applicable for subject English and Communication Skills).
- 4) While assessing figures, examiner may give credit for principal components indicated in the figure. The figures drawn by candidate and model answer may vary. The examiner may give credit for any equivalent figure drawn.
- 5) Credits may be given step wise for numerical problems. In some cases, the assumed constant values may vary and there may be some difference in the candidate's answers and model answer.
- 6) In case of some questions credit may be given by judgement on part of examiner of relevant answer based on candidate's understanding.
- 7) For programming language papers, credit may be given to any other program based on equivalent concept.

Q. No.	Sub Q. N.	Answers	Marking Scheme
1	(A)	Attempt any FIVE of the following:	10- Total Marks
	(a)	Define: (i) Apparent power (ii) Real power	2M
	Ans:	(i) Apparent power It is the product of rms values of applied voltage and circuit current. Unit: volt-ampere (VA) OR kilo-volt-ampere (kVA) OR Mega-volt-ampere (MVA) $S = VI = I^2 Z$ volt-ampere (VA) (ii) Real power The active power is defined as the average power P_{avg} taken by or consumed by the given circuit. (OR)	1 M for each definition



WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

2

	It is the power which is actually dissipated in the circuit resistance. $P = V.I.\cos\phi$ Unit: - Watt OR Kilowatt	
(b)	Write equation of resultant impedance in R-L circuit.	2M
Ans:	The equation of resultant impedance in R-L circuit $Z = \sqrt{(R^2 + X_L^2)}$ Where ,R=Resistance $X_L = \text{Inductive Reactance} = 2\pi fL \Omega.$	2 M for equation
(c)	State condition for resonance in R-L-C series circuit.	2M
Ans:	The condition for resonance in R-L-C series circuit. i) Inductive Reactance should be equal to capacitive reactance. That is $X_L = X_C$ ii) The power factor of the circuit is $\cos \phi = 1$ iii) The voltage and current in the R-L-C series circuit are in phase with each other. iv) Current in the circuit is maximum and given by $I = V/R.$ v) Impedance of the circuit is minimum and given by $Z = R.$	2M for any two conditions
(d)	Draw – (i) Practical voltage source (ii) Ideal current source	2M
Ans:	i) Practical voltage source	1 M for each diagram


WINTER-19 EXAMINATION

Subject Name: Electric circuits and network


Subject Code: 22330

Model Answer

3

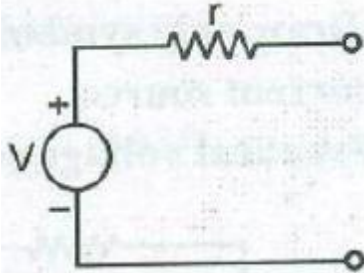

ii) Ideal current source

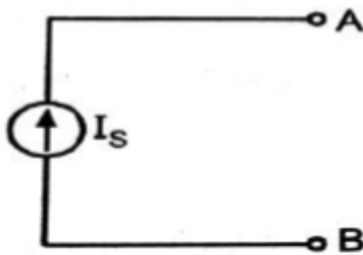


Where,
 I_s = Current Source
 R_s = internal resistance of source

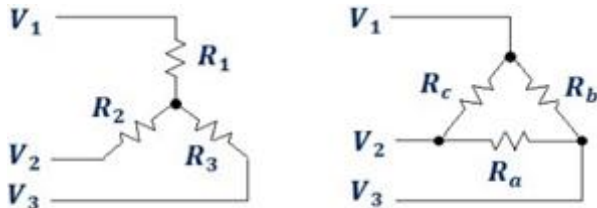e) Write formula for star to delta and delta to star transformation.

2M

Ans: The formula star to delta conversion



$$R_a = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3}$$

1 M for
star to
delta
transfor
mation

1 M for
delta to
star
transfor
mation

WINTER-19 EXAMINATION


Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

4

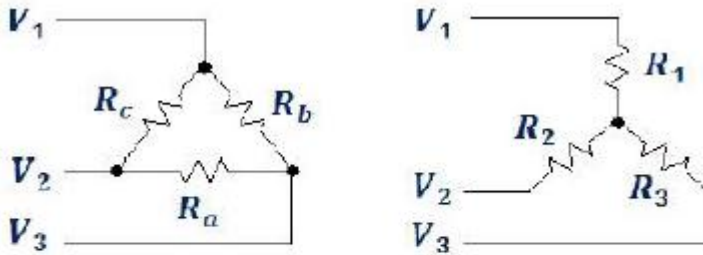The formula for Delta to Star conversion-



$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$


$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

f) State maximum power transfer theorem.

2M

Ans: Maximum Power Transfer Theorem states that "Maximum power is transferred from the source to the load when the load resistance is equal to the Thevenin's equivalent resistance of the given circuit as seen from load terminals"
.i. e, $R_L = R_{TH}$

2M for statement

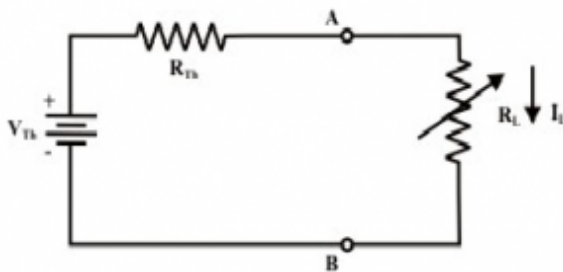

g) Write equation of short circuit Y parameters.

2M

Ans: The equation of short circuit Y parameters.

1 M for each equation



WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code:

22330


Model Answer

5

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \dots\dots\dots 1$$
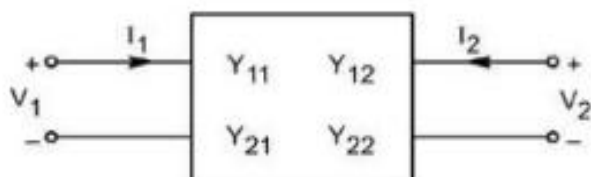
$$I_2 = Y_{21} V_1 + Y_{22} V_2 \dots\dots\dots 2$$



Q. No.	Sub Q. N.	Answers	Marking Scheme
2		Attempt any THREE of the following:	12- Total Marks
	a)	For R-C series circuit draw (i) Circuit diagram (ii) Vector diagram (iii) Waveform of voltage and current	4M
	Ans:	i)Circuit diagram	1M- circuit diagram, 1M- vector diagram, 2M- wavefor ms

WINTER-19 EXAMINATION


Subject Name: Electric circuits and network

Subject Code:


22330

Model Answer

6

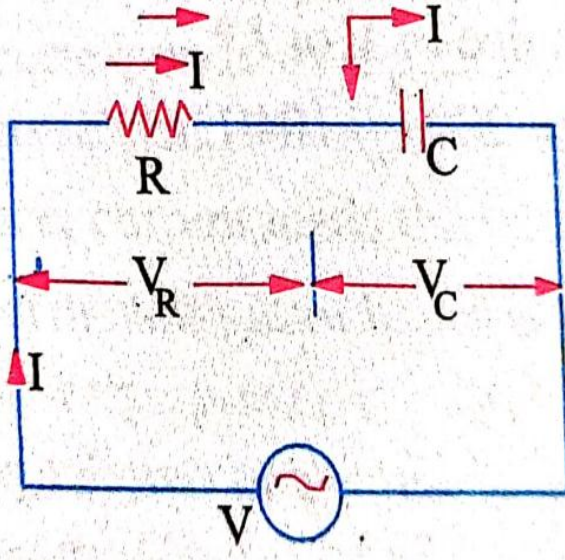

ii) Vector diagram

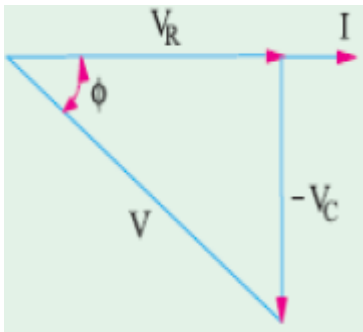

iii) Waveform of voltage and current


WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

7

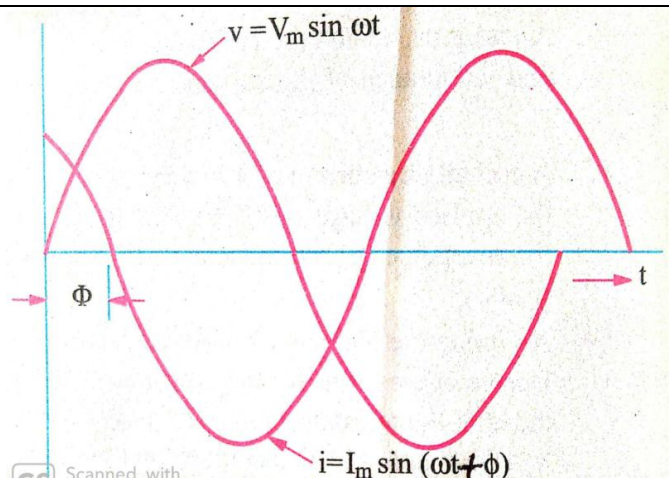

b) Compare series and parallel resonance on the basis of

4M

- (i) Resonating frequency
- (ii) Impedance
- (iii) Current
- (iv) Magnification

Ans:

1M for each point

S. No	Parameter	Series Circuit	Parallel Circuit
1	Resonating frequency	$f_r = \frac{1}{2\pi\sqrt{LC}}$	$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$
2	Impedance	Minimum, $Z = R$	Maximum, $Z = L/CR$
3	Current	Maximum, $I = V/R$	Minimum, $I = V/(L/CR)$
4	Magnification	Voltage magnification takes place	Current magnification takes place

c) Explain the suitable example to convert a practical current source into equivalent voltage source.

4M


WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

Ans:

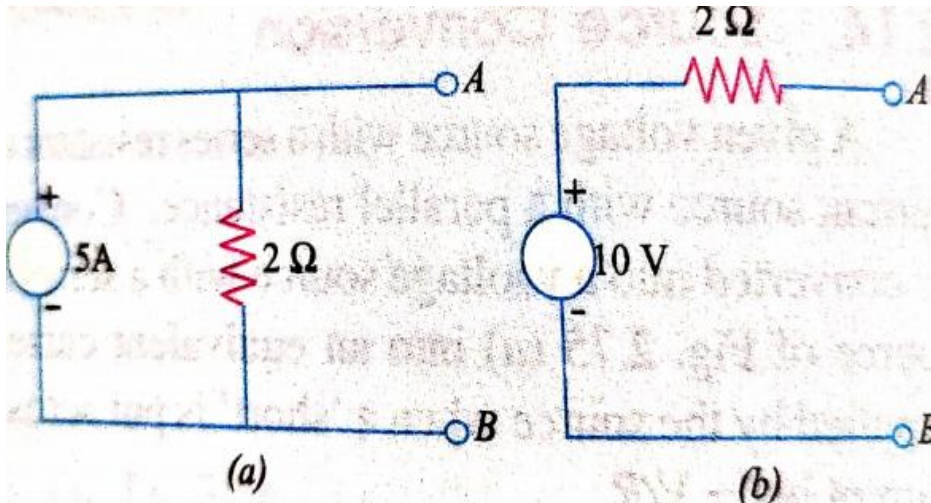

The open-circuit voltage across terminals A and B is

$$V_{oc} = \text{drop across } R \\ = 5 \times 2 = 10V$$

Hence, voltage source has a voltage of 10V and the same resistance of 2Ω

2M-
circuit
diagram,
2M-
conversi
on

d) Write the steps for finding the current through an element by Thevenin's theorem.

4M

Ans: Steps to find Thevenin's equivalent circuit, taking an example is as follows:

1M each
step

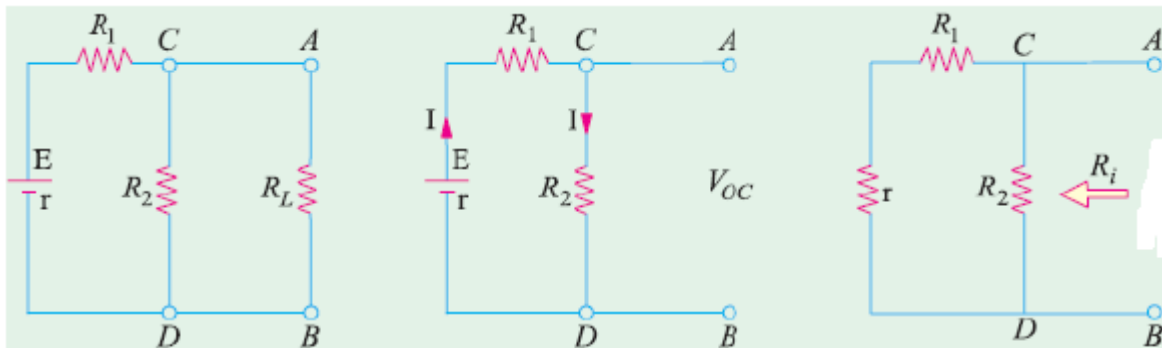


Fig.(a)

fig.(b)

fig.(c)

WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

9

1. From the given circuit (fig.a), Remove R_L from the terminals A and B and redraw the circuit as shown in fig.b.

2. Calculate the open-circuit voltage V_{oc} which appears across terminals A and B. As seen, $V_{oc} = \text{drop across } R_2 = IR_2$ where I is the circuit current when A and B are open.

$$I = \frac{E}{R_1 + R_2 + r} \quad \therefore V_{oc} = IR_2 = \frac{ER_2}{R_1 + R_2 + r} \quad [r \text{ is the internal resistance of battery}]$$

It is also called 'Thevenin voltage' V_{th} .

3. Now, imagine the battery to be removed from the circuit, leaving its internal resistance r behind and redraw the circuit, as shown in Fig.(c). When viewed inwards from terminals A and B, the equivalent resistance is given as,


$$R = R_2 \parallel (R_1 + r) = \frac{R_2(R_1 + r)}{R_2 + (R_1 + r)}$$

This is called Thevenin's equivalent resistance R_{th} .

4. Connect R_L back across terminals A and B (fig.d) from where it was temporarily removed earlier.

Current flowing through R_L is given by

$$I = \frac{V_{th}}{R_{th} + R_L}$$


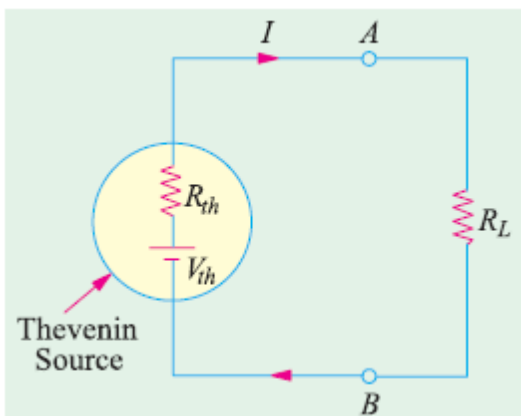


WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

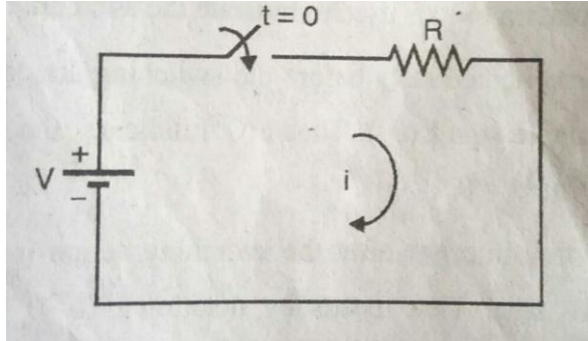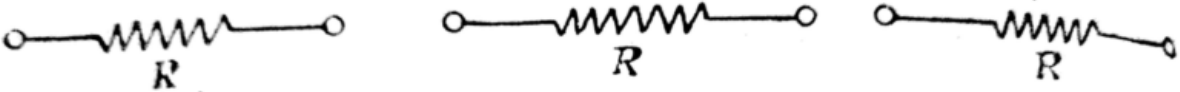
Q. No.	Sub Q. N.	Answers	Marking Scheme
3		Attempt any THREE of the following :	12- Total Marks
	a)	<p>Explain the concept of initial and final conditions in switching circuits for elements R and L.</p> <p>Ans: Concept of Initial and final condition in switching circuits for R: Consider a resistor is connected to a voltage source, using a switch as shown in fig below</p>  <p>The switch is closed at time $t = 0$, so we get $V = iR$ which is time independent equation. Here current changes as per voltage without any time delay. There is no change in the value of resistor R, it remains same for initial condition and final condition.</p>  <p>Initial condition equivalent circuit at $t=0+$ equivalent circuit at $t = \infty$</p>	<p>4M</p> <p>2M for resistance</p> <p>2M for inductance</p>
		<p>Concept of Initial and final condition in switching circuits for L:</p> <p>Consider a inductor is connected to voltage source as shown in fig below:</p>	

WINTER-19 EXAMINATION

Subject Name: Electric circuits and network


Subject Code: 22330

Model Answer

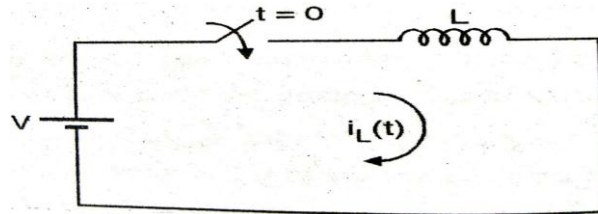


The property of inductor is to oppose any change in current. So the current through an inductor cannot change instantaneously. There are 2 cases.

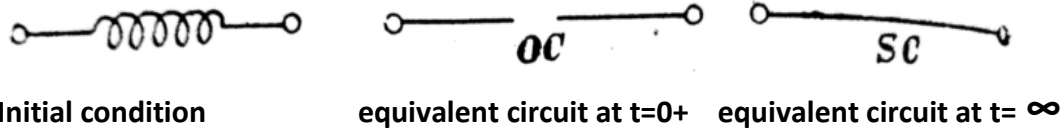- i) If no initial current is passing through inductor, then at $t = 0+$, it acts as open circuit. The final condition is given by the equation $v_L = L di/dt$.
At $t = \infty$, it acts as short circuit.



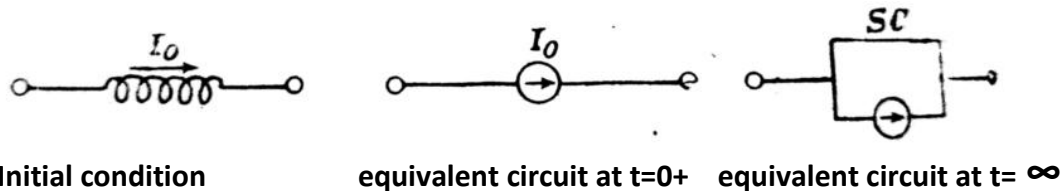- ii) If initial current is passing through inductor, then at $t = 0+$, it acts as constant current source of value I_0 .

At $t = \infty$, (final condition), the inductor acts as current source of value I_0 in parallel with short circuit. (I_0 is the current in inductor just before switching)



b) Derive an expression for resonant frequency of series RLC circuit.

4M



WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

12
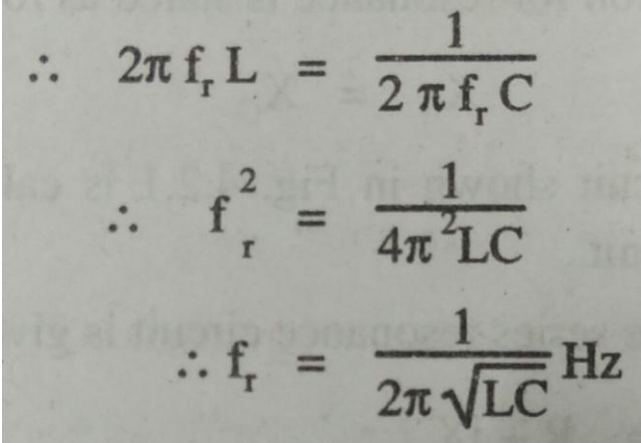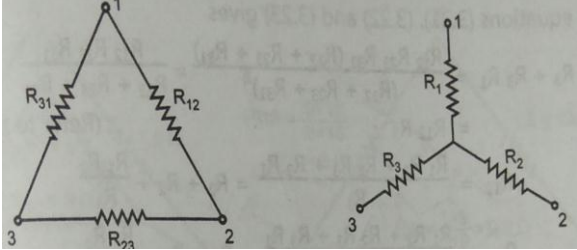
<p>Ans:</p>	<p>At resonance frequency in RLC series circuit, we have inductive reactance is equal to capacitive reactance i.e.</p> $X_L = X_C$ <p>As $X_L = 2\pi f_r L$ and $X_C = 1/2\pi f_r C$, we can write</p>  <p>Where f_r is the resonant frequency in RLC series circuit.</p>	<p>4 M</p>
<p>c)</p>	<p>Derive an expression for delta to star transformation.</p>	<p>4M</p>
<p>Ans:</p>	 <p>Equivalent delta and star network</p> <p>For delta network the resistance between the terminals 1 and 2 consists of R_{12} in parallel with $(R_{23} + R_{31})$. Hence, the resistance between the terminals 1 and 2 is</p>	<p>1M</p>



WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

13

$$= \frac{R_{12} (R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}}$$

In case of star network the resistance between the terminals 1 and 2 is $=R_1+R_2$, so we get

$$R_1 + R_2 = \frac{R_{12} (R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}} \quad \text{---i)}$$

$$R_2 + R_3 = \frac{R_{23} (R_{31} + R_{12})}{R_{12} + R_{23} + R_{31}}$$

$$R_3 + R_1 = \frac{R_{31} (R_{12} + R_{23})}{R_{12} + R_{23} + R_{31}}$$

---ii & iii)

Subtracting equation (ii) from (i), we get

$$R_1 - R_3 = \frac{R_{12} R_{23} + R_{12} R_{31} - R_{23} R_{31} - R_{23} R_{12}}{R_{12} + R_{23} + R_{31}}$$

$$R_1 - R_3 = \frac{R_{12} R_{31} - R_{23} R_{31}}{R_{12} + R_{23} + R_{31}} \quad \text{---iv)}$$

1M

1M




WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

14

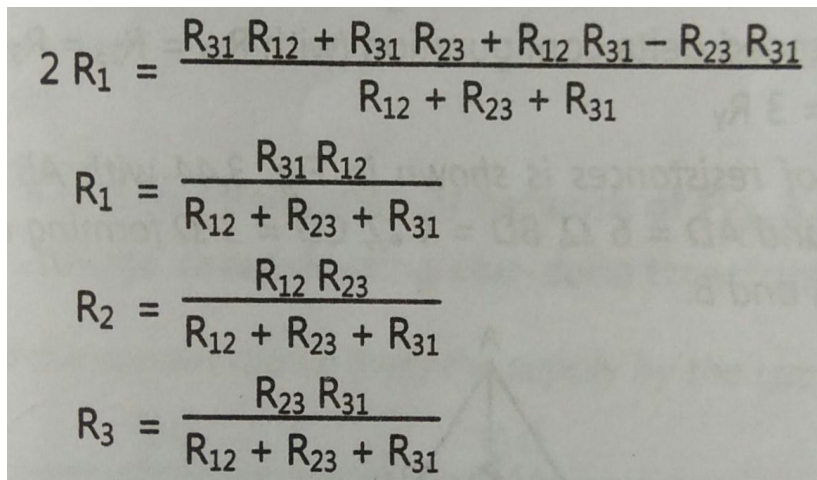	<p>Adding equations (iii) and(iv),we have</p> 	<p>1M</p>
<p>d)</p>	<p>State super position theorem. Write steps to find current in an element using super position theorem.</p>	<p>4M</p>
<p>Ans:</p>	<p>Statement of superposition theorem: In any linear network containing two or more sources, the current in any element is equal to algebraic sum of the current caused by individual source acting alone, while the other sources are replaced for the time being by resistances equal to their internal resistances.</p> <p>Steps to find current using superposition theorem:</p> <ol style="list-style-type: none"> 1. Select any one energy source. 2. Replace all other energy sources i.e. voltage source by short circuit and current source by open circuit. 3. Calculate voltage drop and branch current due to selected energy source. 4. Repeat steps 1,2,3 for each source individually. 5. Add algebraically the voltage drops and branch currents to obtain combined effect of all sources. 	<p>2M – state ment</p> <p>2M for steps</p>



WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code:

22330

Model Answer

15

Q. No.	Sub Q. N.	Answers	Marking Scheme
4		Attempt any THREE of the following :	12- Total Marks
	(a)	A series combination of resistance 100 ohm and capacitance 50 μ f is connected in series to a 230 V, 50HZ supply. Calculate (i) Capacitive reactance (ii) Current (iii) Power factor (iv) Power consumed	4M
	Ans:	Solution: For RC series circuit	1M 1M 1M



WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code:

22330

Model Answer

16

	<p>Given $R=100 \Omega$, $C=50 \mu\text{f}$, $V=230\text{V}$, $f=50\text{Hz}$</p> <p>(i) Capacitive Reactance</p> $X_c = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 50 \times 10^{-6}} = \underline{\underline{63.66 \Omega}}$ <p>(ii) Current</p> $I = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + X_c^2}} = \frac{230}{\sqrt{(100)^2 + (63.66)^2}}$ $= \frac{230}{118.54} = \underline{\underline{1.94 \text{ A}}}$ <p>(iii) Power factor</p> $\cos \phi = \frac{R}{Z} = \frac{100}{118.54} = \underline{\underline{0.8435}} \text{ leading}$ <p>(iv) Power consumed</p> $P = V I \cos \phi = 230 \times 1.94 \times 0.8435$ $= \underline{\underline{376.36 \text{ W}}}$	<p>1M</p>
<p>(b)</p>	<p>Two impedances given by $Z_1 = 10 + j5$ and $Z_2 = 8 + j9$ are joined in parallel and connected across a voltage of $V = 200 + j0$. Calculate the circuit current and branch currents. Draw the vector diagram.</p>	<p>4M</p>
<p>Ans:</p>	<p>Solution:</p> <p>Given, $Z_1=10+j5$, $Z_2=8+j9$, $V=200+j0$</p>	



WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

17

Given: $Z_1 = 10 + j5$, $Z_2 = 8 + j9$ and $v = 200 \angle 0^\circ$

To find circuit current first we have to calculate total admittance

(a) Total admittance

$$\begin{aligned} Y &= Y_1 + Y_2 = \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{(10+j5)} + \frac{1}{(8+j9)} \\ &= \frac{1}{11.18 \angle 26.56^\circ} + \frac{1}{12.04 \angle 48.36^\circ} \\ &= 0.089 \angle -26.56^\circ + 0.083 \angle -48.36^\circ \\ &= (0.08 - 0.04j) + (0.06 - 0.06j) \\ &= 0.14 - 0.1j \\ &= \underline{0.17 \angle -35.53^\circ} \end{aligned}$$

1M

(b) Circuit current, $I = v \times Y$

$$\begin{aligned} &= (200 \angle 0^\circ) (0.17 \angle -35.53^\circ) \\ &= \underline{34 \angle -35.53^\circ} \text{ A} \end{aligned}$$

1M

(c) Branch current

$$\begin{aligned} I_1 &= v \times Y_1 \\ &= (200 \angle 0^\circ) (0.089 \angle -26.56^\circ) \\ &= \underline{17.8 \angle -26.56^\circ} \text{ A} \end{aligned}$$


1M

$$I_2 = v \times Y_2$$

$$\begin{aligned} &= (200 \angle 0^\circ) (0.083 \angle -48.36^\circ) \\ &= \underline{16.6 \angle -48.36^\circ} \text{ A} \end{aligned}$$

1M

(d) Vector Diagram

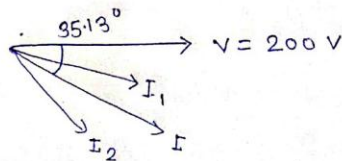

(c) An a.c series circuit has resistance of 10ohm, inductance of 0.1H and capacitance of $10\mu\text{f}$, voltage applied to circuit is 200V. find

4M

- (i) Resonant frequency
- (ii) Current at resonance
- (iii) Power at resonance



WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

18

Ans:	Solution: For RLC series circuit	2M
	Given: $R = 10 \Omega$, $L = 0.1 \text{ H}$, $C = 10 \mu\text{F}$, $V = 200 \text{ V}$	
	(i) Resonant frequency $f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.1 \times 10 \times 10^{-6}}}$ $= 159.13 \text{ Hz}$	1M
	(ii) current at resonance, $I = \frac{V}{Z}$ $= \frac{V}{R} = \frac{200}{10} = 20 \text{ A}$	1M
	(iii) Power at resonance, $P = VI \cos \phi$ $= 200 \times 20 \times 1 = 4000 \text{ W}$ $= 4 \text{ kW}$	
(d)	Use mesh analysis to calculate ammeter current in Fig No. 1	4M


WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

19

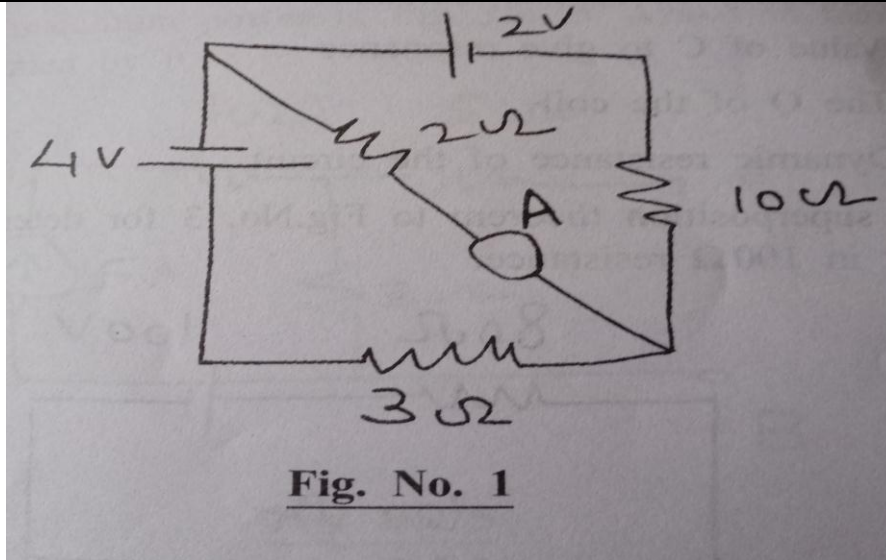

Ans:

(a) Applying mesh analysis to loop ABCA, we have

$$-2 - 10 I_1 - 2 (I_1 - I_2) = 0$$

$$\therefore -2 - 12 I_1 + 2 I_2 = 0$$

$$\therefore -6 I_1 + I_2 = 1 \quad \text{--- (i)}$$

1M

(b) Applying mesh analysis to loop ACDB, we have

$$-2 (I_2 - I_1) - 3 I_2 - 4 = 0$$

$$\therefore -5 I_2 + 2 I_1 - 4 = 0$$

$$\therefore 2 I_1 - 5 I_2 = 4 \quad \text{--- (ii)}$$

1M

Multiplying eqⁿ (ii) by 3 we get,

$$6 I_1 - 15 I_2 = 12 \quad \text{--- (iii)}$$

1/2M

Adding eqⁿ (i) + (iii) we get

$$-14 I_2 = 13$$

$$\therefore I_2 = -13/14 = -0.92 \text{ A}$$

1/2M

From eqⁿ (i) $-6 I_1 + (-0.92) = 1$

$$\therefore -6 I_1 = 1.92$$

$$\therefore I_1 = -0.32 \text{ A}$$

$$\therefore \text{Current in ammeter is } I_1 - I_2 = -0.32 - (-0.92)$$

$$= -0.32 + 0.92$$

$$= \underline{0.6 \text{ A (cta A)}}$$

1M

WINTER-19 EXAMINATION


Subject Name: Electric circuits and network

Subject Code:

22330

Model Answer

20
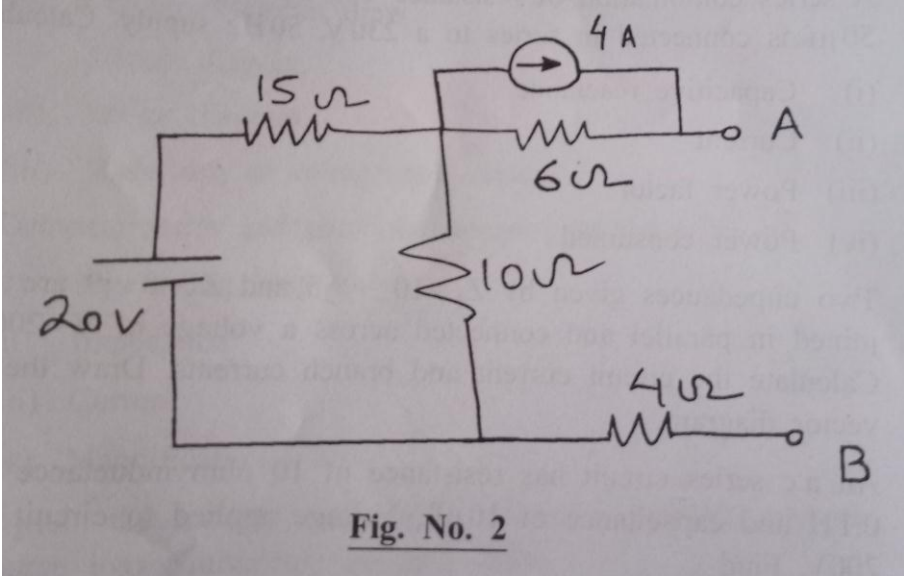
<p>(e)</p>	<p>Find the Norton equivalent resistance for the network shown in Fig No. 2</p>  <p style="text-align: center;"><u>Fig. No. 2</u></p>	<p>4M</p>
<p>Ans:</p>	<p>Solution: To find Norton's equivalent resistance removing voltage source and current source. Voltage source is replaced by short circuit and current source is replaced by open circuit so, we get circuit as</p>	<p>Diagram :1M R_N calculation :3M</p>



WINTER-19 EXAMINATION


Subject Name: Electric circuits and network

Subject Code:

22330

Model Answer

21

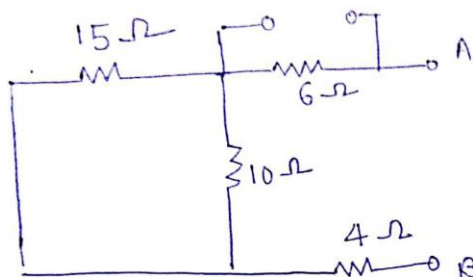

Tracing circuit from A & B, we have 15Ω & 10Ω resistor in parallel.

$$\therefore \text{Its equivalent resistance } R_{eq} = \frac{15 \times 10}{15 + 10} = 6\Omega$$

Now 6Ω , 6Ω & 4Ω resistor are in series,

$$\therefore \text{we have } R_s = 6 + 6 + 4 = 16\Omega$$

$$\therefore \text{Norton's equivalent resistance } \underline{R_N = 16\Omega}$$

Q. No.	Sub Q. N.	Answers	Marking Scheme
5.		Attempt any TWO of the following:	12- Total Marks
	a)	<p>A coil of resistance 20 ohm and inductance of $200\mu\text{H}$ is in parallel with variable capacitor. This combination is in series with a resistance of 8000 ohm. The voltage of the supply is 200 V and at frequency of 10^6 Hz. Calculate</p> <p>(i) Value of C to give resonance (ii) The Q of the coil (iii) Dynamic resistance of the circuit.</p>	6M



WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

22

Ans:

Ans :→

$$\begin{aligned} \textcircled{1} \text{ Inductive Reactance } X_L &= 2\pi fL \\ &= 2 \times \pi \times 10^6 \times 200 \times 10^{-6} \\ &= 1256 \Omega \end{aligned}$$

$$\begin{aligned} \textcircled{2} \text{ Impedance } Z &= \sqrt{R^2 + X_L^2} \\ &= \sqrt{20^2 + (1256)^2} \\ Z &= 1256.16 \Omega \end{aligned}$$

$$\begin{aligned} \textcircled{3} \quad Z_L^2 &= L/C \quad \text{at parallel Resonance} \\ \text{Value of } C \text{ at Resonance} \rightarrow C &= \frac{L}{Z_L^2} = \frac{200 \times 10^{-6}}{(1256.16)^2} = 125.5 \times 10^{-12} \text{ F} \\ &= 125.5 \text{ pF} \end{aligned}$$

$$\begin{aligned} \textcircled{4} \text{ Q of coil} &= \frac{2\pi f r L}{R} \\ &= \frac{2\pi \times 10^6 \times 200 \times 10^{-6}}{20} = 62.8 \end{aligned}$$

⑤ Dynamic Resistance of coil circuit

$$\begin{aligned} Z_r &= \frac{L}{CR} \\ Z_r &= \frac{200 \times 10^{-6}}{125.6 \times 10^{-12} \times 20} = 78957 \Omega \end{aligned}$$

i) Value of C -2 Marks,

ii) Q of coil -2 Marks

iii) Dynamic Resistance -2 Marks



WINTER-19 EXAMINATION


Subject Name: Electric circuits and network

Subject Code:

22330

Model Answer

23

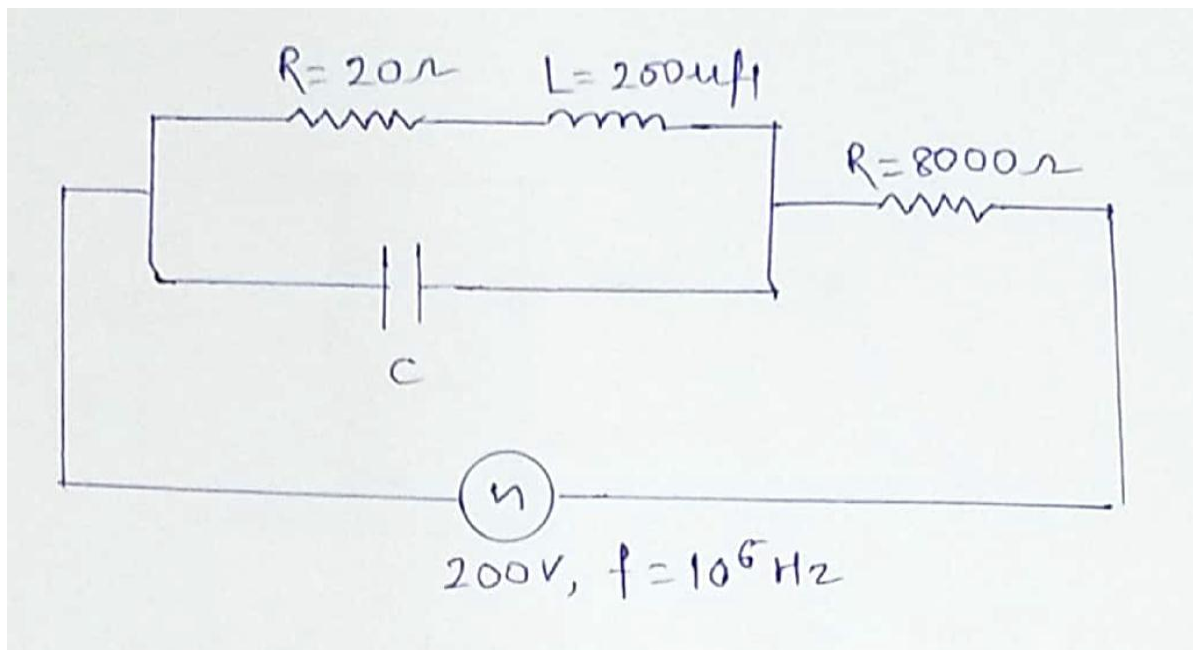

b) Apply superposition theorem to Fig No. 3 for determining the current in 100 Ω resistance.

6M

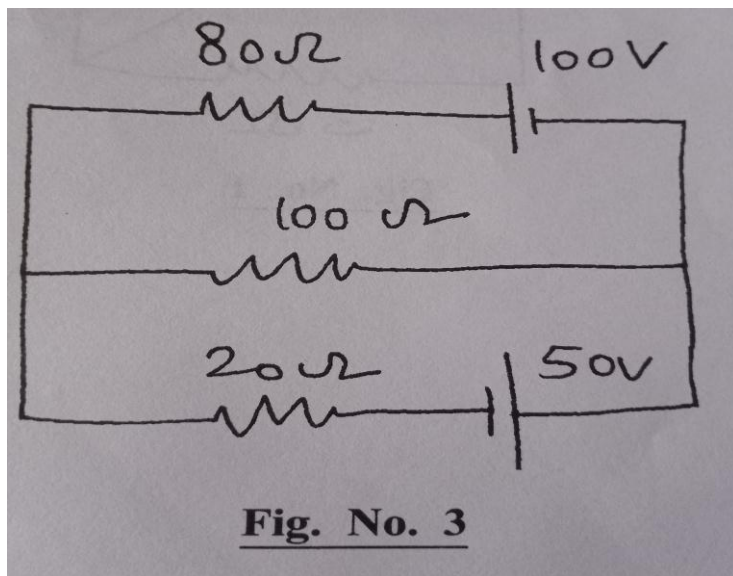


Fig. No. 3

WINTER-19 EXAMINATION


Subject Name: Electric circuits and network

Subject Code: 22330


Model Answer

Ans:

Ans :-

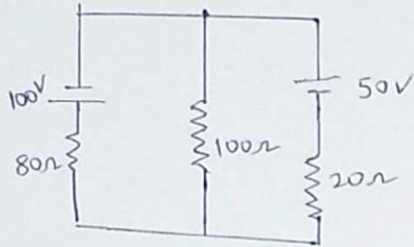

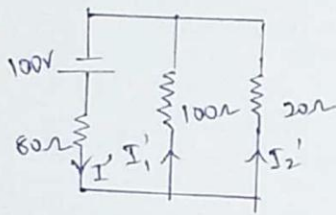step 1:- consider only 100V source & short 50V supply



Total Resistance across supply


$$= 80 + \frac{100 \times 20}{100 + 20} = 96.66$$

$$I' = \frac{100}{96.66} = 1.034$$

current in $\frac{100\Omega}{20\Omega}$ resistor = $\frac{20}{120} \times 1.034 = 0.172$

$$I_1' = 0.172A$$

Step 2:- consider only 50V source

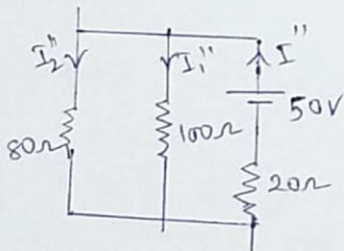

Total Resistance across supply

$$= 20 + \frac{80 \times 100}{80 + 100} = 64.44$$

$$I'' = \frac{50}{64.44} = 0.7759$$

current in 100Ω resistor = $\frac{80}{180} \times 0.7759 = 0.3448$

$$I_1'' = 0.3448$$

Therefore current 100Ω resistor

$$I_1 = I_1'' - I_1' = 0.3448 - 0.172 = 0.1728A$$

Step 1 -
2.5
Marks

Step 2 -
2.5 Marks
Final
current 1
Mark



WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code:

22330

Model Answer
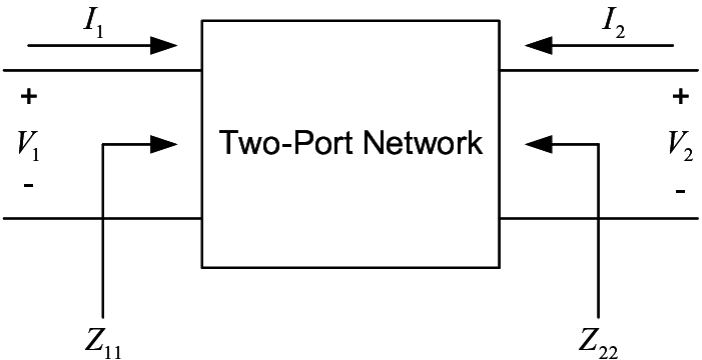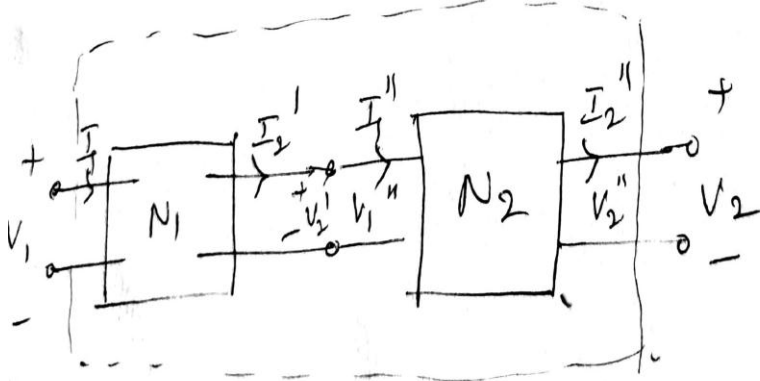
<p>c)</p>	<p>Draw the two port network and determine the indicated parameters for the following configuration</p> <p>(i) Cascade configuration (ABCD parameter) (ii) Series configuration (iii) Parallel configuration</p>	<p>6M</p>
<p>Ans:</p>	 <p>i) Cascade Configuration</p>  <p>2 Nws. N_1 and N_2 connected in <u>cascade</u></p>	<p>Each configuration : 1M</p> <p>Equation for parameter : 1M</p>

WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330


Model Answer

A, B, C, D are the parameters of cascade network, then

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix}$$

for cascade configuration, ABCD parameters has to be multiplied.

ii) Series Configuration

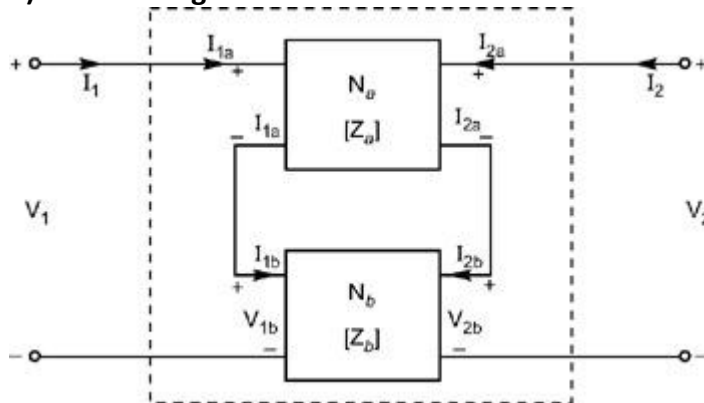

ii) Series configuration (Refer diagram for the same)

$$Z_{11} = Z_{11a} + Z_{11b}$$

$$Z_{12} = Z_{12a} + Z_{12b}$$

$$Z_{21} = Z_{21a} + Z_{21b}$$

$$Z_{22} = Z_{22a} + Z_{22b}$$

$$[Z] = [Z_a] + [Z_b]$$

iii) Parallel Configuration


WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

27

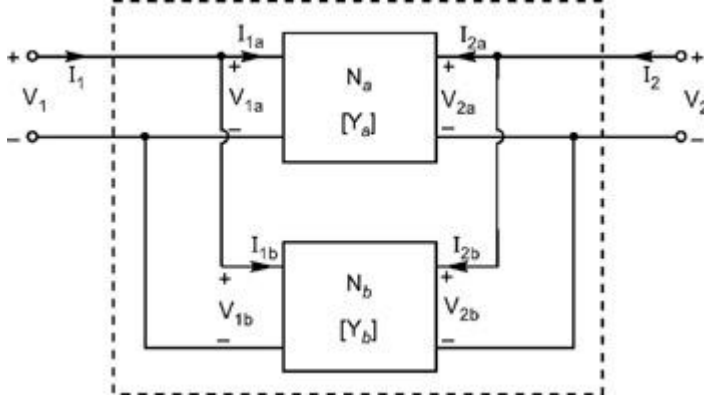

iii) Parallel configuration
(Refer diagram for the same)

$$I_1 = (Y_{11a} + Y_{11b})V_1 + (Y_{12a} + Y_{12b})V_2$$

$$I_2 = (Y_{21a} + Y_{21b})V_1 + (Y_{22a} + Y_{22b})V_2$$

that is Y parameters for combined network can be written as

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

where $Y_{11} = Y_{11a} + Y_{11b}$

$$Y_{12} = Y_{12a} + Y_{12b}$$

$$Y_{21} = Y_{21a} + Y_{21b}$$

$$Y_{22} = Y_{22a} + Y_{22b}$$

Q. No.	Sub Q. N.	Answers	Marking Scheme
6.		Attempt any TWO of the following :	12- Total

WINTER-19 EXAMINATION


Subject Name: Electric circuits and network

Subject Code:

22330

Model Answer

28

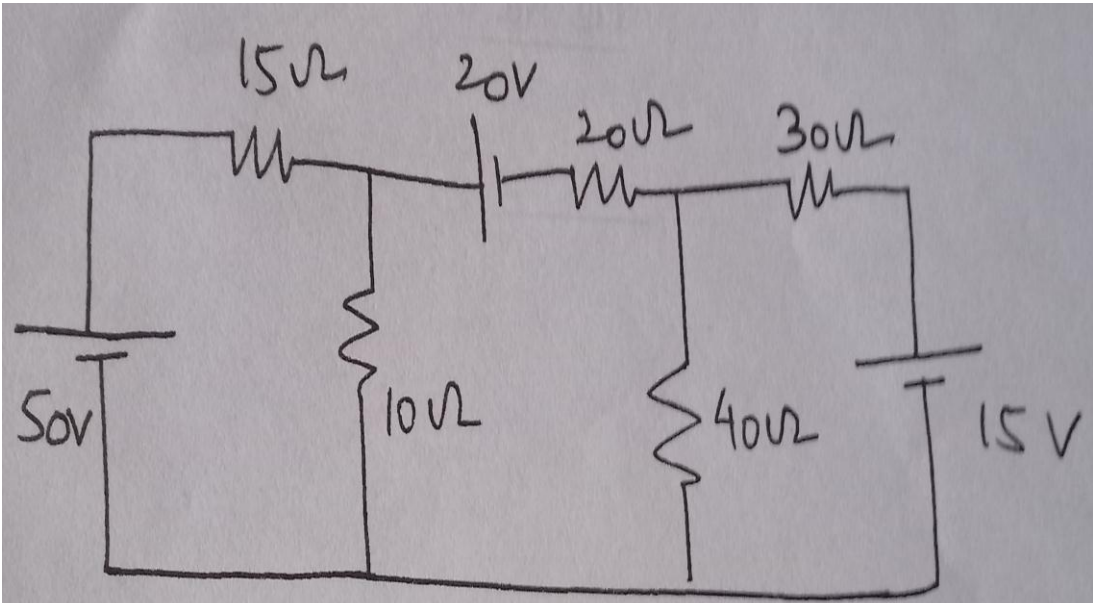		Marks
a)	<p>Find current in $40\ \Omega$ and $10\ \Omega$ in Fig no. 4 node voltage analysis method.</p>  <p><u>Fig. No. 4</u></p>	6M

WINTER-19 EXAMINATION

Subject Name: Electric circuits and network


Subject Code:

22330

Model Answer

29

Ans:

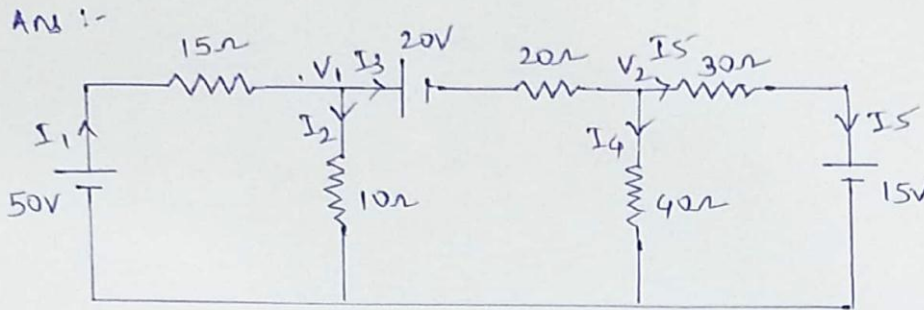

Applying KCL at nodes V_1 & V_2 ,

$$I_1 = I_2 + I_3 \quad \rightarrow \textcircled{1}$$

$$I_3 = I_4 + I_5 \quad \rightarrow \textcircled{2}$$

for first equation

$$I_1 = I_2 + I_3$$

$$\left(\frac{50 - V_1}{15} \right) = \frac{V_1}{10} + \left(\frac{V_1 - 20 - V_2}{20} \right)$$

$$\left(\frac{50 - V_1}{15} \right) = \frac{2V_1 + V_1 - 20 - V_2}{20}$$

$$\frac{50 - V_1}{15} = \frac{3V_1 - 20 - V_2}{20}$$

$$20(50 - V_1) = 15(3V_1 - 20 - V_2)$$

$$1000 - 20V_1 = 45V_1 - 300 - 15V_2$$

$$1300 = 65V_1 - 15V_2 \quad \rightarrow \textcircled{3}$$

for second equation

$$I_3 = I_4 + I_5$$

$$\left(\frac{V_1 - 20 - V_2}{20} \right) = \frac{V_2}{40} + \left(\frac{V_2 - 15}{30} \right)$$

V1 - 2
marks, V2
- 2 Marks,

I through
40 ohms -
1 Mark,

I through
30 ohm -
1 Mark



WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

30

$$\frac{V_1 - V_2 - 20}{20} - \frac{V_2}{40} - \frac{V_2 - 15}{30} = 0$$

$$\frac{6V_1 - 6V_2 - 120 - 3V_2 - 4V_2 + 60}{120} = 0$$

$$6V_1 - 13V_2 - 60 = 0$$

$$6V_1 - 13V_2 = 60 \rightarrow \textcircled{4}$$

By solving $\textcircled{3}$ & $\textcircled{4}$ we get
Multiplying $\textcircled{3}$ by 13 & $\textcircled{4}$ by 15, we get

$$V_1 = 21.19$$

$$V_2 = 5.17$$

$$I_4 = \frac{V_2}{40} = \frac{5.17}{40} = 0.13 \text{ A}$$

$$I_5 = \frac{V_2 - 15}{30} = \frac{5.17 - 15}{30} = -0.327 \text{ A}$$

b) Find the value of resistance to be connected across AB so as to consume maximum power in Fig No. 5. Also find maximum power consumed by it.

6M



WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code:

22330

Model Answer

31

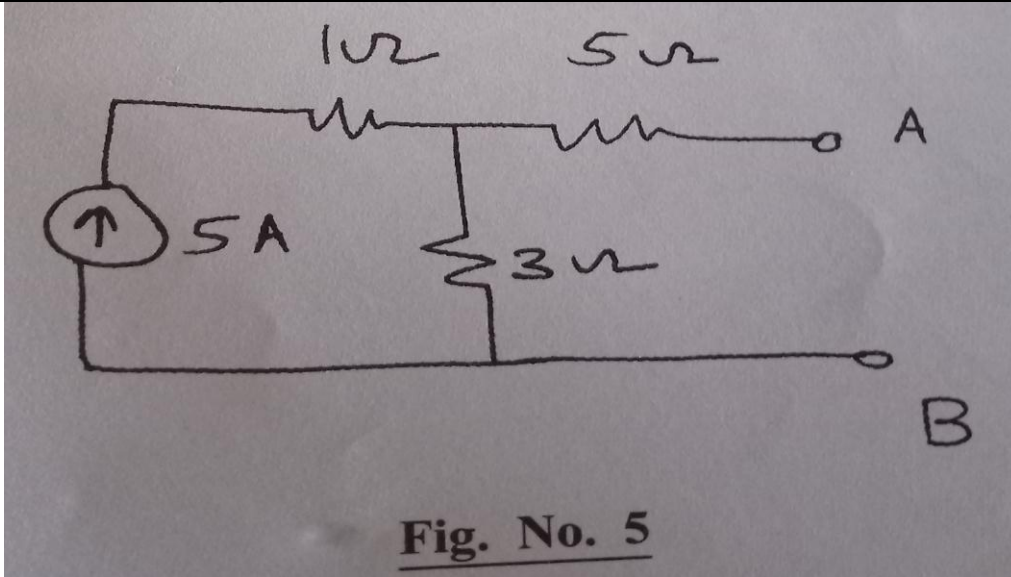


Fig. No. 5

WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330


Model Answer

32

Ans:

Ans :-
Maximum Power will be transferred when $R_{TH} = R_L$, so find out R_{TH} first.


① To find R_{TH} , open SA source

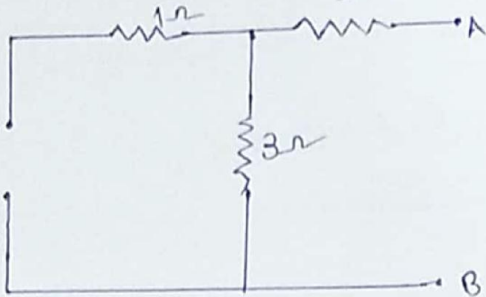

$R_{TH} = 3 + 5 = 8\Omega$

$R_L = 8\Omega = R_{TH}$ to transfer maximum power.

② To find V_{oc} .

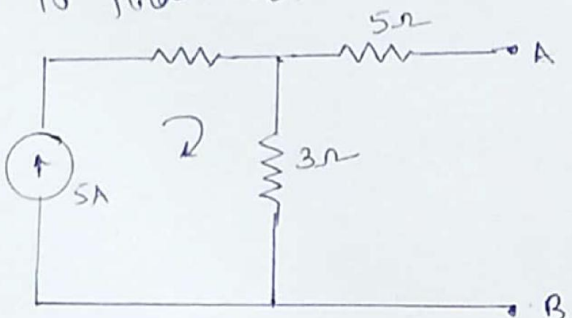

current through $3\Omega = 5 \times 3 = 15$

$\therefore V_{oc} = 5 \times 3 = 15$

Maximum Power = $\frac{V_{oc}^2}{4R_L} = \frac{15^2}{4 \times 8} = 7.03125 \text{ W}$.

Rth -2
Marks,

Voc -
2Marks,

Power -
2Marks

c) Find Z parameters for the network shown in Fig No. 6

6M



WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code:

22330

Model Answer

33

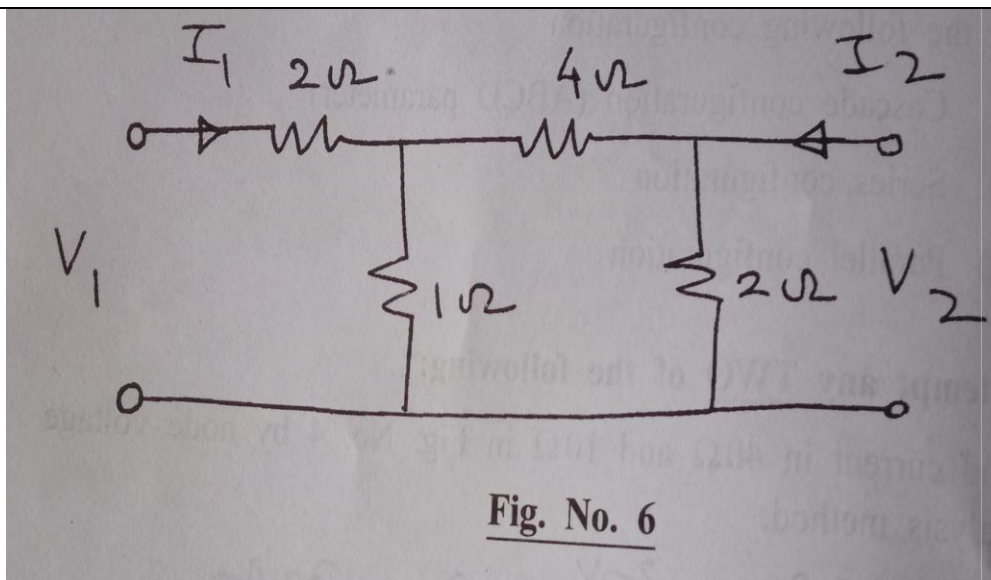


Fig. No. 6

Ans:

Z11-2
Marks,
Z12-
1Mark,
Z21 -
2Marks,
Z22-
1Mark


WINTER-19 EXAMINATION

Subject Name: Electric circuits and network


Subject Code: 22330

Model Answer

Ans :-

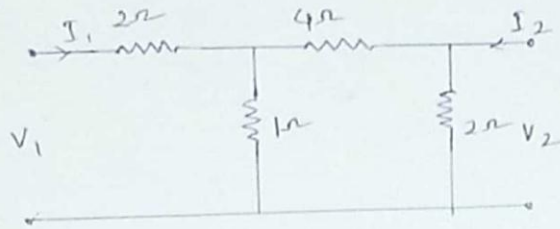

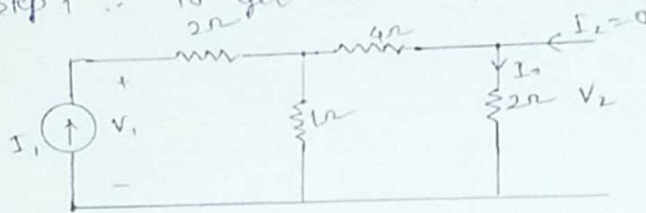Step 1 :- To get Z_{11} & Z_{21} , consider the circuit as




$$Z_{11} = \frac{V_1}{I_1} = 2 + j11(4+2)$$

$$= 2 + \frac{1 \times 6}{1+6} = 2 + \frac{6}{7} = 2.85$$

$$I_0 = \frac{1}{2} I_1$$

$$Z_{21} = \frac{V_2}{I_1} = \frac{2 \left(\frac{1}{2} I_1 \right)}{I_1} = \frac{2}{7} \Omega = 0.28$$

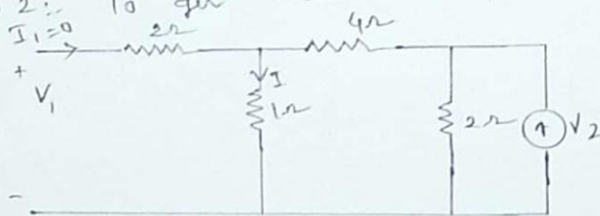Step 2 :- To get Z_{22} & Z_{12} , consider the circuit as



$$Z_{22} = \frac{V_2}{I_2} = 2 \parallel (4+1) = \frac{2 \times 5}{2+5} = \frac{10}{7} = 1.44$$

$$I = \frac{2}{2+5} \times I_2 = \frac{2}{7} I_2 \quad V_1 = 1 \times I = 1 \times \frac{2}{7} I_2 = \frac{2}{7} I_2$$

$$Z_{12} = \frac{V_1}{I_2} = \frac{2}{7} I_2 \times \frac{1}{I_2} = \frac{2}{7} = 0.28$$



WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

35

$$Z = \begin{bmatrix} 2.85 & 0.28 \\ 0.28 & 1.44 \end{bmatrix} \Omega$$