



Summer- 2018 Examinations





Subject Code: 22213

Model Answer

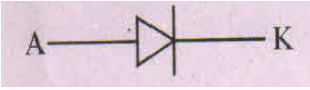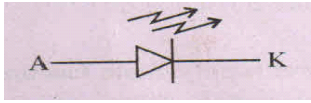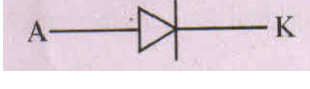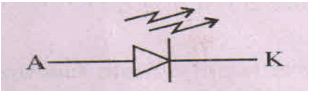
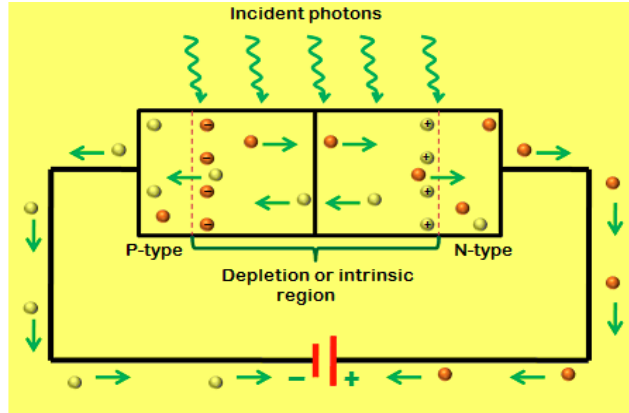
Page 1 of 13

**Important suggestions to examiners:**



- 1) The answers should be examined by key words and not as word-to-word as given in the model answer scheme.
- 2) The model answer and the answer written by candidate may vary but the examiner may try to assess the understanding level of the candidate.
- 3) The language errors such as grammatical, spelling errors should not be given more importance. (Not applicable for subject English and communication skills)
- 4) While assessing figures, examiner may give credit for principle components indicated in a figure. The figures drawn by candidate and model answer may vary. The examiner may give credit for any equivalent figure drawn.
- 5) Credits may be given step wise for numerical problems. In some cases, the assumed constant values may vary and there may be some difference in the candidate's answers and model answer.
- 6) In case some questions credit may be given by judgment on part of examiner of relevant answer based on candidate understands.
- 7) For programming language papers, credit may be given to any other program based on equivalent concept.

| Q.1 | Attempt any FIVE of the following :                                                                                                                                                                                                                           | 10 Marks                                                                                  |
|-----|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-------------------------------------------------------------------------------------------|
| a)  | Name the components of following symbols :                                                                                                                                                                                                                    |                                                                                           |
| (i) |                                                                                                                                                                            | (ii)  |
| Ans | (i)  : Semiconductor Diode                                                                                                                                                 | (1 Mark)                                                                                  |
|     | (ii)  : Light Emitting Diode                                                                                                                                               | (1 Mark)                                                                                  |
| b)  | Define the term 'Ripple factor' for rectifier.                                                                                                                                                                                                                |                                                                                           |
| Ans | <b>Ripple factor:</b> The ratio of RMS value of ac component present in the waveform to the dc component in the waveform is called as ripple factor.<br>OR<br>The unwanted AC components present in output waveform of a rectifier is called as ripple factor | (2 Marks)                                                                                 |
| c)  | State relation between emitter current ( $I_E$ ), Base current ( $I_B$ ) and collector current ( $I_C$ ) of BJT.                                                                                                                                              |                                                                                           |
| Ans | $I_E = I_C + I_B$ $I_E = (1+\beta) I_B$                                                                                                                                                                                                                       | (2 Marks)                                                                                 |
| d)  | Write three terminal voltage regulator IC for obtaining : (i) +5V (ii) -12V                                                                                                                                                                                   |                                                                                           |
| Ans | (i) Terminal voltage regulator IC for obtaining : +5V : IC 7805<br>(ii) Terminal voltage regulator IC for obtaining : -12V : IC 7912                                                                                                                          | (1 Mark)<br>(1 Mark)                                                                      |




| e)                                                                                                                                                                                                                                                                                                                   | <b>'Germanium diode knee voltage is lower than silicon diode knee voltage.' Justify.</b>                                                                                                                                                                            |                 |   |   |        |   |   |   |   |   |   |   |   |   |   |   |   |
|----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----------------|---|---|--------|---|---|---|---|---|---|---|---|---|---|---|---|
| Ans                                                                                                                                                                                                                                                                                                                  | <b>Justification:</b> <span style="float: right;"><b>(2 Marks)</b></span><br>The band gap between conduction and valence band for Germanium (0.66eV) is less as compared to Silicon (1.11eV). Hence less energy is required to start conduction in Germanium diode. |                 |   |   |        |   |   |   |   |   |   |   |   |   |   |   |   |
| f)                                                                                                                                                                                                                                                                                                                   | <b>Define the term 'Load Regulation'.</b>                                                                                                                                                                                                                           |                 |   |   |        |   |   |   |   |   |   |   |   |   |   |   |   |
| Ans                                                                                                                                                                                                                                                                                                                  | <b>Load Regulation :</b> <span style="float: right;"><b>(2 Marks)</b></span><br>Load regulation is the ability of a power supply to maintain a constant output voltage irrespective of any changes in load current.                                                 |                 |   |   |        |   |   |   |   |   |   |   |   |   |   |   |   |
| $\text{Load regulation} = \left( \frac{V_{NL} - V_{FL}}{V_{FL}} \right) \times 100\%$                                                                                                                                                                                                                                |                                                                                                                                                                                                                                                                     |                 |   |   |        |   |   |   |   |   |   |   |   |   |   |   |   |
| g)                                                                                                                                                                                                                                                                                                                   | <b>Draw symbol and write truth table of EX-OR gate.</b>                                                                                                                                                                                                             |                 |   |   |        |   |   |   |   |   |   |   |   |   |   |   |   |
| Ans                                                                                                                                                                                                                                                                                                                  | <b>Symbol and truth table of EX-OR :</b> <span style="float: right;"><b>(1 Mark for symbol &amp; 1 Mark for Truth table)</b></span><br><i>Exclusive-OR gate</i>                                                                                                     |                 |   |   |        |   |   |   |   |   |   |   |   |   |   |   |   |
|                                                                                                                                                                                                                                  |                                                                                                                                                                                                                                                                     |                 |   |   |        |   |   |   |   |   |   |   |   |   |   |   |   |
| <table border="1" style="margin: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table> |                                                                                                                                                                                                                                                                     |                 | A | B | Output | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 0 |
| A                                                                                                                                                                                                                                                                                                                    | B                                                                                                                                                                                                                                                                   | Output          |   |   |        |   |   |   |   |   |   |   |   |   |   |   |   |
| 0                                                                                                                                                                                                                                                                                                                    | 0                                                                                                                                                                                                                                                                   | 0               |   |   |        |   |   |   |   |   |   |   |   |   |   |   |   |
| 0                                                                                                                                                                                                                                                                                                                    | 1                                                                                                                                                                                                                                                                   | 1               |   |   |        |   |   |   |   |   |   |   |   |   |   |   |   |
| 1                                                                                                                                                                                                                                                                                                                    | 0                                                                                                                                                                                                                                                                   | 1               |   |   |        |   |   |   |   |   |   |   |   |   |   |   |   |
| 1                                                                                                                                                                                                                                                                                                                    | 1                                                                                                                                                                                                                                                                   | 0               |   |   |        |   |   |   |   |   |   |   |   |   |   |   |   |
| <b>Q.2</b>                                                                                                                                                                                                                                                                                                           | <b>Attempt any THREE of the following :</b>                                                                                                                                                                                                                         | <b>12 Marks</b> |   |   |        |   |   |   |   |   |   |   |   |   |   |   |   |
| a)                                                                                                                                                                                                                                                                                                                   | <b>State working principle of photo diode. List out its three applications.</b>                                                                                                                                                                                     |                 |   |   |        |   |   |   |   |   |   |   |   |   |   |   |   |
| Ans:                                                                                                                                                                                                                                                                                                                 | <b>Diagram of photo diode :</b> <span style="float: right;"><b>(1 Mark)</b></span>                                                                                                                                                                                  |                 |   |   |        |   |   |   |   |   |   |   |   |   |   |   |   |
|                                                                                                                                                                                                                                  |                                                                                                                                                                                                                                                                     |                 |   |   |        |   |   |   |   |   |   |   |   |   |   |   |   |

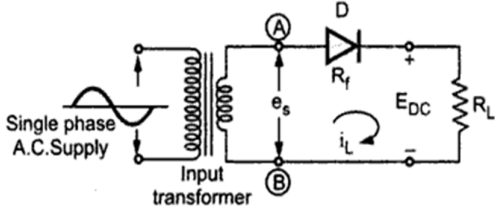
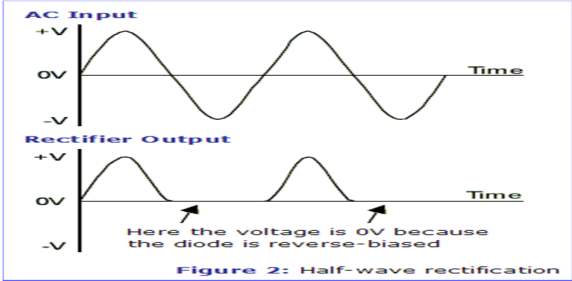


|      |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                              |
|------|----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
|      | <p><b>Working principle of photo diode :</b> <span style="float: right;"><b>(2 Marks)</b></span></p> <p>When photons of energy greater than 1.1 eV hit the diode, electron-hole pairs are created. The intensity of photon absorption depends on the energy of photons – the lower the energy of photons, the deeper the absorption is. This process is known as the inner photoelectric effect.</p> <p>If the absorption occurs in the depletion region of the p-n junction, these hole pairs are swept from the junction - due to the built-in electric field of the depletion region. As a result, the holes move toward the anode and the electrons move toward the cathode, thereby producing photocurrent.</p> <p><b>Applications principle of photo diode :</b> <span style="float: right;"><b>(1 Mark)</b></span></p> <p>Cameras, Medical devices, Smoke detector, Optical communication devices, Position sensors, Bar code scanners, Automotive devices, Surveying instruments</p> |
| b)   | <p><b>Sketch circuit diagram and input, output waveform of Half wave rectifier. State its efficiency.</b></p>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                |
| Ans: | <p><b>Half wave Rectifier (Circuit) :-</b> <span style="float: right;"><b>(Circuit - 2 Mark)</b></span></p> <div style="text-align: center;"></div> <p><b>Waveform:</b> <span style="float: right;"><b>(Waveform - 1 Mark)</b></span></p> <div style="text-align: center;"></div> <p><b>Efficiency : 40.6 %</b> <span style="float: right;"><b>(1 Mark)</b></span></p>                                                                                                                                                                                                                                                                                                                                                                                                                                               |

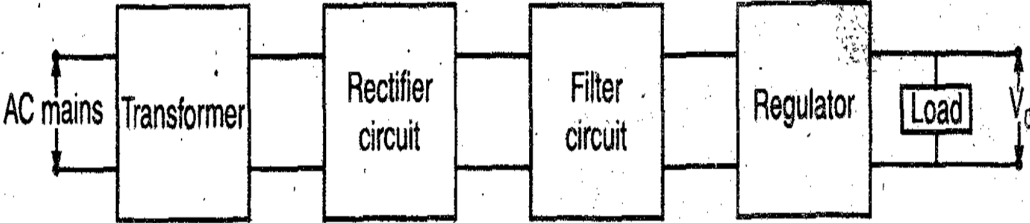

| c)               | <b>Compare BJT common base configuration with common collector configuration on the basis of (i) Current gain (ii) Voltage gain (iii) Input impedance (iv) Output impedance</b>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                           |                    |             |                  |              |               |                    |              |      |   |                 |     |      |                  |      |     |
|------------------|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|--------------------|-------------|------------------|--------------|---------------|--------------------|--------------|------|---|-----------------|-----|------|------------------|------|-----|
| Ans:             | <p><b>Comparison :</b> <span style="float: right;"><b>( 4 Marks)</b></span></p> <table border="1" data-bbox="326 495 1446 758"><thead><tr><th>Parameter</th><th>Common Base</th><th>Common Collector</th></tr></thead><tbody><tr><td>Current gain</td><td>Low (About 1)</td><td>High (<math>1+\beta</math>)</td></tr><tr><td>Voltage gain</td><td>High</td><td>1</td></tr><tr><td>Input impedance</td><td>Low</td><td>High</td></tr><tr><td>Output impedance</td><td>High</td><td>Low</td></tr></tbody></table>                                                                                                                                                                                                                                                                                                                                                                                           | Parameter          | Common Base | Common Collector | Current gain | Low (About 1) | High ( $1+\beta$ ) | Voltage gain | High | 1 | Input impedance | Low | High | Output impedance | High | Low |
| Parameter        | Common Base                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                               | Common Collector   |             |                  |              |               |                    |              |      |   |                 |     |      |                  |      |     |
| Current gain     | Low (About 1)                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                             | High ( $1+\beta$ ) |             |                  |              |               |                    |              |      |   |                 |     |      |                  |      |     |
| Voltage gain     | High                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                      | 1                  |             |                  |              |               |                    |              |      |   |                 |     |      |                  |      |     |
| Input impedance  | Low                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                       | High               |             |                  |              |               |                    |              |      |   |                 |     |      |                  |      |     |
| Output impedance | High                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                      | Low                |             |                  |              |               |                    |              |      |   |                 |     |      |                  |      |     |
| d)               | <b>Sketch block diagram of D.C. regulated power supply. State functions of each block.</b>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                |                    |             |                  |              |               |                    |              |      |   |                 |     |      |                  |      |     |
| Ans:             | <p><b>Diagram :</b> <span style="float: right;"><b>( 2 Mark)</b></span></p>  <p><b>Functions of each block:</b> <span style="float: right;"><b>( 2 Mark)</b></span></p> <ol style="list-style-type: none"><li><b>1) Transformer:</b><br/>It Converts an AC input source to AC required output without changing frequency. The transformer is step up or step down transformer.</li><li><b>2) Rectifier:</b><br/>It is a circuit which is used to convert AC into pulsating DC. A rectifying diode is used.</li><li><b>3) Filter:</b><br/>It is a circuit used to convert pulsating DC into pure DC. A inductor and capacitors are used as filter</li><li><b>4) Voltage regulator:</b><br/>An unregulated DC voltage is converted into regulated DC voltage. IC 78XX &amp; 79XX series are used as regulator.</li></ol> |                    |             |                  |              |               |                    |              |      |   |                 |     |      |                  |      |     |

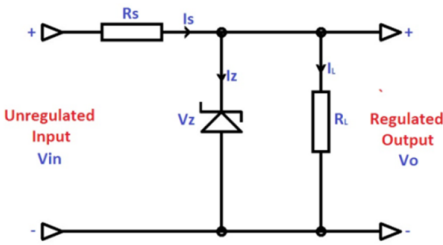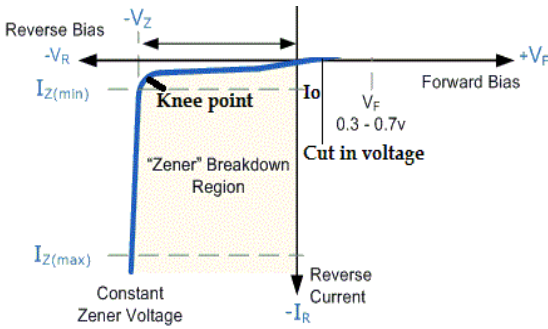

|            |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                |                 |
|------------|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----------------|
| <b>Q.3</b> | <b>Attempt any THREE of the following :</b>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                    | <b>12 Marks</b> |
| a)         | <b>Explain with circuit diagram operation of zener diode as a voltage regulator.</b>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                           |                 |
| Ans:       | <p><b>Diagram of zener diode as voltage regulator:</b> <span style="float: right;"><b>(2 Mark)</b></span></p>  <p><b>Working:</b> <span style="float: right;"><b>(2 Mark)</b></span></p> <p>Zener Diodes are widely used as Shunt Voltage Regulators to regulate voltage across small loads. Zener Diodes have a sharp reverse breakdown voltage and breakdown voltage will be constant for a wide range of currents. Thus we will connect the zener diode parallel to the load such that the applied voltage will reverse bias it. Thus if the reverse bias voltage across the zener diode exceeds the knee voltage, the voltage across the load will be constant.</p> <p><b>Characteristics :</b></p>  |                 |
| b)         | <b>State type of feedback used for oscillator circuit. Explain Barkhausen criteria.</b>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                        |                 |
| Ans:       | <p><b>Type of feedback used for oscillator circuit :</b> Positive feedback <span style="float: right;"><b>(1 Mark)</b></span></p> <p><b>Barkhausen's criterion is a necessary condition for oscillation:</b> <span style="float: right;"><b>(3 Marks)</b></span></p> <p>It states that if <math>A</math> is the gain of the amplifying element in the circuit and <math>\beta(j\omega)</math> is the transfer function of the feedback path, so <math>\beta A</math> is the loop gain around the feedback loop of the circuit, the circuit will sustain steady-state oscillations only at frequencies for which:</p> <ol style="list-style-type: none"><li>1. The loop gain is equal to unity in absolute magnitude, that is, <math> \beta A  = 1</math> and</li><li>2. The phase shift around the loop is zero or an integer multiple of <math>2\pi</math>.</li></ol>         |                 |






| <b>c)</b>               | <b>State condition for both junction to operate BJT in cut off state, Active state and saturation state.</b>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                  | <b>(4 Marks)</b> |            |        |            |                         |         |         |         |                       |         |         |         |  |
|-------------------------|-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|------------------|------------|--------|------------|-------------------------|---------|---------|---------|-----------------------|---------|---------|---------|--|
| Ans:                    | <table border="1" style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th></th> <th style="color: red;">Cutoff</th> <th style="color: red;">Active</th> <th style="color: red;">Saturation</th> </tr> </thead> <tbody> <tr> <td style="text-align: center;">Collector-base junction</td> <td style="text-align: center;">Reverse</td> <td style="text-align: center;">Reverse</td> <td style="text-align: center;">Forward</td> </tr> <tr> <td style="text-align: center;">Base-emitter junction</td> <td style="text-align: center;">Reverse</td> <td style="text-align: center;">Forward</td> <td style="text-align: center;">Forward</td> </tr> </tbody> </table> |                  | Cutoff     | Active | Saturation | Collector-base junction | Reverse | Reverse | Forward | Base-emitter junction | Reverse | Forward | Forward |  |
|                         | Cutoff                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                        | Active           | Saturation |        |            |                         |         |         |         |                       |         |         |         |  |
| Collector-base junction | Reverse                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                       | Reverse          | Forward    |        |            |                         |         |         |         |                       |         |         |         |  |
| Base-emitter junction   | Reverse                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                       | Forward          | Forward    |        |            |                         |         |         |         |                       |         |         |         |  |
| <b>d)</b>               | <b>Name the type of rectifier for each of following feature : (i) Highest rectifier efficiency (ii) Highest form factor (iii) Two diode rectifier circuit (iv) PIV = 2Vm.</b>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                 |                  |            |        |            |                         |         |         |         |                       |         |         |         |  |
| Ans:                    | <b>(4 Marks)</b><br>(i) <b>Highest rectifier efficiency</b> : Center tapped & Bridge full wave Rectifier<br>(ii) <b>Highest form factor</b> : Center tapped & Bridge full wave Rectifier<br>(iii) <b>Two diode rectifier circuit</b> : Center tapped full wave Rectifier<br>(iv) <b>PIV = 2Vm</b> : Center tapped full wave Rectifier                                                                                                                                                                                                                                                                                                                                         |                  |            |        |            |                         |         |         |         |                       |         |         |         |  |
| <b>Q.4 A)</b>           | <b>Attempt any THREE of the following :</b>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                   | <b>12 Marks</b>  |            |        |            |                         |         |         |         |                       |         |         |         |  |
| a)                      | <b>Sketch circuit diagram of Hartely oscillator. State expression for frequency of oscillation</b>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                            |                  |            |        |            |                         |         |         |         |                       |         |         |         |  |
| Ans:                    | <b>Circuit Diagram</b> <span style="float: right;"><b>(3 Marks)</b></span><br>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                |                  |            |        |            |                         |         |         |         |                       |         |         |         |  |



|      |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                     |
|------|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
|      | <p>Expression for frequency of oscillation: <span style="float: right;">(1 Mark)</span></p> $f = \frac{1}{2\pi\sqrt{L_T C}}$ <p>where: <math>L_T = L_1 + L_2 + 2M</math></p>                                                                                                                                                                                                                                                                                                                                                                                                                                                                        |
| b)   | <p>Sketch circuit diagram of bridge rectifier with LC filter. State function of each component. <span style="float: right;">(2 Marks)</span></p>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                    |
| Ans: | <p>Circuit diagram : <span style="float: right;">(2 Marks)</span></p> <p>Components and its function: : <span style="float: right;">(2 Marks)</span></p> <ol style="list-style-type: none"><li>1. Transformer- An electrical device which transfers electrical energy from one electric circuit to other, without changing the frequency. The energy transfer takes place with change in voltage and current.</li><li>2. Rectifier- Convert AC into pulsating DC.</li><li>3. Inductor- Blocks AC components of rectified output and only pass DC components.</li><li>4. Capacitor- It bypasses AC components if any and gives DC to load.</li></ol> |
| c)   | <p>In a common base configuration, the emitter current is 1 mA. If the emitter circuit is open, the collector current is 50 microA. Find total collector current. Assume <math>\alpha = 0.92</math>.</p>                                                                                                                                                                                                                                                                                                                                                                                                                                            |
| Ans: | <p>Given Data : <math>I_E = 1\text{mA}</math><br/><math>I_{CBO} = 50\ \mu\text{A}</math>, <math>\alpha = 0.92</math><br/>Using Equation: <span style="float: right;">(4 Marks)</span></p> $I_C = \alpha I_E + I_{CBO}$ $I_C = (0.92 \times 1\text{mA}) + 0.05\text{mA}$ $I_C = 0.97\text{mA}$                                                                                                                                                                                                                                                                                                                                                       |

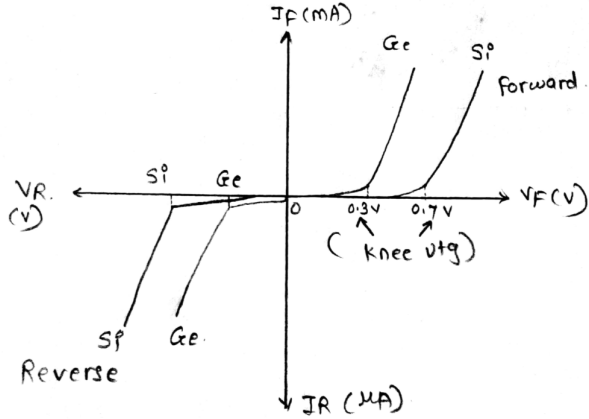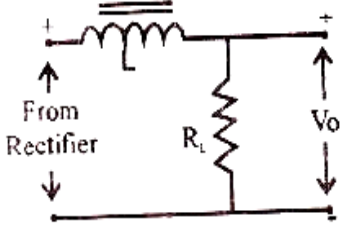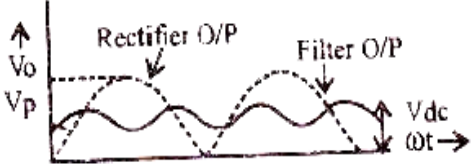


|      |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                         |
|------|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| d)   | <p><b>Sketch and label V-I characteristics of P-N junction diode. Write steps to calculate dynamic forward bias resistance.</b></p>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                     |
| Ans: | <p><b>V-I characteristics of P-N junction diode :</b> <span style="float: right;"><b>(2 Marks)</b></span></p>  <p><b>Dynamic forward bias resistance:-</b> <span style="float: right;"><b>(2 Marks)</b></span></p> <p>Dynamic resistance is defined as the ratio of change in voltage to the change in current. It is denoted as <math>r_f</math>.</p> $r_f = \frac{\text{Change in voltage}}{\text{Change in current}}$                                                                                                                               |
| e)   | <p><b>Explain operation of series inductor filter and find out its ripple factor.</b></p>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                               |
| Ans: | <p><b>Circuit diagram of series inductor filter :</b> <span style="float: right;"><b>(2 Marks)</b></span></p>  <p><b>a) Inductor Filter</b></p>  <p><b>b) Waveforms</b></p> <p><b>Operation of Series Inductor Filter :</b> <span style="float: right;"><b>(1 Mark)</b></span></p> <p>A high value of inductor is connected in series with load. Then the combination is connected across the rectifier. The Inductive reactance is directly proportional to</p> |





|             |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                     |
|-------------|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
|             | <p>frequency. Therefore for AC contents inductor offers high opposition, and hence block the AC signals. For DC signal, freq. is zero. <math>X_L=0</math>. i.e. inductor acts as a short ckt. Thus all DC signals from rectifier are given to load.</p> <p>Applying KVL to the series inductor ckt.</p> $V_0 = V_R - I * X_L$ <p>For DC input <math>F=0</math> and <math>X_L=0</math>. Therefore <math>V_0=V_R</math>. Thus DC components reach to load.</p> <p>For AC input Freq. is high, <math>X_L</math> is high, <math>I * X_L</math> drop is high, therefore <math>V_0</math> is small as compared to <math>V_R</math>.</p> <p>Inductor opposes change in current through it. So, current waveform is made smooth.</p> <p>This filter operates properly and effectively for higher values of currents. Hence increase in current reduces ripple factor.</p> $\text{Ripple Factor:- } RF = \frac{R}{3\sqrt{2}\omega L} \quad (1 \text{ Mark})$ |
| <b>Q.5</b>  | <b>Attempt any TWO of the following : <span style="float: right;">12 Marks</span></b>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                               |
| (a)         | <b>A transistor is connected in common emitter (CE) configuration with collector supply <math>V_{CC}</math> of 8V. Voltage drop across resistance <math>R_C</math> connected in series with collector is 0.5 V. The value of <math>R_C</math> is 800 ohm. If alpha (<math>\alpha</math>) equal to 0.96, calculate : (i) Collector-emitter voltage (ii) Collector current (iii) Base current</b>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                     |
| <b>Ans:</b> | <p><b>Given data :</b></p> <p><math>V_{CC} = 8V</math>      <math>R_C = 800 \Omega</math>      <math>\alpha = 0.96</math>      <math>V_{RC} = 0.5 V</math>.</p> <p>By using Equations</p> <p>(i) <b>Collector-emitter voltage :</b> <span style="float: right;">( 2 Marks)</span></p> $V_{CE} = V_{CC} - I_C R_C$ $V_{CE} = 8 - 0.5 = 7.5 V$ <p>(ii) <b>Collector current :</b> <span style="float: right;">( 2 Marks)</span></p> $I_C = \frac{V_{CC} - V_{CE}}{R_C}$ $= 0.625 mA$ <p>(iii) <b>Base current :</b> <span style="float: right;">( 2 Marks)</span></p> $I_B = \frac{I_C(1 - \alpha)}{\alpha}$ $= 26.04 \mu A$                                                                                                                                                                                                                                                                                                                          |

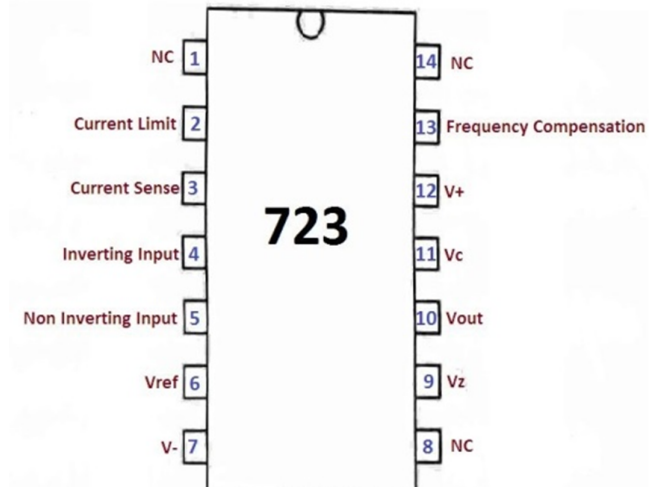

|      |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                       |
|------|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| b)   | <b>Sketch pin configuration of IC 723. State functions of each pin. Sketch circuit diagram for obtaining 6V output d.c. regulated voltage using IC 723.</b>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                           |
| Ans: | <p style="text-align: center;"><b>(Configuration : 2 Mark, Function : 2 Marks &amp; Diagram : 2 Marks)</b></p> <p>1) Pin configuration of IC 723 : <span style="float: right;"><b>(2 Mark)</b></span></p> <div style="text-align: center;"></div> <p>2) Functions of each pin:- <span style="float: right;"><b>(2 Marks)</b></span></p> <p><b>V<sub>+</sub> and V<sub>-</sub>:</b> These are the supply voltage terminals of the IC. V<sub>+</sub> is the positive terminal and V<sub>-</sub> is the negative terminal.</p> <p><b>Non Inverting Input:</b> This is the non-inverting input of the error amplifier whose output is connected to the series pass transistor. Reference voltage or a portion of it is given to the non-inverting input.</p> <p><b>Inverting Input:</b> This is the inverting input of the error amplifier whose output is connected to the series pass transistor. Usually output voltage or a portion of it is given to the inverting input. This makes the output voltage constant.</p> <p><b>V<sub>ref</sub>:</b> It is the reference voltage output of the IC. It is the output of voltage reference amplifier. Its output voltage is about 7.15V.</p> <p><b>V<sub>out</sub> :</b> It is the output terminal of the IC. Usually output voltage ranges from 2 to 37V. This pin can provide up to 150mA current.</p> <p><b>Current Limit:</b> It is the base input of the current limiter transistor. This pin is used for current limiting or current fold back applications.</p> <p><b>Current Sense:</b> This is the emitter of current limiting transistor. This terminal is used with current limiting and current fold-back applications.</p> |



**V<sub>c</sub>** : This is the collector input of the series pass transistor. It is usually directly connected to the positive supply voltage if an external transistor is not used.

**Freq. Comp:** Frequency Compensation : This pin is used to connect a capacitor which bypasses high frequency noises. It is the output of error amplifier. The capacitor is connected between this pin and inverting input of the error amplifier. The prescribed value of this capacitor varies for different types of regulators.


**Current Sense:** This is the emitter of current limiting transistor. This terminal is used with current limiting and current fold-back applications.

**V<sub>c</sub>**: This is the collector input of the series pass transistor. It is usually directly connected to the positive supply voltage if an external transistor is not used.

**Freq. Comp:** Frequency Compensation: This pin is used to connect a capacitor which bypasses high frequency noises. It is the output of error amplifier. The capacitor is connected between this pin and inverting input of the error amplifier. The prescribed value of this capacitor varies for different types of regulators.

**V<sub>z</sub>**: It is the anode of the zener diode whose cathode connected to the output terminal. It is usually used for making negative regulators.

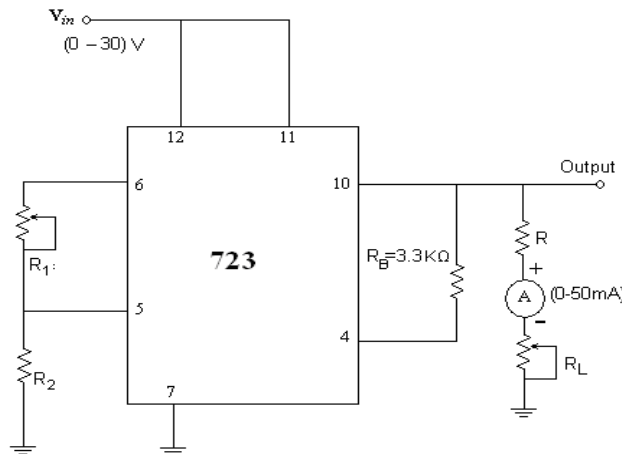**3) Circuit diagram for obtaining 6V output d.c. regulated voltage using IC 723 (2 Marks)**





**Expression**  $V_{out} = V_{ref} * (R_2 / R_1 + R_2)$

Assume any value of  $R_2$ ,  $R_1$  can be calculated.



|            |                                                                                                                                                                                                                                                                                                                                                                                                                                           |
|------------|-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| c)         | <b>Implement the fundamental logic gates 'OR gate', 'AND gate', 'NOT gate' using only NAND gates.</b>                                                                                                                                                                                                                                                                                                                                     |
| Ans:       | <b>Fundamental logic gates 'OR gate', 'AND gate', 'NOT gate' using only NAND gates:</b><br><p style="text-align: right;"><b>(6 Marks)</b></p> <p style="text-align: right;"><b>(6 Marks)</b></p>                                                                                                                                                                                                                                          |
| <b>Q.6</b> | <b>Attempt any TWO of the following : <span style="float: right;">12 Marks</span></b>                                                                                                                                                                                                                                                                                                                                                     |
| a)         | <b>Sketch circuit diagram of RC phase shift oscillator. If value of capacitor <math>C = C_1 = C_2 = C_3 = 5 \text{ pF}</math> and frequency of oscillation is 800 Hz, calculate value of resistor R, (<math>R = R_1 = R_2 = R_3</math>).</b>                                                                                                                                                                                              |
| Ans:       | <b>Circuit diagram of RC phase shift oscillator <span style="float: right;">(3 Marks)</span></b><br><p style="text-align: right;">or equivalent circuits</p> <p><b>Given data :</b></p> <p style="text-align: center;"><math>f_o = 800 \text{ Hz}</math> and <math>C = 5 \text{ pF}</math></p> <p>Using Expression for frequency of oscillation</p> $f_o = \frac{1}{2\pi(\sqrt{6})CR}$ <p style="text-align: right;"><b>(1 Marks)</b></p> |

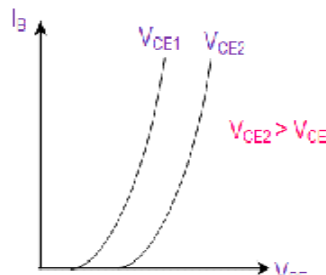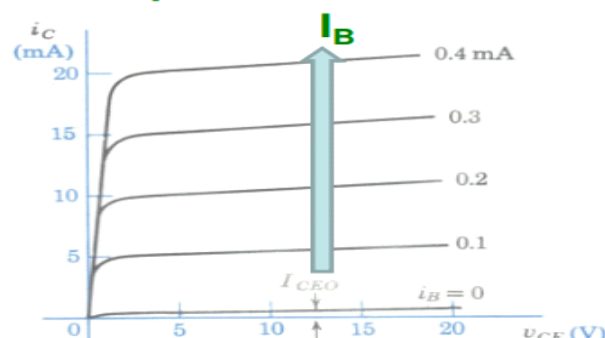

|      |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                      |
|------|----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
|      | <p>Putting values in above equation</p> <p style="text-align: center;"><b>R = 16.24 MΩ</b></p> <p style="text-align: right;"><b>(2 Marks)</b></p>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                    |
| b)   | <p>For common emitter configuration sketch input Characteristics for two different values of <math>V_{CE}</math> and output characteristics for two different values of <math>I_B</math>. Write formula for input resistance and output resistance.</p>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                              |
| Ans: | <p style="color: red;"><b>( Input characteristics 2 Marks &amp; Output characteristics 2 Marks)</b></p> <div style="display: flex; justify-content: space-around;"> <div style="text-align: center;"> <p style="color: green;"><b>Input characteristics</b></p>  </div> <div style="text-align: center;"> <p style="color: green;"><b>Output characteristics</b></p>  </div> </div> <div style="margin-top: 20px;"> <p><math>r_i = \frac{\Delta V_{BE}}{\Delta I_B}</math>      .....for <math>V_{CE} = \text{constant}</math>      <b>(1 Mark)</b></p> <p><math>r_o = \frac{\Delta V_{CE}}{\Delta I_C}</math>      .....for <math>I_B = \text{constant}</math>      <b>(1 Mark)</b></p> </div> |
| c)   | <p><b>Perform following number system conversion :</b></p> <p>(i) <math>(589)_{10} = ( \quad )_2</math>      (ii) <math>(101101)_2 = ( \quad )_{16}</math></p> <p>(iii) <math>(413)_8 = ( \quad )_2</math>      (iv) <math>(5AF)_{16} = ( \quad )_{10}</math></p> <p>(v) <math>(AC8)_{16} = ( \quad )_2</math>      (vi) <math>(106)_8 = ( \quad )_{10}</math></p>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                   |
| Ans: | <p style="text-align: right;"><b>(1 Mark for each)</b></p> <p>(i) <math>(589)_{10} = (1001001101)_2</math></p> <p>(ii) <math>(101101)_2 = ( 2D )_{16}</math></p> <p>(iii) <math>(413)_8 = (100001011)_2</math></p> <p>(iv) <math>(5AF)_{16} = (1455)_{10}</math></p> <p>(v) <math>(AC8)_{16} = (101011001000)_2</math></p> <p>(vi) <math>(106)_8 = (70)_{10}</math></p>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                              |