

# 17318

**21314**

**3 Hours / 100 Marks**

Seat No.

--	--	--	--	--	--	--	--

- 
- Instructions* – (1) All Questions are *Compulsory*.
- (2) Answer each next main Question on a new page.
- (3) Illustrate your answers with neat sketches wherever necessary.
- (4) Figures to the right indicate full marks.
- (5) Assume suitable data, if necessary.
- (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
- (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

1. a) Attempt any **SIX** of the following: **12**
- i) Define the r.m.s. value of an alternating current.
- ii) Define the bandwidth of a series resonant circuit and give the expression of the same.
- iii) Explain the purpose of four wires in three phase four wire option..
- iv) Draw voltage waveform of a 3-phase ac supply w.r.t. time.
- v) Draw a star connected 3 phase load and show line voltages and phase voltages on it.

P.T.O.

- vi) State any two methods for reducing the starting current of induction motor.
- vii) For reversing the direction of rotation of rotor of induction motor, what changes has to be done in the supply system ?
- viii) State four types of wires used for wiring of an electrical installation.

b) **Attempt any TWO of the following:**

**08**

- i) Explain the meaning of in phase voltages and out of phase voltages with the help of waveform diagrams and phasor diagram.
- ii) State the Faraday's laws of electromagnetic induction and give the expression for the induced emf with the meaning of each term.
- iii) State the types of single phase induction motor. Explain working of any one with a neat diagram.

2. **Attempt any FOUR of the following:**

**16**

- a) Consider R-L series circuit connected across an a.c. voltage  $v = V_m \sin \omega t$ . Write expression for instantaneous current, phasor diagram, voltage triangle and power consumed.
- b) Explain the concept of impedance and impedance triangle.
- c) State the different types of power in A.C. circuit. Write the expression and units for the same.
- d) Explain the meaning of resonance in series R.L.C. circuit. Derive expression of resonant frequency in R.L.C. series circuit.
- e) Explain three phase balanced load and unbalanced load.
- f) Compare two winding transformer with auto-transformer. (any four points)

**3. Attempt any FOUR of the following:****16**

- a) Define and explain the meaning of Q-factor and give the mathematical expression for Q factor in RLC series circuit.
- b) The voltage and current equations in an A.C Circuit are  
 $V = 140\sin 314t$  and  $i = 3\sin\left(314t - \frac{\pi}{2}\right)$  find the rms value, average value 2 power factor and state the power factor lagging or leading.
- c) A resistance of 25 ohm, inductance of 0.4H and capacitance of 125 microfarads are connected in series to a 230V, 50Hz supply, find the impedance of the circuit, p.f, active power and apparent power.
- d) Explain statically induced emf and dynamically induced emf.
- e) State and explain the Fleming's Right hand rule and Lenz's law for deciding the direction of induced emf.
- f) What is KVA rating of transformer ? Why transformer is rated in KVA.

**4. Attempt any FOUR of the following:****16**

- a) A 50Hz voltage of 130V (r.m.s. value) is connected across an R.L series combination of  $80\Omega$  and 0.4H, find the expressions for voltage and current, p.f. and draw the phasor diagram.
- b) A single phase transformer has 375 turns on the input side and 1050 turns on the output side. The transformer is connected to a 400V, 50Hz a.c. supply. The net cross sectional area of core is  $40\text{cm}^2$ , find the flux density in Tesla and voltage developed across the supply side of the transformer.
- c) "The actual speed of an induction motor can never be equal to the synchronous speed of the motor." Explain why ?

- d) Explain the principle of operation of induction motor.
- e) Explain the stator frequency control method for speed control of induction motor.
- f) Explain the method of making single phase induction motors as self-start motors.

**5. Attempt any FOUR of the following:**

**16**

- a) An R-L-C series circuit has an impedance of  $14.28\Omega$ . When connected across an a.c. source of supply of 200V and 50Hz. If the resistance of the circuit is  $10\Omega$  and inductance is 0.1H find the capacitance of the circuit and the current drawn by the circuit.
- b) Three impedances each of  $4\Omega$  resistance, and  $4\Omega$  inductive reactance in series are connected in star and the potential difference between a line and neutral terminal is 231 volts, find the phase current, p.f. and the total power drawn.
- c) Explain in brief the constructional features and working of isolating transformer and state its application.
- d) Draw the torque speed characteristics of 3 phase induction motor and explain the same.
- e) Explain how stepper motor rotates in steps.

**6. Attempt any FOUR of the following:****16**

- a) Three resistances each of  $30\Omega$  are connected in delta across a 3 phase, 440V, 50Hz supply. Calculate the phase current, line current and the active power of the cct.
  - b) A 50 KVA, 1- $\phi$  transformer has a full load on loss of 4kW and ironloss of 2 kW. Find the efficiency of the transformer at half and full load at unit power factor.
  - c) State two application of each of the following type of transformers.
    - i) Power transformer
    - ii) R. F transformer
    - iii) Pulse transformer
    - iv) A. F. transformer
  - d) Explain the working principle and the operation of universal motors.
  - e) Explain the working of a servomotor.
  - f) Explain the necessity of earthing. State the types of earthing.
-

17318

**21314**

**3 Hours / 100 Marks**

---