

# 17319

**21314**

**3 Hours / 100 Marks**

Seat No.

--	--	--	--	--	--	--	--

- Instructions* –
- (1) All Questions are *Compulsory*.
  - (2) Illustrate your answers with neat sketches wherever necessary.
  - (3) Figures to the right indicate full marks.
  - (4) Assume suitable data, if necessary.
  - (5) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

1. a) **Attempt any SIX of the following:** **12**
- i) Name different operating region of BJT.
  - ii) Define the term stability factor.
  - iii) List advantages of transformer coupled amplifier (any two).
  - iv) Define enhancement mode and depletion mode w.r.t. MOSFET.
  - v) Draw basic tuned circuit.
  - vi) List application of class A amplifier (any two).
  - vii) Draw symbol of n-channel and p-channel JFET.
  - viii) Draw output characteristics of UJT.
- b) **Attempt any TWO of the following:** **8**
- i) Draw the ckt diagram for common base configuration and draw its output characteristics.
  - ii) Explain need of biasing. List any two methods of biasing.
  - iii) Draw block diagram of DC power supply and explain function of each block.

P.T.O.

2. **Attempt any FOUR of the following:** **16**
- Explain thermal runaway. How it should be avoided?
  - Draw D.C. load line of common emitter amplifier and define Q. point.
  - Draw construction and describe working of n-channel JFET with neat sketch.
  - Compare CB, CE, CC on basis of following points:
    - input resistance
    - output resistance
    - current gain
    - voltage gain.
  - Draw block diagram of voltage series and current series feedback.
  - Draw the circuit diagram of negative 5 voltage using 7905 IC. Describe its working.
3. **Attempt any FOUR of the following:** **16**
- In common emitter configuration if  $\beta = 150$  leakage current  $I_{CEO} = 100 \mu\text{A}$  and base current is 0.5 mA determine  $I_c$  and  $I_E$ .
  - Describe source self bias method of FET with neat circuit diagram.
  - Describe UJT as a relaxation oscillator with neat circuit diagram.
  - Draw the circuit diagram of two stage R–C coupled amplifier and describe its working.
  - Draw the functional block diagram of IC 723. Describe its working.
  - What is necessity of regulated power supply? Define load and line regulation.

**4. Attempt any FOUR of the following:****16**

- a) Describe the working of n-channel JFET with diagram.
- b) Describe transformer coupled amplifier with neat circuit diagram.
- c) Describe working of D-MOSFET with neat diagrams.
- d) Compare Class A, Class B, Class AB and Class C amplifier w.r.t. following points:
  - i) position of operating pt. on load line
  - ii) efficiency
  - iii) conduction angle
  - iv) O/P waveform.
- e) Describe the working of single stage Class A amplifier with circuit diagram.
- f) Describe the working of Bootstrap time base generator with circuit diagram.

**5. Attempt any FOUR of the following:****16**

- a) In common base connection  $\alpha = 0.95$  the voltage drop across resistance which is connected in collector is 2 V. Find base current if the value of resistance connected in collector is 2 k.
- b) A phase shift oscillator has  $R = 220\text{ k}$   $C = 500\text{ pf}$  calculate frequency of sine wave generator.
- c) Describe Class B push pull amplifier with neat circuit diagram.
- d) Describe FET as an amplifier with circuit diagram.
- e) Draw the circuit diagram of RC phase shift oscillator and describe its working.
- f) Describe +ve voltage regulator using IC 78XX series.

**6. Attempt any FOUR of the following:****16**

- a) Describe voltage divider biasing method in BJT with circuit diagram.
  - b) Describe the working of shunt voltage regulator using transistor with circuit diagram.
  - c) State Barkhausen criteria. List advantages of negative feedback over positive feedback (any two).
  - d) Describe the operating principle of single tuned amplifier with circuit diagram.
  - e) Describe the working principle of crystal oscillator with circuit diagram.
  - f) Draw construction and describe its working principle of UJT.
-

17319

**21314**

**3 Hours / 100 Marks**

---