



17320

21415

3 Hours/100 Marks

Seat No.

--	--	--	--	--	--	--	--	--	--

- 
- Instructions:** (1) **All questions are compulsory.**  
(2) **Illustrate your answers with neat sketches wherever necessary.**  
(3) **Figures to the right indicate full marks.**  
(4) **Assume suitable data, if necessary.**
- 

MARKS

1. A) Attempt **any six** :

12

- Convert the decimal no. 46 into BCD code and in excess 3 code.
- Give the two advantages of multiplexer.
- State the different triggering methods in digital circuit.
- State the various types of shift registers.
- Identify the IC 0800 and IC 0809.
- Compare EPROM and EEPROM (any two pts.).
- Write associative and commutative Boolean laws.
- Draw the logic symbol and truth table for two input NAND gate.

B) Attempt **any two** :

8

- Solve the following subtraction using 1's and 2's complement method.
  - $(52)_{10} - (65)_{10}$
  - $(101011)_2 - (11010)_2$ .
- Explain Full adder with its truth table, K-map simplification and logic diagram.
- Design a 4 : 1 MUX using 2 : 1 MUX and write truth table.

P.T.O.

2. Attempt **any four** :

16

- a) Perform the following multiplication in binary number system  $(15)_{10} \times (8)_{10}$ .
- b) State and prove the both De-Morgan's theorems with logic diagram.
- c) Explain the concept of Minterm and Maxterm with example.
- d) Draw and explain OR flip flop using NAND gate with its truth table.
- e) Draw the circuit diagram of 3 bit synchronous up counter with its truth table and explain its working.
- f) Define the following specifications of DAC :
  - i) Resolution
  - ii) Linearity
  - iii) Accuracy
  - iv) Settling time.

3. Attempt **any four** :

16

- a) State the rules for BCD addition.
- b) Compare CMOS and TTL logic family on following points : propagation delay, fan out, power dissipation, Noise immunity.
- c) Design 1 : 16 demultiplexer using 1 : 4 demultiplexer.
- d) Compare combinational circuit with sequential circuit (any 4 points).
- e) Draw the block diagram of dual slope ADC and explain its working with waveforms.
- f) State the different types of ROMs and explain any one type of ROM.



**MARKS**

4. Attempt **any four** : **16**

- a) Design a 3 : 8 line decoder with truth table and logic diagram and give IC No. for the same.
- b) Draw and explain decimal to BCD priority encoder using IC 74147.
- c) What is race around condition in JKFF ? How it can be avoided ?
- d) Explain the working of 4 bit ring counter with a neat diagram.
- e) Describe successive approximation ADC with neat circuit diagram.
- f) Compare Static RAM with Dynamic RAM (any 4 pts.).

5. Attempt **any four** : **16**

- a) Draw the circuit of TTL totem pole two input NAND gate and explain its working.
- b) Draw and explain the circuit diagram of 1 : 4 demultiplexer using logic gates.
- c) Explain with neat diagram. How to convert JK flip flop into TFF ? Write truth table.
- d) How can IC 7490 be used as a decade counter with neat block diagram ?
- e) How many bits are required for a resolution of 5 mV and full scale voltage is 15 V ?
- f) Compare volatile and non-volatile memory (any 4 pts.).

6. Attempt **any four** : **16**

- a) Convert the following :
  - i)  $(5C7)_{16} = (?)_{10}$
  - ii)  $(2598)_{10} = (?)_{16}$
  - iii)  $(10110)_2 = (?)_{10} = (?)_{16}$ .
- b) Why NAND & NOR gates are called as an universal gates ? Realise OR gate using NAND gate.



c) Reduce the following Boolean expression using Boolean laws :

i)  $Y = A\bar{B} + \bar{A}B + AB + \bar{A}\bar{B}$

ii)  $Y = A\bar{B}C + \bar{A}BC + ABC$  .

d) Realize the following function using demultiplexer :

i)  $F_1 = \Sigma m (0, 1, 3, 7, 11, 13, 15)$

ii)  $F_2 = \Sigma m (2, 4, 8, 10, 12)$  .

e) Design MOD 10 asynchronous up counter, with its truth table and timing diagram.

f) Calculate the analog output of a 4 bit DAC, if the digital input is 1011. Assume  $V_{FS} = 5$  V.

---