

correction in Q 4 e) last line:

voltage drop in 10 Ohm resistance is  $= I \times R = 3.09 \times 10 = 30.9 \text{ V}$