

17444

21314

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* – (1) All Questions are *Compulsory*.
- (2) Answer each next main Question on a new page.
- (3) Illustrate your answers with neat sketches wherever necessary.
- (4) Figures to the right indicate full marks.
- (5) Assume suitable data, if necessary.
- (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.
- (7) Preferably write the answer in sequential order.

Marks

1. a) Answer any **SIX** of the following: 12
- i) Draw the symbols of:
- 1) UJT
- 2) TRIAC
- ii) State two advantages of IGBT.
- iii) List two applications of TRIAC.
- iv) Write classification of choppers.
- v) What are the limitations of R triggering circuit?
- vi) List applications of inverters. (Any four)

P.T.O.

- vii) State the need of polyphase rectifiers.
- viii) Draw the block diagram of SMPS and label it.

b) Answer any **TWO** of the following:

08

- i) A single phase full controlled bridge rectifier is supplied with voltage $v = 230 \sin (314 t)$; and is delivering power to a resistive load. Find the average output voltage, if the firing angle $\alpha = 45^\circ$.
- ii) Define inverter. Give classification of inverters.
- iii) Define the following terms with respect to inverters.
 - 1) Harmonic factor of n^{th} harmonic
 - 2) Total harmonic distortion
 - 3) Distortion factor
 - 4) Lowest order harmonics

2. Answer any **FOUR** of the following:

16

- a) Define firing angle and conduction angle. What is the effect of firing angle on average output voltage?
- b) Draw the circuit diagram of step up chopper. State its operating principle.
- c) Draw the block diagram of UPS. State the function of each block.
- d) Draw the constructional details of DIAC. Draw the VI characteristics of DIAC.
- e) Draw the circuit diagram of full wave RC triggering circuit to turn ON the thyristor. Draw the waveforms of input voltage and output voltage.
- f) Draw the circuit diagram of series inverter. Draw the input and output waveforms.

3. Answer any FOUR of the following:**16**

- a) Differentiate between SCR and TRIAC on the basis of :
 - i) symbol
 - ii) layered diagram
 - iii) operating quadrant and
 - iv) applications
- b) Draw the circuit diagram of single phase half wave controlled rectifier with R load. Draw the waveforms of input voltage, load voltage and voltage across SCR.
- c) Draw the VI characteristics of SCR. State the effect of gate current on the breakover voltage.
- d) Draw the VI characteristics of power transistor. Label different regions.
- e) Draw the single phase full wave bridge type controlled rectifier. Draw the waveforms of input voltage, load voltage and voltage across SCR.
- f) Differentiate between controlled and uncontrolled rectifiers.
(Any four points)

4. Answer any FOUR of the following:**16**

- a) Draw the circuit diagram of step down chopper. Draw the input output waveforms.
- b) Draw the constructional diagram of GTO. State the operating principle.
- c) Draw the circuit diagram of light dimmer using DIAC and TRIAC and sketch the i/p - o/p voltage waveforms.
- d) Draw the circuit diagram of class C commutation circuit.
Draw the waveforms.

- e) Draw the circuit diagram of a battery charger. State its operation.
- f) Compare between step up and step down chopper with respect to:
 - i) Input and output waveforms
 - ii) Output voltage equation
 - iii) Switch position (connection)
 - iv) Applications

5. Answer any FOUR of the following:

16

- a) Draw the neat circuit diagram of Fan Speed Regulator using TRIAC. Describe its working.
- b) Draw the VI characteristics of LASCR. What is the effect of light intensity on forward breakover voltage?
- c) Describe the effect of freewheeling diode with respect to single phase centre tap full controlled rectifier with RL load.
- d) Describe the operation of pulse transformer used in triggering circuits.
- e) Draw the labelled constructional diagram of N-channel IGBT.
- f) Differentiate between single phase controlled half wave rectifier and single phase controlled full wave rectifier.

6. Answer any FOUR of the following:**16**

- a) Draw the circuit diagram of DC low power flasher. Describe its operation.
 - b) Draw the circuit diagram of three phase half wave controlled rectifier. Draw the waveforms of input voltage and output voltage.
 - c) What is forward voltage triggering method of turning on the thyristor?
 - d) State two applications each for :
 - i) SCR
 - ii) PUT
 - e) What is the second breakdown in power BJT? How is it avoided?
 - f) Draw the circuit diagram of synchronized UJT triggering and describe its working.
-

17444

21314

3 Hours / 100 Marks
