



17329

15162

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) *All questions are compulsory.*
 - (2) *Answer **each** Section on **separate** answer sheet.*
 - (3) *Illustrate your answers with neat sketches **wherever** necessary.*
 - (4) *Figures to the **right** indicate **full** marks.*
 - (5) *Assume suitable data, if **necessary**.*
 - (6) *Use of Non-programmable Electronic Pocket Calculator is **permissible**.*
 - (7) *Mobile Phone, Pager and any other Electronic Communication devices are **not** permissible in Examination Hall.*

Marks

SECTION – I

1. Attempt **any nine** of the following :

18

- a) Define the following terms related to A.C. fundamental.
 - i) Frequency
 - ii) RMS value.
- b) For delta connected load, state numerical relationship between,
 - i) Line current and phase current
 - ii) Line voltage and phase voltage.
- c) State working principle of transformer.
- d) Define energy and power. State its unit.
- e) Draw a 3-phase star connected supply system.
- f) State the working principle of A.C. motor.
- g) State the functions of ELCB and MCCB.
- h) List applications of autotransformer.
 - i) Name different types of safety tools.
- j) State emf equation of single phase transformer. Write the meaning of each term.
- k) Write the classification of drives.

2. Attempt **any four** of the following :

16

- a) State and explain the factors to be considered for the selection of electrical drives.
- b) Explain the concept of voltage and current with their units.
- c) Three resistances of 25 ohm each are connected in delta across a 3-phase 400 volt a.c. supply. Draw the circuit. Find phase current, line voltage and phase voltage.
- d) Define the following terms :
 - i) Transformation ratio
 - ii) Voltage ratio
 - iii) Current ratio
 - iv) Turns ratio.
- e) Explain safety precautions to be taken to avoid electrical shocks.
- f) Explain construction and working principle of universal motor.

P.T.O.



3. Attempt **any four** of the following :

16

- Draw a speed-torque characteristics of 3-phase induction motor and explain the nature of the same characterize.
- Draw a neat diagram of sodium vapour lamp, label the parts. Also state how it emits the light.
- Define earthing. State the necessity of earthing of an electrical motors and appliances.
- Explain the construction of 3-phase autotransformer with diagram.
- With neat sketch explain Direct ON line starter for 3-phase Induction motor.
- Explain the functions of enclosures and mountings used for electrical drives.

SECTION – II

4. Attempt **any nine** of the following :

18

- Define insulator and semiconductor with example.
- Draw the symbols of
 - Photodiode
 - Zener diode
 - UJT
 - PN junction diode.
- What is rectifier ? What are its types ?
- Draw the labelled symbol of OP-AMP.
- Define filter. State the function of filter.
- Draw the symbol of PNP and NPN transistor and state one application of transistor.
- Draw the energy band diagram for conductor and semiconductor.
- Draw the circuit diagram of single stage CB amplifier.
- Name the universal gates. Draw their symbol.
- List two ideal characteristics of operational amplifier.
- Convert $(100)_{10}$ to binary.

5. Attempt **any four** of the following :

16

- Explain bridge type full wave rectifier with circuit diagram and waveform nature.
- Draw the circuit of two stage RC coupled amplifier.
- Convert $(500.21)_{10}$ to its equivalent binary.
- Draw and explain non-inverting configuration of an OP-AMP.
- With the help of a neat diagram, explain the working and characteristics of LED.
- Draw the logic symbol and write the truth table for each of the following :
 - AND gate
 - NOT gate.

6. Attempt **any four** of the following :

16

- Draw and explain block diagram of regulated power supply.
 - Draw circuit diagram of phase shift oscillator and list its two applications.
 - Draw the symbol and truth table for following gate :
 - XOR
 - XNOR.
 - Describe the working of Hartley oscillator with circuit diagram.
 - Explain zener diode as a voltage regulator.
 - Explain OP-AMP as subtractor.
-