

17475

15162

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Assume suitable data, if necessary.
 - (5) Use of Non-programmable Electronic Pocket Calculator is permissible.

Marks

1. **Attempt any FIVE :**

4 × 5 = 20

- (a) State advantages and disadvantages of digital systems.
- (b) Convert :
 - (i) $12.8_{(10)}$ to binary no.
 - (ii) 423 (BCD) to binary no.
- (c) Draw symbols and write truth table for following gates :
 - (i) NAND gate
 - (ii) EX-NOR gate
- (d) Simplify given functions using k-map, $p = \Sigma_m (1, 2, 3, 8, 12)$; $q = \Sigma_m (0, 3, 5, 8, 14)$.
- (e) Compare : Combinational circuits with sequential circuit. (any four points)
- (f) State and explain specifications of DAC.
- (g) Give classification of ROM and RAM.

2. **Attempt any FOUR :**

4 × 4 = 16

- (a) Simplify given expression using boolean algebra, de-Morgan's theorem and draw the simplified circuit using NAND gates.

$$n = xy\bar{z} + y\bar{z} + \bar{x}yz + \bar{x}\bar{y}\bar{z}$$

- (b) Draw the block diagram of digital comparator (IC 7485) and write its truth table.
- (c) Design half adder using NAND gates only.
- (d) List triggering methods for flip-flop. Explain positive and negative edge triggering methods.
- (e) Shift registers are considered as basic memory devices, justify your answer with suitable example.
- (f) With block diagram, explain working 3-bit binary down counter.

3. Attempt any TWO :**8 × 2 = 16**

- (a)
 - (i) Perform $81_{(10)} - 92_{(10)}$ in binary using 2's complement method.
 - (ii) Compare TTL with CMOS family with reference to power supply, fan-out, power dissipation and speed.
- (b) Draw neat circuit diagram of 16 : 1 multiplexer using NAND gates. Write its logical equation and truth table. State the need of MUX.
- (c) Draw and explain successive approximation type ADC and state its advantages and draw backs.

4. Attempt any TWO :**8 × 2 = 16**

- (a) Solve :
 - (i) Convert 1100 0101 1100 GRAY code to Binary.
 - (ii) Convert $59_{(10)}$ to Octal & Hexadecimal.
 - (iii) Subtract 10101 from 01111 (using 1's complement method)
 - (iv) Add : $11111_2 + 01110_2$
- (b) State need of DEMUX. Explain logic diagram of 1 : 8 DEMUX using NAND logic, with its truth table. Also, state the difference between DEMUX & decoder.
- (c) List different types of DAC techniques and explain any of them with the help of circuit diagram. State drawbacks of used technique.

5. Attempt any TWO :**8 × 2 = 16**

- (a) List any four laws of boolean algebra :
 - (i) Draw logic circuit for Boolean expression $y = A\bar{B}C + \bar{A}B$ using basic gates.
 - (ii) Simplify $y = \bar{A}B + ABC + \bar{A}\bar{B}CD$ using k-map.
- (b) Draw circuit diagram of J-K f/f using NAND gate S. Explain its working with truth table. What is race-around condition ? How it can be overcome ? List the methods to be used for avoiding race-around condition.
- (c)
 - (i) Compare : Synchronous counter with Asynchronous counter by four points.
 - (ii) Draw pin diagram of universal shift reg. IC (7495) and list its applications.

6. Attempt any FOUR :**4 × 4 = 16**

- (a) Convert the expression in POS form : $K = P\bar{Q}R + \bar{P}QR + PQRS + P\bar{S}$. Draw POS & SOP logic circuit.
 - (b) Explain operation of full adder using half adders.
 - (c) Draw the block diagram for BCD to 7-segment decoder (IC 7447) & draw its truth table.
 - (d) State & prove de-Morgan's theorem.
 - (e) Implement OR and EX-OR gates using NAND gates.
 - (f) Draw the logic diagrams & write truth tables for D-f/f & T-f/f.
-

