



17541

15162

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) *All questions are compulsory.*
 - (2) *Illustrate your answers with **neat** sketches **wherever** necessary.*
 - (3) *Figures to the **right** indicate **full** marks.*
 - (4) *Assume suitable data, if **necessary**.*
 - (5) *Mobile Phone, Pager and any other Electronic Communication devices are **not** permissible in Examination Hall.*

Marks

1. A) Attempt **any three**: **12**
 - a) State the need of protection circuits for power devices. List different types of protection circuits.
 - b) What are the types of choppers? Draw the basic circuit of step down chopper and describe its operation in brief.
 - c) State the types of inverters. Draw the circuit of current source inverter and describe its operation in brief.
 - d) Describe the working of relay type AC voltage stabilizer with suitable diagram.
- B) Attempt **any one**: **6**
 - a) Describe with circuit diagram how chopper can be operated in four quadrants.
 - b) Describe the working of series inverter with neat circuit diagram and waveforms.
2. Attempt **any two**: **16**
 - a) Draw di/dt protection circuit and describe its operation.
 - b) Describe the operation of single phase cycloconverter with suitable diagram and waveforms.
 - c) Draw block diagram of sequential timer for resistance welding. Describe the function of each block.
3. Attempt **any four**: **16**
 - a) Describe how SCR can be protected from overvoltage with neat circuit diagram.
 - b) Draw the circuit of servo type AC voltage stabilizer and describe its operation.
 - c) With the help of suitable diagram, explain the working of ON line UPS.
 - d) Draw neat diagram of line contractor using SCR and describe its working.
 - e) Explain the working of single quadrant class A chopper using SCRs with suitable diagram.

P.T.O.

4. A) Attempt **any three**:

- a) Describe the operation of Jones chopper with suitable diagram.
- b) Describe the operation of non-isolated SMPS with diagram.
- c) Draw symbols and V-I characteristics of SIT and MCT.
- d) Compare series inverter and parallel inverter on the basis of any four points.

B) Attempt **any one**:

- a) State the need of series and parallel connections of SCR. Draw circuit diagram of three SCRs in series and parallel connections.
- b) Describe how O/P voltage of inverter can be controlled using PWM techniques.

5. Attempt **any two**:

- a) Describe how voltage is stabilized using phase control method with suitable diagram. List two advantages of it.
- b) Describe operating principle of resistance welding with neat diagram. Explain types of resistance welding.
- c) Describe the operation of isolated SMPS with circuit diagram. List any two advantages and disadvantages.

6. Attempt **any four**:

- a) Draw the constructional diagram of FCT. Draw V-I characteristics of it.
 - b) Distinguish between relay type and servo type AC voltage stabilizer with reference to operating principle, efficiency, distortion and application.
 - c) Draw block diagram of OFF line UPS and describe its working.
 - d) State need of UPS. Draw the diagram of line interactive UPS and describe its working.
 - e) Draw the circuit of synchronous weld control and describe its operation.
-