



# 17563

**15162**

**3 Hours / 100 Marks**

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) *All questions are compulsory.*
  - (2) *Answer **each** next main question on a **new** page.*
  - (3) *Illustrate your answers with neat sketches **wherever** necessary.*
  - (4) *Figures to the **right** indicate **full** marks.*
  - (5) *Assume suitable data, if **necessary**.*

**Marks**

**1. Attempt any five :**

**20**

- a) What are active and passive components ? State any two example of each.
- b) Compare conductor and insulator (any four points).
- c) State the need of bridges in signal conditioning circuits.
- d) Give detail classification of types of control system.
- e) Compare digital and analog electronics (any four points).
- f) Explain in brief tensile testing method.
- g) Draw the symbol of AND gate and OR gate and write their truth table.

**2. Attempt any two :**

**16**

- a) What is PN junction diode ? Draw the diagram of full wave rectifier and explain its working.
- b) Draw and explain the construction and working of the following pressure sensors :
  - A) Bound on tube
  - B) Bellows.
- c) Draw the block diagram of PLC and explain the function of each block.

**3. Attempt any four :**

**16**

- a) Determine the value of resistor for following colour codes :
  - 1) Red, black, brown, silver
  - 2) Orange, blue, yellow, gold.
- b) Explain intrinsic and extrinsic type of semi-conductors.
- c) Describe how displacement is measured using LVDT.
- d) What is open loop system ? Explain with suitable example.
- e) What is flip flop ? Explain the working of JK flip flop with the help of truth table.
- f) Explain the working of card autoleveller.

**P.T.O.**



## Marks

**4. Attempt any four :**

16

- What is capacitor ? List its any two specification.
- Draw the symbol of PNP transistor and explain its working.
- Explain the active and saturation region of transistor with help of graph.
- What is a thermocouple ? State its principle and working.
- Explain the principle of automatic textile control system.
- List any eight features of 8051.

**5. Attempt any four :**

16

- State the property of inductor. List the types of inductors.
- Draw and explain the working of investing amplifier.
- What is actuator ? Explain the principle of pneumatic actuation.
- Explain in brief the concept of combined loop control system.
- Describe the working principle 3-bit asynchronous up counter.
- Explain the working of yarn evenness tester.

**6. Attempt any four :**

16

- a) How a transistor can be used as a switch ? Explain.
- b) Draw and explain V-I characteristics of diode.
- c) What is photo transistor ? Draw its symbol and state any two applications of it.
- d) Convert the following decimal number into binary :  
A)  $[15]_{10}$  B)  $[09]_{10}$ .  
and following binary number into decimal :  
A)  $[11011001]_2$  B)  $[00111001]_2$ .
- e) Compare RAM and ROM memory (any four points).
- f) Explain the mechanism of automatic weft straightening.

A)  $[15]_{10}$

B)  $[09]_{10}$ .

and following binary number into decimal :

A)  $[11011001]_2$

B)  $[00111001]_2$ .