

17215

16172

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Figures to the right indicate full marks.
 - (3) Assume suitable data, if necessary.
 - (4) Use of Non-programmable Electronic Pocket Calculator is permissible.

Marks

1. Attempt any TEN :

2 × 10 = 20

- (a) What is magnetic material ? State it's two applications.
- (b) Define Inductor. Draw its symbol.
- (c) What is dielectric material ? Enlist dielectric material used in capacitor.
- (d) State any Four applications of PN junction diode.
- (e) Draw symbol of (i) Tunnel diode (ii) LED
- (f) Calculate equivalent resistance IFRI and R_2 resistors are connected in parallel
 $R_1 = 10 \Omega$, $R_2 = 5 \Omega$
- (g) Define (i) Open circuit (ii) Short circuit
- (h) State Kirchhoff's voltage law.
- (i) State the need of Rectifier circuits.
- (j) State types of filters.
- (k) What is need of wave shaping circuit ?
- (l) Draw RC differentiator circuit.

2. Attempt any FOUR :**4 × 4 = 16**

- (a) Write down the colour code for following resistor :
 - (i) $150 \Omega \pm 5\%$ (ii) $4.6 \text{ k}\Omega \pm 20\%$
- (b) With help of constructional diagram, explain working of LDR.
- (c) State any Four specifications of capacitor and explain any two in details.
- (d) With help of constructional diagram, explain working of slug tunned inductor.
- (e) Draw and explain V-I characteristics of a P–N junction diode.
- (f) Calculate the value of capacitor with the help of colour code.
 - (i) Orange, Orange, Blue
 - (ii) Yellow, Violet, Yellow

3. Attempt any FOUR :**4 × 4 = 16**

- (a) Define static and dynamic resistance of diode.
- (b) Compare avalanche and zener breakdown.
- (c) Draw construction of Schottky diode and state it's four applications.
- (d) Which material is used for manufacturing of following LED ?
 - (i) Infrared LED (ii) Red or Green LED
 - (iii) Red or Yellow LED (iv) Blue LED
- (e) Draw circuit diagram and waveforms for centre-tap full wave rectifier.
- (f) With help of circuit diagram and waveform, explain shunt capacitor filter.

4. Attempt any FOUR :**16**


- (a) Define : (i) Efficiency (ii) TUF of Rectifier
- (b) With help of constructional diagram, explain working of air-gang capacitor.

- (c) Compare half wave rectifier and full wave rectifier.
- (d) With help of circuit diagram and waveform, explain working of CLC or π filter.
- (e) Write working principle of photodiode and state its two applications.
- (f) Give four applications of LASER diode.

5. Attempt any FOUR :

4 × 4 = 16

- (a) Compare linear and nonlinear waveshaping circuits.
- (b) Draw circuit diagram of RC Integrator and explain its working.
- (c) Compare : (i) Active n/w and passive n/w
(ii) Bilateral n/w and unilateral n/w
- (d) Define : (i) Clipper (ii) Clamper
- (e) State and explain Thevenin's theorem.
- (f) Using Norton's theorem find Norton's equivalent circuit of following :

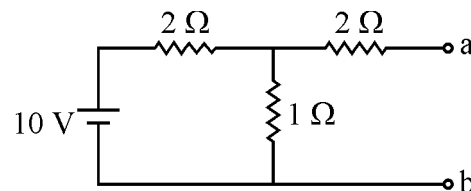

6. Attempt any FOUR :

4 × 4 = 16


- (a) With help of circuit diagram and waveform, explain working of positive series clipper.
- (b) Compare Integrator and differentiator.
- (c) State and explain superposition theorem.

P.T.O.

17215

[4 of 4]

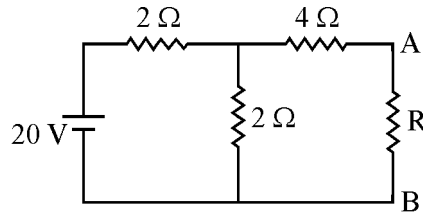- (d) Three resistances of 8Ω each are connected in delta. Find equivalent star connected network.
- (e) Calculate the value of resistance R in the branch AB so that maximum power is transferred to the load of the following circuit :



- (f) Using thevenin's theorem find load current I_L .

