

# 17319

**16172**

**3 Hours / 100 Marks**

Seat No.

--	--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
  - (2) Answer each next main Question on a new page.
  - (3) Illustrate your answers with neat sketches wherever necessary.
  - (4) Figures to the right indicate full marks.
  - (5) Assume suitable data, if necessary.
  - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
  - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

**1. (A) Attempt any SIX :**

**12**

- (a) What is transistor ? State any two applications of transistor.
- (b) Define operating point (Q) of the transistor as an amplifier.
- (c) Draw the circuit diagram and waveforms of single stage CE amplifier.
- (d) Draw the symbol of N-channel MOSFET. State any two application of MOSFET.
- (e) Define tuned amplifier. State types of resonant circuit.
- (f) What is cross-over distortion ?
- (g) Draw the transfer characteristics of N-channel JFET.
- (h) Draw the symbol and equivalent circuit of UJT.

- (B) Attempt any TWO :** **08**
- (a) Explain how transistor works as a switch. Also draw its input and output waveforms.
  - (b) Explain the concept of DC load line and operating point for biasing circuit.
  - (c) Describe the action of zener voltage regulator with neat diagram. Write any two limitations of unregulated power supply.
- 2. Attempt any FOUR :** **16**
- (a) List the types of biasing method of transistor. Explain any one method.
  - (b) What is thermal runaway ? How it can be avoided ?
  - (c) Sketch the drain characteristics of N-channel JFET for various values of  $V_{GS}$ . State the condition at which the drain current essentially becomes constant.
  - (d) Draw and explain the input and output characteristics of CE configuration.
  - (e) List different types of negative feedback. Draw their diagrams.
  - (f) Explain the block diagram of regulated power supply and also state its need.
- 3. Attempt any FOUR :** **16**
- (a) Compare CB,CC & CE configurations (any 4 points).
  - (b) With the help of neat circuit diagram explain the working of self bias method for FET.
  - (c) Draw and explain the working of miller sweep generator.
  - (d) Describe how excellent impedance matching is achieved with transformer coupling.
  - (e) State load and line regulation.
  - (f) Draw the dual power supply capable of giving  $\pm 12$  V using three terminal regulator IC's and describe its working.

**4. Attempt any FOUR :****16**

- (a) Explain the construction and working of N-channel JFET.
- (b) Draw the circuit diagram and frequency response of two stage RC coupled amplifier.
- (c) Differentiate the MOSFET and FET for the following points :
  - (i) Schematic symbol
  - (ii) Trans conductance curve
  - (iii) Modes of operation
  - (iv) Input impedance
- (d) Compare the small signal amplifier and power amplifier w.r. to following points :
  - (i) Input voltage
  - (ii) output power
  - (iii) output impedance
  - (iv) Applications
- (e) Sketch the output waveforms of class A, class AB and class C with respect to operating point on load line.
- (f) Draw V-I characteristics of UJT. State any two applications of UJT.

**P.T.O.**

**5. Attempt any FOUR :****16**

- (a) Derive relation between  $\alpha$  &  $\beta$  with respect to BJT.
- (b) The phase shift oscillator uses equal resistances of  $1\text{ M}\Omega$  & equal capacitances of  $68\text{ PF}$ . At what frequency does the circuit oscillate ? And also find value of resistance to produce a frequency of  $800\text{ kHz}$  if phase shift oscillator uses  $5\text{ PF}$  capacitor.
- (c) Explain the working of class-B push-pull amplifier.
- (d) Explain with neat sketch how FET can be used as an amplifier.
- (e) State Barkhausen criterion of oscillation.
- (f) Draw the functional block diagram of IC 723. State any two features of 723.

**6. Attempt any FOUR :****16**

- (a) Discuss steps to be taken to design transistor biasing and stabilizing circuit.
  - (b) Draw circuit diagram of transistorised series voltage regulator and explain its working.
  - (c) State the meaning of positive and negative feedback with neat sketch.
  - (d) Plot frequency response of doubled tuned amplifier and explain it.
  - (e) The ac equivalent circuit of crystal has these values  $L = 1\text{H}$ ,  $C = 0.01\text{ PF}$ ,  $R = 1000\ \Omega$  &  $C_m = 20\text{ PF}$ . Determine the series resonant and parallel resonant frequencies.
  - (f) Draw circuit diagram & waveforms of voltage sweep generator using UJT.
-