

# 17353

**16172**

**3 Hours / 100 Marks**

Seat No.

--	--	--	--	--	--	--	--

- Instructions* – (1) All Questions are *Compulsory*.  
(2) Answer each Section on separate answer sheet.  
(3) Answer each next main Question on a new page.  
(4) Figures to the right indicate full marks.  
(5) Assume suitable data, if necessary.  
(6) Use of Non-programmable Electronic Pocket Calculator is permissible.  
(7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

**SECTION - I**

- 1. Attempt any SEVEN of the following: **14****
- Define:
    - Time period
    - Frequency
  - List any four wiring accessories.
  - State the relation between line voltage and phase voltage in 3 $\phi$  STAR connection.
  - Write working principle of PMMC meter.
  - Define regulation of transformer.
  - State the working principle of electric welding.

P.T.O.

- g) State any two factors which is to be considered for selecting the motor for electrical drives.
- h) Give two applications of single phase induction motor.
- i) List different types of enclosers.
- j) Define slip in case of induction motor.

**2. Attempt any FOUR of the following: 12**


- a) Explain the concept of energy conservation.
- b) Explain working principle of transformer.
- c) Explain with neat diagram the working principle of MI instrument.
- d) Explain with one example the necessity of earthing.
- e) Name the different methods of power factor improvement.
- f) Compare between AC and DC power supply.

**3. Attempt any FOUR of the following: 12**

- a) Explain operating principle of Auto Transformer.
- b) Draw neat diagram of STAR-DELTA starter.
- c) Give the advantages of AC supply over DC supply.
- d) Explain working principle of Electroplating.
- e) Draw labeled diagram of 1-phase energy meter.
- f) Explain working of capacitor RUN induction motor.

**4. Attempt any FOUR of the following: 12**

- a) For the R-L circuit shown in Figure No. 1 find value of impedance, current and power factor.

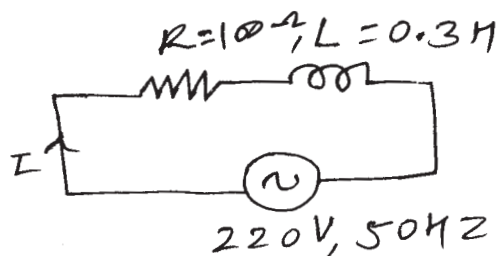

**Fig. No. 1**

- b) In STAR connected circuit if supply voltage is 415V, 50Hz and phase resistance and inductor are of  $25\Omega$  and 0.1 Henry. Calculate line current, phase current and phase impedance.
- c) Draw wiring diagram for 2 switches and 2 fans used for residential purpose.
- d) Name the different types of welding techniques and given any two applications.
- e) Describe emf equation for transformer.
- f) State three applications of electrical machines used in agrosystem.

### SECTION - II

**5. Attempt any NINE of the following: 18**

- a) Define inductance and resistance.
- b) Define Doping.
- c) Draw symbol for P-N junction diode and zener diode.
- d) Define semiconductors and name two intrinsic semiconductor.
- e) Write two applications of SCR.
- f) Draw the symbol of NAND gate.
- g) Why NAND and NOR gates known as universal gates?
- h) Give the statement for Demozgan's first and second theorem.
- i) List different types of display.
- j) Define filter.
- k) Name the different types of rectifiers.
- l) Give two applications of LED.
- m) State the need of voltage regulator.

- 6. Attempt any FOUR of the following:** **16**
- a) Compare between NPN and PNP transistor.
  - b) Draw the circuit diagram of half wave rectifier and explain its working.
  - c) Draw construction of SCR and explain its working principle.
  - d) Implement OR and AND gate using NAND gate only.
  - e) Draw the circuit diagram of single stage CE amplifier and explain its working.
  - f) Draw and explain Pi ( $\pi$ ) filter.
- 7. Attempt any FOUR of the following:** **16**
- a) Draw energy band diagram for conductors semi conductor and insulator.
  - b) Draw symbol and truth table for Ex-NOR gate.
  - c) State any four applications of TRIAC.
  - d) Draw and explain zener diode characteristics.
  - e) Explain the operation of NPN transistor.
  - f) Draw the block diagram for the regulated power supply and explain the working of each block.
-