

17584

16172

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.

Marks

1. (A) Attempt any SIX :

12

- (a) Draw neat symbol of SCR, DIAC, TRIAC, GTO.
- (b) Give detail classification of inverter.
- (c) Explain necessity of choppers and its working principle.
- (d) List any two applications of converters.
- (e) Explain concept of harmonics. Also explain sources and effects of harmonics.
- (f) Draw labelled characteristics of TRIAC.
- (g) Name the devices used to suppress spikes in supply voltage. (Any two)
- (h) Draw neat circuit diagram of single phase fully controlled bridge converter with free wheeling diode.

- (B) Attempt any ONE :** **6**
- (a) Draw neat circuit of single phase. Cycloconverter and explain its working with neat input & output waveforms.
 - (b) List different triggering methods of SCR. Explain any one method with circuit.
- 2. Attempt any FOUR :** **16**
- (a) Draw neat circuit of stepup chopper. Explain its operation with neat waveforms.
 - (b) With the help of neat circuit diagram and waveforms, explain working of single phase fully controlled half wave converter with R load.
 - (c) Draw circuit of line (Natural) commuted inverter and explain its working.
 - (d) Draw two transistor analogy of SCR and derive anode current equation.
 - (e) Draw neat circuit diagram and waveform of three phase fully controlled bridge. Converter with R load.
 - (f) Draw neat symbol and labelled characteristics of LASCR & IGBT.
- 3. Attempt any FOUR :** **16**
- (a) Explain working of parallel inverter with neat circuit diagram.
 - (b) Explain effect of source impedance on converter operation.
 - (c) Draw circuit of AC phase control using triac with diac as triggering device and explain its operation.
 - (d) Draw circuit of battery charger using SCR's and explain its working.
 - (e) Draw block diagram of SMPS and explain working of each block.

- (f) Draw labelled characteristics of SCR and define.
- (i) Holding current
 - (ii) Latching current

4. Attempt any THREE :

18

- (a) Draw neat circuit of single phase fully controlled bridge converter with RL load and explain its working with necessary waveforms.
- (b) Draw block diagram of OFF line UPS and ON line UPS and explain the working of them.
- (c) Explain working of basic series inverter with neat circuit diagram. Also draw circuit diagram of modified series inverter.
- (d) List different methods of commutation of choppers and explain any one method with neat circuit diagram.

5. Attempt any FOUR :

16

- (a) List different methods of output voltage control of single phase inverter. Explain any one method in detail.
- (b) Compare single phase and three phase converter on the basis of
 - (i) Efficiency
 - (ii) Ripple factor
 - (iii) RMS value
 - (iv) Average value
- (c) Define commutation of SCR. Explain any one type of commutation method of SCR with neat circuit diagram.

P.T.O.

- (d) Give classification of chopper. Explain class A chopper with neat circuit.
- (e) Draw circuit diagram of static DC circuit breaker and explain its working.
- (f) Explain deviation in quality of power supply with respect to waveform, frequency, current and voltage level.

6. Attempt any FOUR :

16

- (a) Draw neat circuit of three phase inverter & explain its working.
 - (b) Draw circuit of single phase full wave controlled converter with R load and explain its working.
 - (c) With the help of neat circuit diagram and waveforms, explain the operation of step down chopper.
 - (d) Explain basic principles of SMPS and UPS.
 - (e) Compare MOSFET based inverters and thyristor based inverters. (any four points)
 - (f) Draw neat circuit diagram of Induction heating control and dielectric heating control using SCR's.
-