

17667

16172

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.
 - (8) Use of steam tables, logarithmic, Mollier's chart is permitted.

Marks

1. (A) Attempt any THREE :

12

- (a) Draw and explain the block diagram of electric drive.
- (b) State the need of electric drives.
- (c) State eight functions of microprocessor in drive technology.
- (d) Draw and explain the operation of single phase semi-converter drive with waveforms.

(B) Attempt any ONE :

6

- (a) Explain the 4 quadrant operation of a drive.
- (b) Compare semiconverter drives and full converter drives on the basis of
 - (i) Quadrant of operation
 - (ii) Regenerative braking
 - (iii) Power flow
 - (iv) Harmonic contents
 - (v) Peak motor current
 - (vi) Motor heating

2. Attempt any FOUR :**16**

- (a) State the factors to be considered for the selection of a drive.
- (b) State the requirements and the type of drives used in sugar mills.
- (c) Draw and explain a dc chopper using MOSFET.
- (d) State four advantages of converter fed induction motors.
- (e) Draw the block diagram and explain V/f control using square wave inverter.
- (f) Draw and explain a 2 quadrant chopper drive.

3. Attempt any FOUR :**16**

- (a) State the types of electric braking and state 2 advantages of electric braking.
- (b) State the stages involved in textile mills and the type of drives used for it.
- (c) Draw the circuit for three phase dual converter.
- (d) Draw and explain the operation of a chopper circuit used for reversible drive.
- (e) Draw and explain the operation of multiphase chopper drive.

4. (A) Attempt any THREE :**12**

- (a) Draw the circuit of a three phase semiconverter drive. State the equation of average armature voltage.
- (b) State the methods of speed control of Induction Motor.
- (c) Draw and explain PLL control of dc motor.
- (d) Draw and explain stepper motor control using microcontroller.

(B) Attempt any ONE :

6

- (a) State the different stages in paper mill and the type of drive used for it.
- (b) State different stages in steel rolling mills and the type of drive used for it.

5. Attempt any FOUR :

16

- (a) A 4 pole, 1440 rpm 3 ϕ I/M is operated from per phase voltage of 240 V, 50 Hz and driving a constant torque load. Calculate the following at frequency of 25 Hz, $\phi_{ag} = 4.8$: (i) supply voltage/phase, (ii) slip, (iii) slip frequency, (iv) slip at 25 Hz.
- (b) A semiconverter operated from 1 ϕ 230 V, 50 Hz supply drives a 10 H.P, 200 V, 1500 rpm separately excited dc motor. Rated armature current is 40 A, motor parameter are $R_a = 0.5 \Omega$, $L_a = 10 \text{ mH}$, $K_a \phi_{\text{constant}} = 0.2 \text{ V/rpm}$. Find the following for $\alpha = 30^\circ$
 - (i) average armature voltage
 - (ii) speed of the motor
- (c) Draw the block diagram and explain the working of PWM control of I/M.
- (d) List different requirements of motors used for machine tools.
- (e) State the types of SCR controlled drives. State 4 advantages of converter controlled drives.
- (f) Draw and explain microprocessor based control of synchronous motor.

P.T.O.

6. Attempt any FOUR :**16**

- (a) Draw the block diagram of microprocessor based control of dc motor.
 - (b) State eight advantages of microprocessor based control of drives.
 - (c) Draw the block diagram and explain the working of motor resistance control using chopper.
 - (d) Draw the characteristics of dc shunt and series motor.
 - (e) Draw the block diagram and working of closed loop control of synchronous motor.
-