



# 17319

15116

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

*Instruction : All questions are compulsory.*

**Marks**

1. A) Attempt **any six** : **12**
- Draw the symbols of NPN and PNP BJT.
  - State two advantages of voltage divider biasing technique.
  - State two applications of direct coupling method used in multistage amplifiers.
  - Draw the symbols enhancement p type and enhancement n type MOSFET.
  - Sketch the circuit diagram of single tuned amplifier.
  - State the maximum efficiency of class A power amplifier.
  - State two advantages of JFET over BJT.
  - Define intrinsic stand-off ratio  $\eta$  of UJT.
- B) Attempt **any two** : **8**
- Compare CB, CE and CC with respect to input impedance, output impedance, current gain and voltage gain. Give typical figures of each parameter.
  - Draw the circuit diagram and explain the operation of fixed biasing circuit used in BJT. State its advantages and disadvantages.
  - With the help of neat circuit diagram and V-I characteristics explain the working of zener diode as voltage regulator.
2. Attempt **any four** : **16**
- Explain the concept of DC load line used in BJT amplifier.
  - Draw the circuit diagram of voltage divider biasing circuit used with BJT CE amplifier and explain its operation.
  - Draw the constructional sketch of n channel JFET and explain its working principle.
  - With neat circuit and waveform diagrams explain how BJT works as switch.
  - Draw the block diagrams of current series and current shunt feed-back.
  - Draw the block diagram of DC regulated power supply and state the function of each block.
3. Attempt **any four** : **16**
- Draw the input and output characteristics of CE configuration and label it.
  - With neat circuit diagram and mathematical expressions explain the self biasing used in FET.

**P.T.O.**



- c) Draw the circuit diagram and explain the working principle of UJT relaxation oscillator.
- d) Draw the circuit diagram and frequency response of two stage RC coupled amplifier and explain its operation. State its important applications.
- e) Draw the high voltage regulator using IC 723 and explain its operation.
- f) Draw the circuit diagram of transistorized series voltage regulator and explain its working. State its advantages and disadvantages.

**4. Attempt any four :****16**

- a) Draw the drain characteristics and transfer characteristics of JFET.
- b) How BJT can be used as an amplifier ? Explain.
- c) Compare Miller integrator and bootstrap sweep generator with respect to the technique used.
- d) Compare small signal amplifier and power amplifier (any 4 points).
- e) Draw the circuit diagram of class-B push-pull amplifier and explain its operation. State its important applications.
- f) With neat sketch explain working principle of enhancement type MOSFET. State its important applications.

**5. Attempt any four :****16**

- a) Define  $\alpha$ ,  $\beta$  and  $\gamma$  w.r.t. BJT. Derive the relation between  $\alpha$  and  $\beta$ .
- b) State the working principle of crystal oscillator and list its two applications.
- c) Compare class A, class B and class AB power amplifiers (any four points).
- d) Draw the circuit diagram common source FET amplifier and explain its working principle. State its applications.
- e) Draw the circuit diagram of Miller crystal oscillator and explain its operation. State advantages and disadvantages of crystal oscillator.
- f) Draw the pin diagram of IC 78XX and IC 79XX and state their features and advantages.

**6. Attempt any four :****16**

- a) What do you understand by stabilization of operating point ? Explain the need for stabilization.
  - b) Draw the diagram transistorized shunt regulator and explain its working.
  - c) Compare positive feedback and negative feedback (any four points).
  - d) Compare single tuned amplifier and double tuned amplifier w.r.t. circuit diagram and frequency response.
  - e) What do you mean by an oscillator ? State Barkhausen's criteria required for oscillations. State important applications of oscillator.
  - f) Draw the constructional sketch and equivalent circuit of UJT and explain its V-I characteristics.
-