

17215

21718

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Illustrate your answers with neat sketches wherever necessary.
 - (3) Figures to the right indicate full marks.
 - (4) Assume suitable data, if necessary.
 - (5) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any TEN :

20

- (a) Write colour code of 1 k Ω resistor.
- (b) Draw the symbol of (i) zener diode, (ii) Schottky diode, (iii) LED, (iv) Tunnel diode.
- (c) List the two advantages of Bridge Rectifier.
- (d) List any four applications of laser diode.
- (e) State different types of filters.
- (f) Define clipper. Draw circuit of negative shunt clipper.
- (g) Define linear and non-linear wave-shaping circuit.
- (h) Draw an ideal current source and practical current source.
- (i) List any two applications of Schottkey diode.
- (j) Define self-inductance and mutual inductance.
- (k) State the necessity of wave-shaping circuit.
- (l) State Kirchoff's current law along with its formulae.
- (m) State superposition theorem.
- (n) List any two applications of photo diode and IRLED (each).

[1 of 4]

P.T.O.

2. Attempt any FOUR :

4 × 4 = 16

- (a) Draw circuit diagram and waveforms for centre-tap full wave rectifier.
- (b) Describe working of negative clamper circuit with neat diagram and waveform.
- (c) Describe the operating principle of LASER diode with diagram.
- (d) By using Maxwell’s loop current method, calculate current in 4 W resistance for the network shown in figure no. 1.

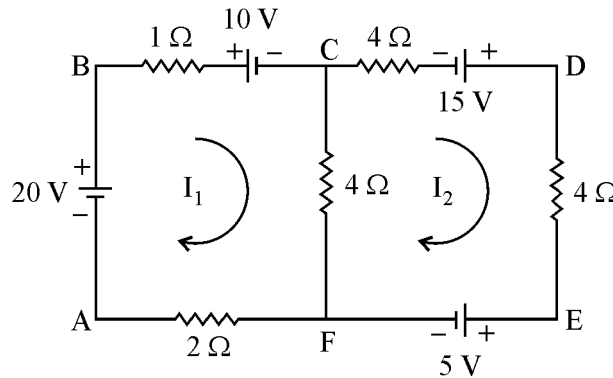


Fig. 1

- (e) Draw and explain B-H curve.
- (f) Define static and dynamic resistance of diode.

3. Attempt any FOUR :

4 × 4 = 16

- (a) With the help of circuit diagram and waveforms, explain working of RC differentiator.
- (b) State the advantages of L and C filter. (four points)
- (c) Describe avalanche and zener breakdown of PN junction with neat graph.
- (d) Calculate current flowing through 6 Ω resistor using KVL (refer fig. 2)

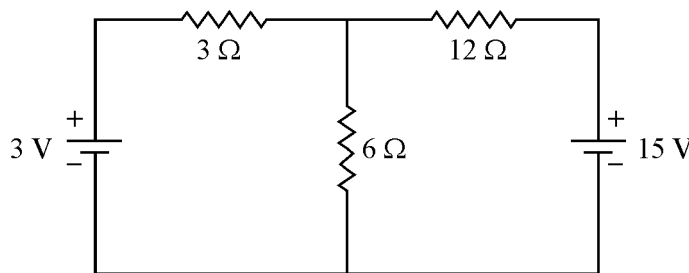


Fig. 2

- (e) Draw and describe construction of LED.
- (f) Define given parameters and state their values for bridge rectifier (i) Ripple factor (ii) PIV of diode.

4. Attempt any FOUR :

4 × 4 = 16

- (a) Write down the colour code for following resistor :
- (i) $150 \Omega \pm 5\%$ (ii) $3.3 \text{ k}\Omega \pm 20\%$
- (b) Describe working of variable air gang capacitor with neat sketch.
- (c) Describe the working of PN junction diode with neat sketch under forward biased condition.
- (d) Compare soft magnetic materials and hard magnetic materials. (four points)
- (e) In bridge rectifier load resistance $R_L = 2 \text{ kW}$. The diode has forward dynamic resistance of 10 W . The AC voltage across the secondary winding of transformer is $V = 50 \sin 413 \text{ tV}$. Determine : (i) Peak current (ii) DC value of current (iii) PIV of diode (iv) DC voltage
- (f) Using Thevenin's theorem find load current I_L (refer figure 3)

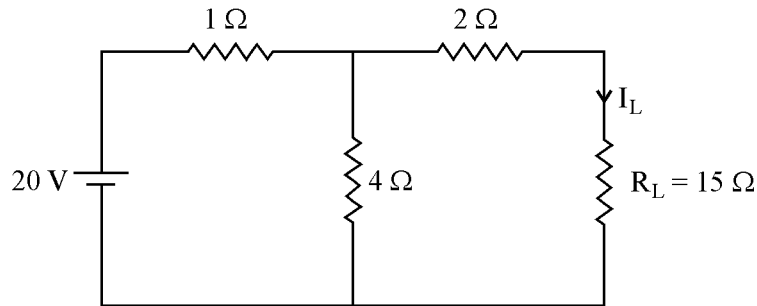


Fig. 3

5. Attempt any FOUR :

4 × 4 = 16

- (a) With help of circuit diagram & waveform, explain working of CLC or π filter.
- (b) Identify the following circuit. Draw its input / output waveforms. (refer figure 4)

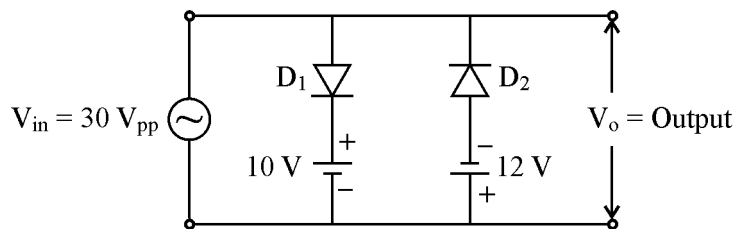


Fig. 4

- (c) Compare HWR and FWR. (four points)
- (d) State Maximum Power Transfer Theorem.

P.T.O.

- (e) Calculate the value of current in $10\ \Omega$ resistor using Norton's Theorem. (refer fig. 5)

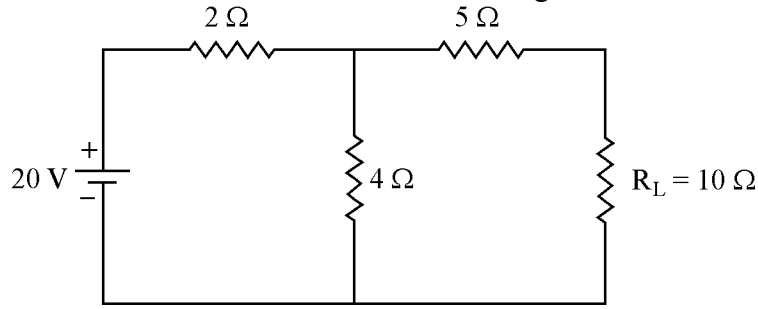


Fig. 5

- (f) Compare linear and logarithmic potentiometer.

6. Attempt any FOUR :

$4 \times 4 = 16$

- (a) Calculate value of capacitor if following is printed on body of capacitors :
(i) 404 (ii) 2K3.
- (b) Describe the working of tunnel diode. Draw its characteristics.
- (c) With the help of constructional diagram, explain the working of LDR with neat sketch.
- (d) Explain with neat circuit, concept of open circuit and short circuit.
- (e) Calculate equivalent resistance, R_{AB} between terminals A & B using delta-star transformation. (refer fig. 6)

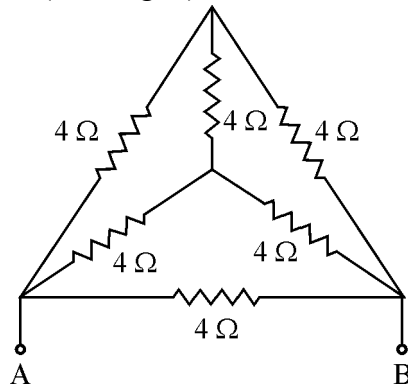


Fig. 6

- (f) Find current through resistance R_4 using super-position theorem. (refer fig. 7)

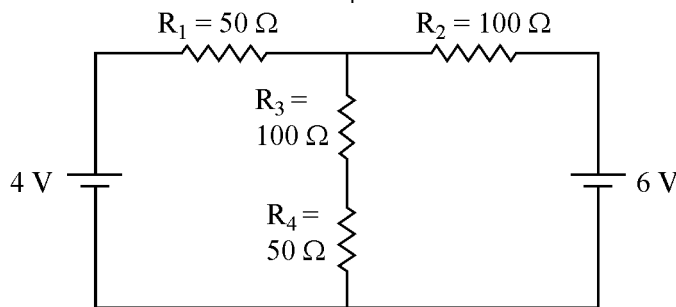


Fig. 7