

# 17323

11718

**3 Hours / 100 Marks**

Seat No.

--	--	--	--	--	--	--	--


- Instructions* – (1) All Questions are *Compulsory*.
- (2) Illustrate your answers with neat sketches wherever necessary.
- (3) Figures to the right indicate full marks.
- (4) Assume suitable data, if necessary.
- (5) Use of Non-programmable Electronic Pocket Calculator is permissible.

**Marks**

1. **Attempt any TEN of the following:** **20**
- Define cycle and time period related to a.c. waveform.
  - Define active power and reactive power for R-L-C series circuit.
  - Draw impedance triangle and voltage phasor diagram for R-L series circuit.
  - Define susceptance and admittances for a parallel circuit.
  - State superposition theorem applied to D.C. circuits.
  - State maximum power transfer theorem for D.C. circuits.
  - Write down the units of R, L, C and G.
  - Define quality factor of series A.C. circuit.
  - How current source can be converted into equivalent voltage source?
  - Draw the sinusoidal waveform of 3 phase emf and also indicate the phase sequence.

P.T.O.

- k) Find frequency and RMS value of the following voltage waveform Refer Figure No. 1

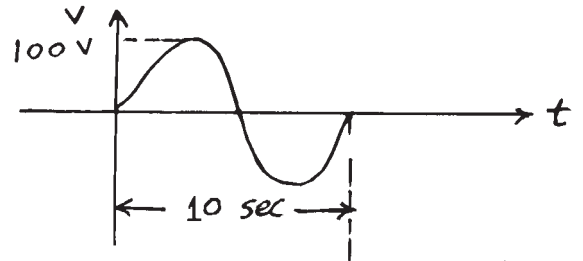

**Fig. No. 1**

- l) State the behaviour of following elements at the time of switching i.e. transient period:
- (i) Pure L
  - (ii) Pure C

**2. Attempt any FOUR of the following:**

**16**

- a) Draw waveform and vector diagram to show following voltage and current.  $V = 100 \sin \omega t$ . and  $i = 4 \sin(\omega t - 30^\circ)$
- b) Compare series and parallel circuits on any six points.
- c) An alternating voltages of 250 V, 50 Hz is applied to a coil which takes 5A of current the power absorbed by the circuit is 1kW. Find the resistance and inductance of the coil.
- d) Derive the expression for resonance frequency for a R-L-C series circuit.
- e) Draw the phasor diagram and waveforms of voltage, current and power in a pure inductance circuit supplied by a 1-phase a.c. source.
- f) Compare series and parallel circuit.


**3. Attempt any FOUR of the following:****16**

- a) A choke coil has a resistance of  $2\Omega$  and an inductance of  $0.035\text{H}$  is connected in parallel with a  $350\mu\text{F}$  capacitor which is in series with a resistance of  $20\Omega$ . When the combination is connected across a  $200\text{ V}$ ,  $50\text{Hz}$  supply. Calculate:
- The total current taken and
  - Power factor of whole circuit.
- b) A coil having resistance of  $5\Omega$  and inductance of  $0.2\text{H}$  is arranged in parallel with another coil having resistance of  $1\Omega$  and inductance of  $0.08\text{H}$ . Calculate the current through the combination and power absorbed when a voltages of  $100\text{ V}$ ,  $50\text{ Hz}$  is applied. Use impedance method.
- c) Define the following terms:
- Leading quantity
  - Lagging quantity
- d) A RC series circuit consisting of  $R = 10\Omega$  and  $C = 100\mu\text{F}$  is connected across  $200\text{V}$ ,  $50\text{Hz}$  AC supply. Find the value of current and power factor. What will be the value of current and power factor if the value of resistance is doubled?
- e) A  $200\text{ W}$ ,  $100\text{ V}$  lamp is connected in series with a capacitor to a  $120\text{ V}$ ,  $50\text{ Hz}$  a.c. supply calculate:
- the capacitance required
  - the phase angle between voltage and current.
- f) State the relation between line and phase values of current and voltage for star and delta connection.

4. Attempt any FOUR of the following:

16

- Three coils each with a resistance of  $10\ \Omega$  and inductance of  $0.35\text{mH}$  are connected in star to a 3-phase,  $440\ \text{V}$ ,  $50\ \text{Hz}$  supply. Calculate the line current and total power taken per phase.
- State any four advantages of polyphase circuit over single phase circuit.
- Derive the formulae for star and delta transformation.
- A delta connected induction motor is supplied by 3-phase,  $400\text{V}$ ,  $50\text{Hz}$  supply the line current is  $43.3\text{A}$  and the total power taken from the supply is  $24\ \text{KW}$ . Find the resistance and reactance per phase of motor winding.
- Using mesh analysis find values of  $R_1$  and  $R_2$  shown in Figure No. 2

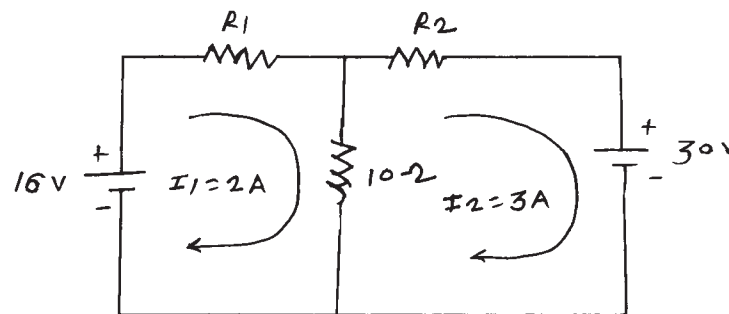

**Fig. No. 2**


- Derive the condition for maximum power transfer theorem.

5. Attempt any TWO of the following:

16

- A coil of resistance  $50\ \Omega$  and inductance of  $0.1\ \text{H}$  is connected in series with  $100\ \mu\text{F}$  capacitor. The combination is supplied with  $230\ \text{V}$ ,  $50\ \text{Hz}$  A.C. supply. Calculate voltage across each, current through the circuit, power factor and draw complete vector diagram.
- With the help of necessary phasor diagram, derive the relationship between line and phase current in balanced delta connected load connected to 3 phase A.C. supply.


- c) (i) State Thevenin's theorem and write its procedural steps to find current in a branch. (Assume simple circuit)
- (ii) Develop Thevenin's equivalent across A and B in network shown below in Figure No. 3

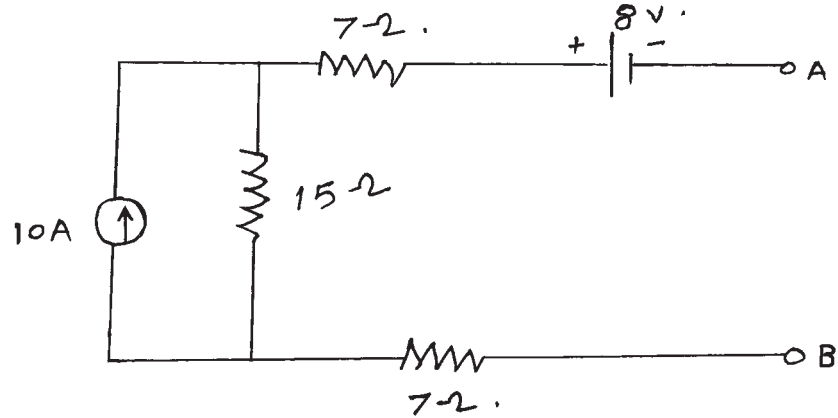

**Fig. No. 3**

6. Attempt any FOUR of the following: 16

- a) Calculate current through  $10\ \Omega$  resistance in the network shown in Figure No. 4 using superposition theorem.

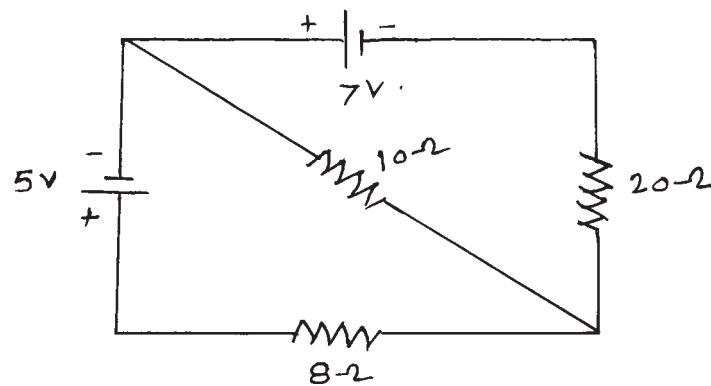

**Fig. No. 4**

- b) Using Norton's theorem. Find current through  $4\ \Omega$  resistance in Figure No. 5.

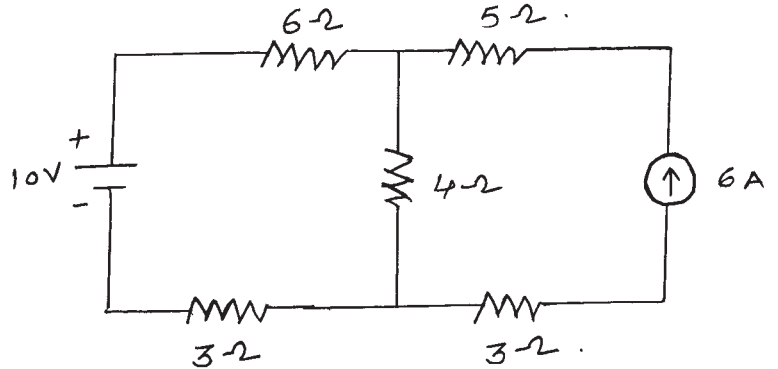


Fig. No. 5

- c) Find current through  $8\ \Omega$  resistance using nodal analysis in Figure No. 6

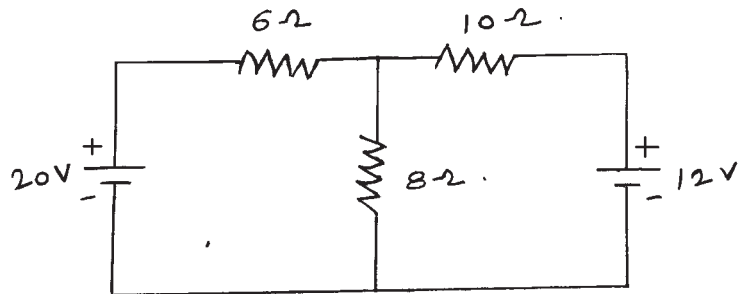


Fig. No. 6

- d) Find the value of  $R_L$  to transfer maximum power in the network shown in Figure No. 7

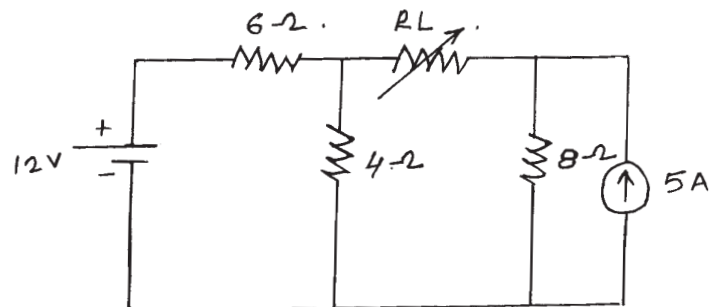


Fig. No. 7

- e) Explain concept of initial and final conditions in switching circuits. For the elements R, L and C.
- f) Give the expression for star to delta and delta to star transformation.