

17667

11718

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Illustrate your answers with neat sketches wherever necessary.
 - (3) Figures to the right indicate full marks.
 - (4) Assume suitable data, if necessary.

Marks

1. (A) Attempt any THREE : 12

- (a) State the need of adjustable speed drives.
- (b) List advantages of electrical braking system.
- (c) Draw the block diagram of phase locked loop control of D.C. motor.
- (d) Draw circuit diagram of single-phase semi-converter and draw its voltage and current waveforms.

(B) Attempt any ONE : 6

- (a) Explain with diagram four quadrant operation of a motor driving hoist.
- (b) Compare between single phase and three phase drives on the basis of following factors :
 - (i) Value of ripple frequency
 - (ii) Motor current
 - (iii) Motor performance
 - (iv) Use for large horsepower drives
 - (v) Cost of drives
 - (vi) Harmonic contents and motor heating

2. Attempt any FOUR:**16**

- (a) Explain starting of electric motors. State different methods of starting of electric motors.
- (b) With suitable block diagram describe role of drives in different sections of Hot Rolling Mill.
- (c) Draw circuit diagram of D.C. chopper using power MOSFET and explain its operation briefly.
- (d) State the advantages of converter fed induction motors over direct line fed motors.
- (e) With neat block diagram explain working of PWM control of induction motor.
- (f) With neat circuit describe the working of two quadrant class B chopper drive.

3. Attempt any FOUR :**16**

- (a) Describe the operation of four-quadrant transistorized chopper drive with circuit diagram.
- (b) Explain the working of multi-phase chopper drives with circuit and waveforms.
- (c) Draw circuit of 3-phase full converter drive for the D.C. motor.
- (d) Compare D.C. shunt & D.C. series motors.
- (e) Compare A.C. drives and D.C. drives on the basis of any four valid points.

4. (A) Attempt any THREE :**12**

- (a) With circuit diagram and waveforms explain working of single phase full wave converter.
- (b) Explain with diagram operation of stator voltage control method of speed control of induction motor.
- (c) With block diagram explain operation of stepper motor drive employing micro-controller.
- (d) State the drawback or limitations of conventional motor speed control methods as compared to micro-controller based system.

(B) Attempt any ONE :**6**

- (a) Explain speed control methods of induction motor using chopper controlled resistance in rotor circuit.
- (b) In paper mill, describe the drives required for making pulp from raw material and for converting pulp into paper.

5. Attempt any FOUR :**16**

- (a) A semiconverter operated from single phase 230 V, 50 Hz supply drives 10 HP motor at 200 V running with speed 1500 RPM, separately excited d.c. motor. The rated armature current is 40 A. The motor has $R_a = 0.5 \Omega$ & $L_a = 10 \text{ mH}$ $K_a \phi = 0.2 \text{ V/rpm}$. Find out the following at $\alpha = 30^\circ$
 - (i) Average armature voltage (ii) Buck emf of motor (iii) speed of motor (iv) motor torque.
- (b) Compare between stator voltage control method and rotor resistance control method of speed control methods of induction motor.

P.T.O.

- (c) Draw block diagram & explain marking of closed loop control of synchronous motors.
- (d) Describe requirement of drives for sugar mill.
- (e) State the method of braking of electric motors.
- (f) Explain frequency control method to control the speed of induction motor.

6. Attempt any FOUR :

16

- (a) State advantages of microcontroller / microprocessor based control for drives over conventional methods.
 - (b) Which type of drive motor is suitable for machine tool application ?
 - (c) Write different eight stages involved in textile mill and requirement of speed at each stage.
 - (d) What factors are considered for selection of drive for particular application ?
 - (e) State importance of phase failure protection in three phase drives.
-