



17329

16117

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :** (1) *All questions are compulsory.*
(2) *Attempt all questions including question No.1 which is compulsory.*
(3) *Answer each Section on separate answer sheet.*
(4) *Answer each next main question on a new page.*
(5) *Illustrate your answers with neat sketches wherever necessary.*
(6) *Figures to the right indicate full marks.*
(7) *Assume suitable data, if necessary.*
(8) *Use of Non-programmable Electronic Pocket Calculator is permissible.*

Marks

SECTION – I

1. Attempt **any nine** of the following :

18

- Define average and r.m.s. value of alternating quantity.
- Define power and energy with their unit.
- State the relation between line current and phase current in star and delta connected circuit.
- List any two applications of transformer.
- Draw speed torque characteristics of 3 phase induction motor.
- State classification of fuses.
- State necessity of earthing.
- State expression for active power, reactive power and apparent power for three phase circuit.
- Define transformation ratio and KVA rating of single phase transformer.
- State type of single phase induction motor used in following application.
 - Food mixer
 - Refrigerator.
- State the function of term :
 - MCCB
 - ELCB.
- State advantages of three phase circuit.

P.T.O.



2. Attempt **any four** of the following :

16

- a) Describe two different types of enclosures.
- b) State applications of sodium vapour lamps.
- c) Compare capacitor start induction motor and universal motor.
- d) Define efficiency, voltage regulation of transformer. Two transformer A and B have voltage regulation of 5% and 10% respectively. Which transformer is better and why ?
- e) Three identical coils each of $R = 4 \Omega$ and $C = 100 \mu F$ connected in star across 415V, 3 ϕ , 50Hz supply. Calculate V_{ph} , I_{ph} , power factor, total power absorbed.
- f) Define frequency, phase, maximum value of alternating quantity.

3. Attempt **any four** of the following :

16

- a) State first aid measure to be given to person who has received electric shock.
- b) Explain with block diagram speed control of induction motor by variable frequency drive method.
- c) Draw circuit diagram of direct on line starter.
- d) What are different types of safety tools used in electrical ?
- e) i) Draw neat labelled diagram for single phase transformer.
ii) Write the e.m.f. equation of transformer and state the meaning of each term in it also state their units.
- f) Describe the concept of 3-phase transformer and auto transformer.

SECTION – II

4. Attempt **any four** of the following :

16

- a) Draw symbols of FET, BJT, photodiode and optocoupler.
- b) Draw block diagram of regulated power supply. State function of each block.
- c) State Barkhausen's criteria of oscillations. List different types of oscillators.
- d) What is rectifier ? Describe the working of half wave rectifier with circuit diagram and waveforms.



e) Compare CB, CE and CC configuration (4pts).

f) Draw the symbols of following gates :

i) AND

ii) OR

iii) NDT

iv) XOR

5. Attempt any three of the following :

18

a) Compare

i) BJT with FET (3pts)

ii) Define intrinsic and extrinsic semiconductors.

b) Draw and explain circuit of full wave bridge rectifier with C filter and draw its input and output waveforms.

c) Draw the block diagram of OP-AMP and explain each block of it.

d) What is universal gate ? Design basic gates using NAND universal gate.

6. Attempt any four of the following :

16

a) Describe the working of zener diode as a voltage regulator.

b) Explain working principle of PN junction diode in forward and reverse bias condition.

c) Draw and explain working of crystal oscillator.

d) Convert the following :

i) $(32)_{10} = (?)_2$

ii) $(99)_{BCD} = (?)_2$

e) Draw circuit diagram of RC coupled amplifier and show its frequency response with proper notations.

f) Draw symbols and truth table of :

i) NDR gate

ii) NAND gate.
