

17444

16117

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* – (1) All Questions are *Compulsory*.
- (2) Answer each next main Question on a new page.
- (3) Illustrate your answers with neat sketches wherever necessary.
- (4) Figures to the right indicate full marks.
- (5) Use of Non-programmable Electronic Pocket Calculator is permissible.
- (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. a) **Attempt any SIX of the following:**

12

- (i) Draw symbols of SCS and SUS.
- (ii) State any two advantages of power MOSFET.
- (iii) Define holding current (I_H) and Latching current (I_L) of SCR.
- (iv) Give classification of Inverter.
- (v) State the importance of pulse transformer in triggering circuit.
- (vi) List any two applications of chopper.
- (vii) State the need of Polyphase Rectifier.
- (viii) Draw circuit diagram of light dimmer using DIAC-TRIAC.

P.T.O.

b) **Attempt any TWO of the following:**

8

- (i) Compare single phase half wave and three phase half wave uncontrolled Rectifiers based on.
 - 1) No. of diodes
 - 2) Output power
 - 3) Ripple present in output
 - 4) Output voltage waveform
- (ii) Define four performance parameters of an inverter.
- (iii) With the help of neat diagram explain operation of temperature controller using SCR.

2. **Attempt any FOUR of the following:**

16

- a) Describe working of single phase centre tapped full wave controlled Rectifier with Resistive load.
- b) With the help of circuit diagram and waveforms explain step down chopper using power MOSFET.
- c) Draw block diagram of UPS. Explain each block in detail.
- d) Draw VI characteristics of SCR. State the effect of increasing gate current of SCR.
- e) What are different Turn ON methods of SCR? Explain dv/dt triggering.
- f) Describe working of single phase half bridge inverter with help of neat circuit diagram and waveforms.

3. **Attempt any FOUR of the following:**

16

- a) Compare UJT and DIAC w.r.t.
 - (i) symbol
 - (ii) layer diagram
 - (iii) operating quadrant
 - (iv) application

- b) Draw circuit diagram, input and output waveforms for single phase half controlled Rectifier with RL load.
- c) Define following w.r.t. GTO.
 - (i) Maximum controllable Anode current
 - (ii) Turn off gain.
- d) Draw neat labeled characteristics of power transistor. Show its regions.
- e) Define firing angle (α) and conduction angle (θ). State effect of changing firing angle (α) on output voltage of Rectifier.
- f) A single phase full wave controlled Rectifier is supplied with a voltage $V_S = 300 \sin (314 t)$. Find average output voltage and current if firing angle is 60° and load resistance is 500Ω .

4. Attempt any FOUR of the following:

16

- a) With the help of circuit diagram and waveform explain set-up chopper.
- b) Explain four modes of operation of TRIAC with neat constructional diagram.
- c) Draw block diagram of SMPS. State its advantages over linear regulators.
- d) What is commutation? Explain class C commutation with neat diagram.
- e) Describe working of emergency lighting system with neat circuit diagram.
- f) Compare step up and step down chopper based on
 - (i) Position of chopper switch
 - (ii) Output voltage
 - (iii) Expression of output voltage
 - (iv) Application

5. Attempt any FOUR of the following:**16**

- a) Draw circuit diagram of low power DC flasher. List any two applications.
- b) Describe constructional details of PUT. Why it is called programmable?
- c) Draw circuit diagram of three phase half wave controlled Rectifier. Draw its input and output voltage waveforms.
- d) Explain RC triggering of SCR with neat circuit diagram.
- e) Draw neat labeled construction of IGBT. State any two advantages.
- f) Compare Uncontrolled and Controlled Rectifiers (Any four points)

6. Attempt any FOUR of the following:**16**

- a) Explain operation of Electronic timer using SCR. Give any two applications.
 - b) Describe working of fully controlled bridge rectifier with RL load.
 - c) What is class B commutation? Explain its operation with neat diagram.
 - d) Draw layered diagram of LASCR. What is the effect of increasing intensity of light? State any two applications.
 - e) Compare power transistor and power MOSFET w.r.t.
 - (i) symbol
 - (ii) switching speed
 - (iii) SiO₂ layer
 - (iv) on state loss
 - f) Draw circuit diagram of UJT Relaxation oscillator. Draw output waveform and give expression for frequency of oscillation.
-