

17948

16117

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* –
- (1) All Questions are *Compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. **Attempt any TEN of the following:** **20**
- a) State the terms instantaneous value and maximum value of an alternating quantity.
 - b) Draw impedance triangle and voltage phasor diagram for R–L series circuits.
 - c) Define power factor and state its value for pure inductive circuits.
 - d) Define susceptance and admittance for a parallel circuit.
 - e) Draw sinusoidal waveform of 3-phase emf and indicate the phase sequence.
 - f) Define balanced and unbalanced load in case of polyphase circuits.

P.T.O.

- g) Write the procedure of converting a given practical voltage source into current source.
- h) Define quality factor of series A.C. circuit.
- i) State Thevenin's theorem.
- j) State maximum power transfer theorem.
- k) State the behaviour of following elements at the time of switching i.e. transient period
 - (i) Pure L
 - (ii) Pure C.
- l) An alternating quantity is given by $i = 14.14 \sin 314t$. Find rms value and frequency of the wave.

2. Attempt any FOUR of the following:

16

- a) An alternating current is represented by $i = 70.7 \sin 520t$. Determine -
 - (i) the frequency
 - (ii) the current 0.0015 second after passing through zero, increasing positively.
- b) Derive an expression for resonant frequency of a series RLC circuit.
- c) Write down different powers in A.C. circuits, also write their equations and units. Draw power triangle.
- d) Two impedance $(3+j4) \Omega$ and $(12-j4) \Omega$ are connected in parallel across 230V, 1 ϕ , 50Hz a.c. supply. Determine current drawn by each path and total current in the circuit.
- e) State any four advantages of polyphase circuits over single phase circuit.

- f) Using mesh analysis calculate voltage drop across 10Ω resistance for the circuit shown in Fig. No. 1

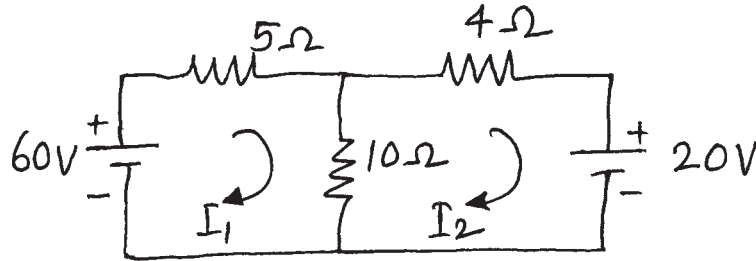


Fig. No. 1

3. Attempt any FOUR of the following: **16**

- a) Derive the expression for current in pure inductive circuit when connected to a sinusoidal ac voltage. Draw the phasor diagram.
- b) A series combination of a resistance of 100Ω and capacitance of $50\mu\text{F}$ is connected across 230V , 50Hz a.c. supply. Calculate -
 - (i) Capacitive reactance
 - (ii) Current
 - (iii) Power factor of the circuit
 - (iv) Power consumed.
- c) Compare series resonance with parallel resonance on the basis of -
 - (i) Resonant frequency
 - (ii) Impedance
 - (iii) Current and
 - (iv) Magnification
- d) A balanced delta connected load having phase impedance of $3+j4\Omega$ connected to 400V , 3ϕ , a.c. supply. Determine -
 - (i) Line current
 - (ii) Power factor
 - (iii) Active power
 - (iv) Apparent power

- e) Using mesh analysis for Fig. No. 2 find the values of R_1 and R_2 .

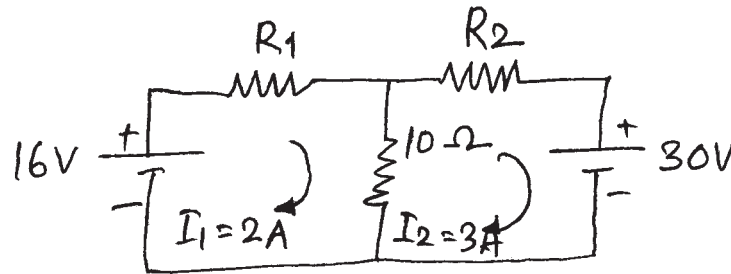


Fig. No. 2

- f) Explain the concept of initial and final conditions in switching circuits for the elements R , L and C .

4. Attempt any FOUR of the following:

16

- a) Define the following terms with reference to alternating quantity.
 - (i) Waveform
 - (ii) Cycle
 - (iii) Frequency
 - (iv) Time period
- b) A resistance of 100Ω , an inductance of 0.2H and capacitance of $150\mu\text{F}$ are connected in series across 230V , 50Hz a.c. supply. Calculate the current drawn by the circuit, power factor, its nature and power consumed by the circuit.
- c) Impedance $Z_1 = (10 + j5)\Omega$ and $Z_2 = (8 + j6)\Omega$ are connected in parallel across $V = (200 + j0)\text{V}$. Using the admittance method, calculate circuit current and the branch currents.
- d) Three coils each with a resistance of 10Ω and inductance of 0.35mH are connected in star to a 3-phase, 440V , 50Hz supply. Calculate the line current and total power taken per phase.

- e) Find the node voltages V_1 and V_2 in the circuit shown in Fig. No. 3.

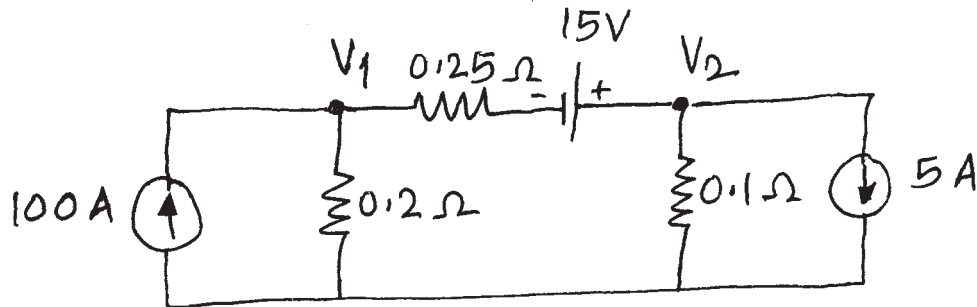


Fig. No. 3

- f) Using superposition theorem find current through R_L as shown in Fig. No. 4.

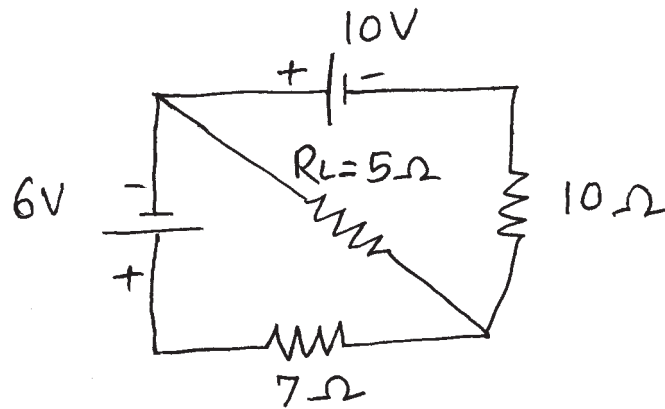


Fig. No. 4

5. Attempt any TWO of the following:

16

- a) With the help of phasor diagram, derive the relationship between line and phase values in a balanced star connected 3-phase supply

- b) Find current through impedance $3+j5\Omega$ using superposition theorem in the Fig. No. 5.

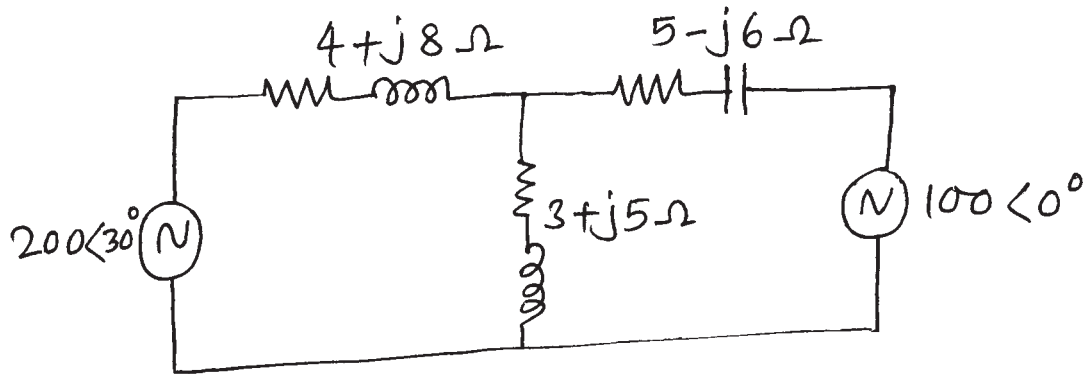


Fig. No. 5

- c) (i) Apply Thevenin's Theorem to find current flowing through 10Ω resistor in the circuit shown in Fig. No. 6.

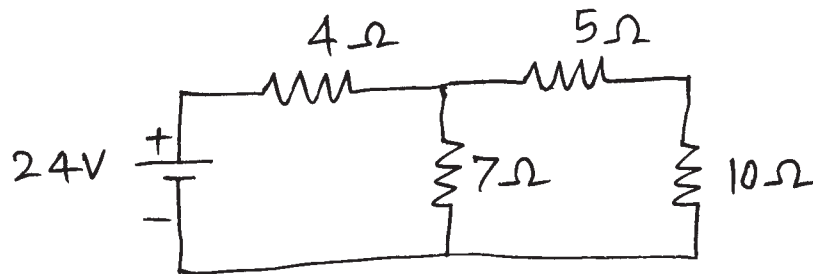


Fig. No. 6

- (ii) Using Norton's theorem find current through R_L in Fig. No. 7.

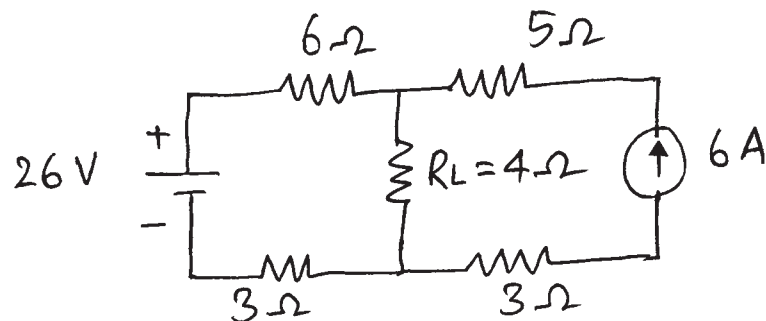
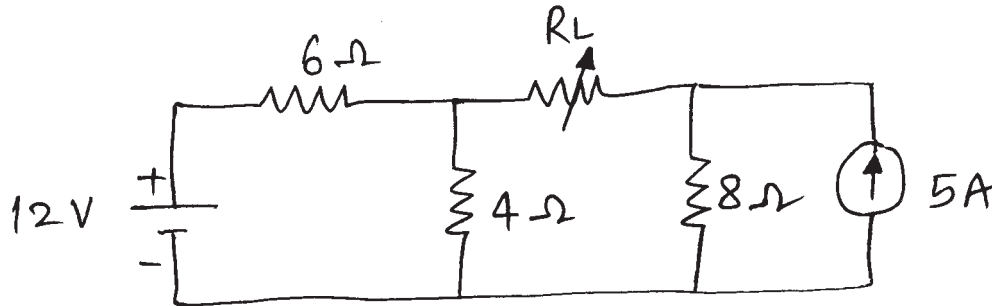


Fig. No. 7

6. Attempt any FOUR of the following:

16

- a) Find the value of R_L to transfer maximum power in the network shown in Fig. No. 8.

Fig. No. 8

- b) Derive the formulae for star to delta transformation.
- c) Explain the phenomenon of resonance in parallel circuit by drawing a parallel electric circuit.
- d) Draw a circuit diagram of R.C. Series circuit. Draw impedance triangle, waveform and phasor diagram for the same circuit.
- e) Draw graphical representation of resistance, inductive reactance, capacitive reactance and impedance related to frequency for series resonance circuit.
- f) Explain how three phase emf can be generated. Write down three phase voltage equations and the meaning of phase sequence.
-