

16117

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Illustrate your answers with neat sketches wherever necessary.
 - (3) Figures to the right indicate full marks.
 - (4) Assume suitable data, if necessary.
 - (5) Use of Non-programmable Electronic Pocket Calculator is permissible.

Marks**1. Attempt any TEN of the following :****20**

- (a) Define ripple factor and efficiency w.r.t. rectifiers.
- (b) Write any two applications of transistor.
- (c) Draw ladder diagram of NOR gate.
- (d) List any two applications of DAC.
- (e) Draw the labelled symbol of an Op-Amp.
- (f) Give factors affecting the stability of Q point.
- (g) Draw symbol of OR gate. Give its truth table.
- (h) Write any two features of Real Time Mechatronics system.
- (i) Explain the terms with respect to amplifier :
 - (i) Bandwidth
 - (ii) Half power points
- (j) State different types of flip-flops.
- (k) List any two applications of monostable multivibrator.
- (l) List basic components of computer integrated manufacturing (CIM) system.
- (m) What are the various methods of triggering flip-flop ?
- (n) Write any two applications of crystal oscillators.

2. Attempt any FOUR of the following :**16**

- (a) Draw and explain transistor as an amplifier.
- (b) Implement AND gate and OR gate using NOR gate only.
- (c) Draw block diagram of CNC system and explain it.

- (d) Draw and explain block diagram of Op-Amp.
- (e) Draw and explain block diagram of instrumentation system.
- (f) Draw characteristics of zener diode and explain it.

3. Attempt any FOUR of the following : 16

- (a) Explain Barkhausen criteria.
- (b) Draw and explain single channel DAS (Data Acquisition System).
- (c) Describe the elements of Robot.
- (d) With suitable block diagram describe the operation of multiplexer.
- (e) Explain center tapped full wave rectifier with circuit diagram and waveform.
- (f) Draw a neat circuit of single stage CE-amplifier using NPN transistor.

4. Attempt any FOUR of the following : 16

- (a) Explain any four important characteristics of a transducer.
- (b) Compare CB, CE & CC configuration of transistor (any four points).
- (c) Draw the block diagram of IC555 and label it.
- (d) Explain procedure to plot the DC load line.
- (e) Describe Flexible Manufacturing System (FMS).
- (f) Draw S-R flip flop using NOR gates and explain its operation.

5. Attempt any FOUR of the following : 16

- (a) Draw and explain frequency response of single stage CE amplifier. Why gain falls at very low and very high frequencies ?
- (b) Draw circuit diagram of three bit ripple counter and explain.
- (c) Describe a block diagram of PLC with neat diagram.
- (d) Draw and explain circuit of Op-Amp as adder.
- (e) Explain the working principle of n-channel J-FET with suitable diagram.
- (f) Explain the need of signal conditioning. Draw block diagram of AC signal conditioning system.

6. Attempt any FOUR of the following : 16

- (a) Differentiate between microcontroller and microprocessor (any four points).
 - (b) Draw and explain instrumentation amplifier.
 - (c) Explain the selection criteria for a transducer.
 - (d) Describe the working principle of optocoupler.
 - (e) Draw the ladder diagram for following boolean expression :
$$Y = (A + B) \cdot (C + D)$$
 - (f) Draw and explain transformer-coupled amplifier.
-