

17215

11819

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
  - (2) Illustrate your answers with neat sketches wherever necessary.
  - (3) Figures to the right indicate full marks.
  - (4) Assume suitable data, if necessary.
  - (5) Use of Non-programmable Electronic Pocket Calculator is permissible.
  - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

1. Attempt any TEN :

2 × 10 = 20

- (a) Give the detail classification of capacitor.
- (b) Write two applications of (i) LED (ii) photodiode.
- (c) State maximum power transfer theorem.
- (d) Define active and passive network.
- (e) List four specifications of resistor.
- (f) Draw ideal and practical voltage source and current source.
- (g) List two applications of (i) clipper (ii) clamper.
- (h) Draw the symbol of (i) Iron core inductor (ii) variable capacitor (iii) resistor (iv) Ferrite core inductor.
- (i) State the need of filters.
- (j) Define ferromagnetic and ferrimagnetic materials.
- (k) State Kirchoff's current and voltage law (kCL & kVL).
- (l) Define self and mutual induced emf.

## 2. Attempt any FOUR :

 $4 \times 4 = 16$ 

- (a) Draw negative clamper circuit and explain its working.  
 (b) Draw Thevenin's equivalent circuit for the circuit shown in fig. 2 (b).

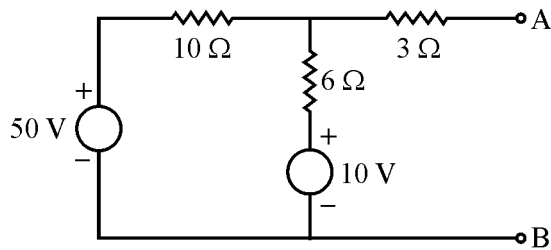


Fig.-2(b)

- (c) Draw and describe circuit diagram of centre tapped rectifier with LC filter along with its input and output waveforms.  
 (d) Find resistance value for the given colour codes :  
 (i) Red Brown Black Gold  
 (ii) Blue Yellow Grey  
 (iii) Blue Violet Red Silver  
 (iv) Red Red Orange Gold  
 (e) Compare half and full wave bridge rectifier on the basis of :  
 (i) DC output voltage  
 (ii) Ripple factor  
 (iii) Efficiency  
 (iv) rms value of voltage  
 (f) Draw and describe constructional diagram of electrolytic capacitor.

## 3. Attempt any FOUR :

 $4 \times 4 = 16$ 

- (a) Draw B-H curve and define coercivity and reluctivity.  
 (b) Draw and describe working of RC integrator with output waveform for square wave input.  
 (c) Compare C, L, LC &  $\Pi$  filter. (any four points)

- (d) Draw and describe working of series biased clipper with input – output waveforms.
- (e) Calculate  $I_L$  for the network shown in fig. (3 e)

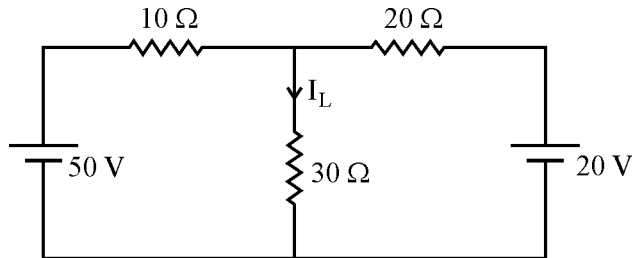


Fig.-3(e)

- (f) Draw and describe working of bridge rectifier with its input and output waveforms.

4. Attempt any FOUR :

$4 \times 4 = 16$

- (a) Compare PN junction diode with zener diode (any four points).
- (b) State Norton's theorem with suitable example.
- (c) Draw VI characteristic of PN junction diode and define knee voltage, leakage current, reverse saturation current, breakdown voltage.
- (d) Draw VI characteristic of Tunnel diode and describe it.
- (e) Draw and describe the construction of LDR.
- (f) Define :
- |                         |                         |
|-------------------------|-------------------------|
| (i) Linear network      | (ii) Non-linear network |
| (iii) Bilateral network | (iv) Unilateral network |

5. Attempt any FOUR :

$4 \times 4 = 16$


- (a) Compare clipper and clamper circuit (any four points).
- (b) Describe the working principle of LED with neat construction.
- (c) Define :
- |                     |                           |
|---------------------|---------------------------|
| (i) Rectifier       | (ii) PIV of diode         |
| (iii) Ripple factor | (iv) Rectifier efficiency |

P.T.O.

17215

[4 of 4]

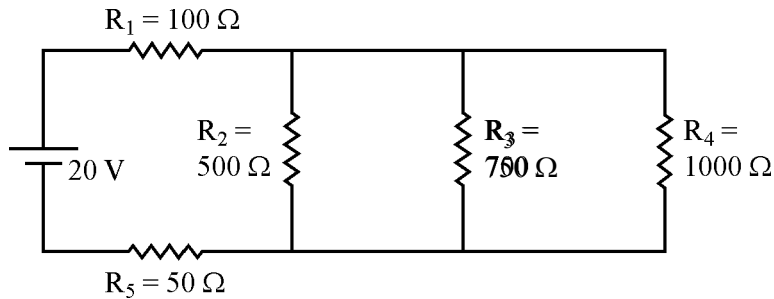- (d) An AC supply of 230 V is applied to half wave rectifier through a transformer with turns ratio 10:1. Find DC output voltage and PIV of diode.
- (e) Find current through  $R_1$  in following circuit :




- (f) List types of TDR and compare them. (any two)

6. Attempt any FOUR :

$4 \times 4 = 16$

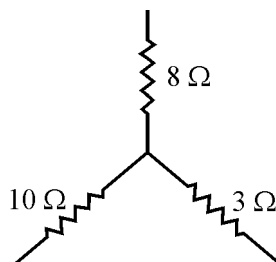- (a) Describe working of schottky diode with neat construction.
- (b) Convert the given star network into equivalent delta network.



- (c) Compare RC integrator with RC differentiator (any four points).
- (d) Describe working principle of LASER.
- (e) State superposition theorem with suitable example.
- (f) Draw and describe the VI characteristics of zener diode.
-