

22310

11819

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.

SECTION - A

- | | Marks |
|---|--------------|
| 1. Attempt any SIX of the following : | 12 |
| (a) Define permeability. | |
| (b) Define MMF. | |
| (c) Define form factor of an alternating quantity. | |
| (d) Define frequency and time period of an alternating quality. | |
| (e) Define transformation ratio of transformer. | |
| (f) State the EMF equation of a 1ϕ transformer and state the meaning of each term used. | |
| (g) Give two applications of single phase motors. | |
| 2. Attempt any THREE of the following : | 12 |
| (a) Draw and explain B – H curve. | |
| (b) Draw a balanced 3-phase star connected load. Show various line and phase values and also state the relationship between them. | |
| (c) Explain the working principle of 1ϕ transformer. | |
| (d) Explain the working principle of 1ϕ motor with a neat diagram. | |

- 3. Attempt any TWO of the following :** **12**
- (a) State and explain Faraday's laws of electromagnetic Induction.
 - (b) An inductance of 0.1H and a resistance of 50Ω are connected in series across a 220 V, 50 Hz AC supply.
Determine : (i) Impedance (ii) Current (iii) Power factor (iv) Power Consumed
 - (c) Derive the EMF equation of a 1ϕ transformer.

SECTION - B

- 4. Attempt any FIVE of the following :** **10**
- (a) Define Active component. Give two examples.
 - (b) Draw the symbol of PN-junction diode and give two applications.
 - (c) Draw the symbols of PNP and NPN transistor.
 - (d) Define PIV.
 - (e) Draw the symbol of ideal voltage source and ideal current source.
 - (f) Define α and β of a transistor.
- 5. Attempt any THREE of the following :** **12**
- (a) Define amplitude and phase of a sinusoidal quantity.
 - (b) Explain the constructional details of LED.
 - (c) Explain zener diode as a voltage regulator.
 - (d) Find the value of resistor from the given colour code :
 - (i) Red Red Red Gold
 - (ii) Blue Orange Green Silver
 - (e) Explain with neat diagram how transistor can be used as a switch.
- 6. Attempt any TWO of the following :** **12**
- (a) Differentiate between analog and digital ICs.
 - (b) Explain the working of half wave rectifier with suitable diagram.
 - (c) Draw the diagram of transistor operating regions.
-