

22430

21819

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* –
- (1) All Questions are *Compulsory*.
 - (2) Illustrate your answers with neat sketches wherever necessary.
 - (3) Figures to the right indicate full marks.
 - (4) Assume suitable data, if necessary.
 - (5) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

- 1. Attempt any FIVE of the following: **10****
- a) State the difference between single phase and three phase controlled rectifiers (any two points).
 - b) Enlist the name of any two triggering circuit for phase controlled rectifiers.
 - c) Define chopper and state its classification.
 - d) State the applications of inverter (any four)
 - e) State any four thyristor ratings.
 - f) Draw the neat sketch of SCR stud mounting technique.
 - g) Sketch the neat circuit diagram and waveform of single phase Cycloconverter.

P.T.O.

- 2. Attempt any THREE of the following:** **12**
- a) List any four applications of phase controlled rectifier and explain any one in brief.
 - b) Explain with neat sketch the working of three phase half wave controlled rectifier with resistive load.
 - c) Draw circuit diagram of three phase bridge inverter.
 - d) Describe with neat sketches the operation of firing circuits using logic gates.
- 3. Attempt any THREE of the following:** **12**
- a) Draw a neat circuit diagram of single phase full bridge inverter with waveform and give its operation.
 - b) Describe with neat sketch the working of single phase cycloconverter with R-load.
 - c) Describe the use of PLL in triggering circuit.
 - d) Explain with circuit diagram of Mc Murray half bridge inverter.
- 4. Attempt any THREE of the following:** **12**
- a) Describe the operation of basic parallel inverter with waveforms.
 - b) Explain the three phase fully controlled bridge converter with resistive load with neat sketch and waveform.
 - c) Describe with neat sketch pulse triggering of phase controlled rectifier with waveforms.
 - d) Explain with operation of four quadrant chopper with quadrant diagram.

- e) Identify the circuit and draw output waveforms across load.
Kindly refer Figure No. 1

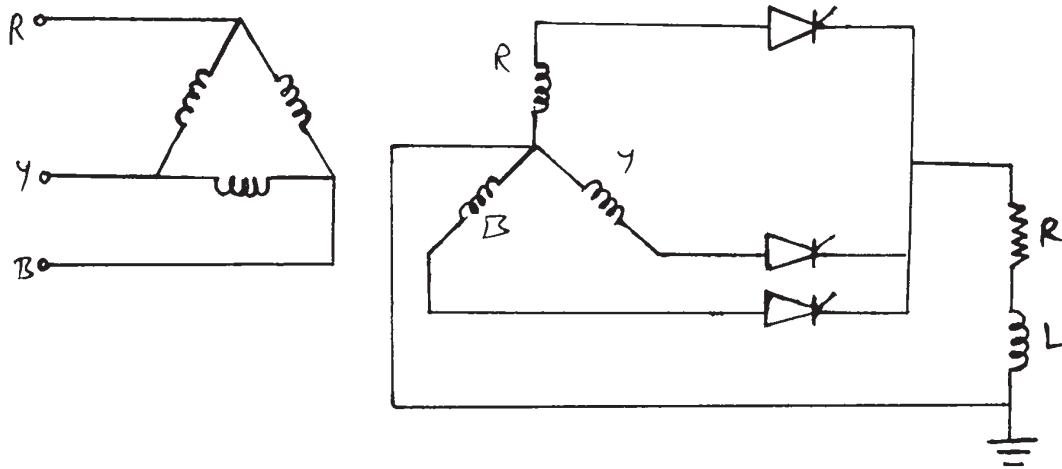


Fig. No. 1

5. Attempt any TWO of the following: 12
- Draw circuit of single phase to three phase cycloconverter and explain its operation with waveforms.
 - Three phase fully controlled rectifier is connected to three phase ac supply of 230V, 50Hz. Load current is continuous and negligible ripple. If average load current $I_{dc} = 100$ A and commutating inductance $L_c = 0.1$ mH. Determine the overlap angle with $\alpha = 25^\circ$.
 - Explain the function of step-up chopper using MOSFET with circuit diagram and waveforms.
6. Attempt any TWO of the following: 12
- State types of heat sink used in power electronics application and explain any one.
 - Explain the working of Jones Chopper with its waveform.
 - A Mc Murray inverter uses a commutation circuit consisting of $C = 25\mu\text{F}$ and $L = 25\mu\text{H}$ the source voltage $E_{DC} = 230$ Vdc. The load current varies from 100 to 150 A at the instant of commutation. Find the value turn off time E_{dc} minimum is 20% of E_{dc} .