

312310

12526

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

-
- Instructions* – (1) All Questions are *Compulsory*.
(2) Answer each next main Question on a new page.
(3) Illustrate your answers with neat sketches wherever necessary.
(4) Figures to the right indicate full marks.
(5) Assume suitable data, if necessary.
(6) Use of Non-programmable Electronic Pocket Calculator is permissible.
(7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

- 1. Attempt any FIVE of the following :** **10**
- a) Define Ohm's Law and state its equation.
 - b) State Lenz's Law.
 - c) Write the equation of Energy stored in Capacitor.
 - d) Define "MMF" and state its unit.
 - e) If two resistances 3Ω and 5Ω are in series, calculate their equivalent resistance.
 - f) State "Fleming's Right Hand Rule".
 - g) State any two types of inductors.

P.T.O.

2. Attempt any THREE of the following :

12

- Derive the equation of energy stored in a capacitor.
- Define “Resistance” and “Resistivity” and state their units.
- Three capacitors having capacitances of $4 \mu\text{F}$, $5 \mu\text{F}$ and $10 \mu\text{F}$. Find total capacitance when they are connected in –
 - Series
 - Parallel
- Draw the symbol and characteristics of Ideal Voltage Source and Practical Voltage Source.

3. Attempt any THREE of the following :

12

- Define the following :
 - Magnetic Lines of Force
 - Flux
 - Flux Density
 - Magnetic Flux intensity.
- State any four types of Inductors and state their applications.
- Derive an equation for capacitance of parallel plate capacitor.
- Find the current (I) flowing through 8Ω resistor shown in Figure No. 1 using Kirchhoff's Voltage Law.

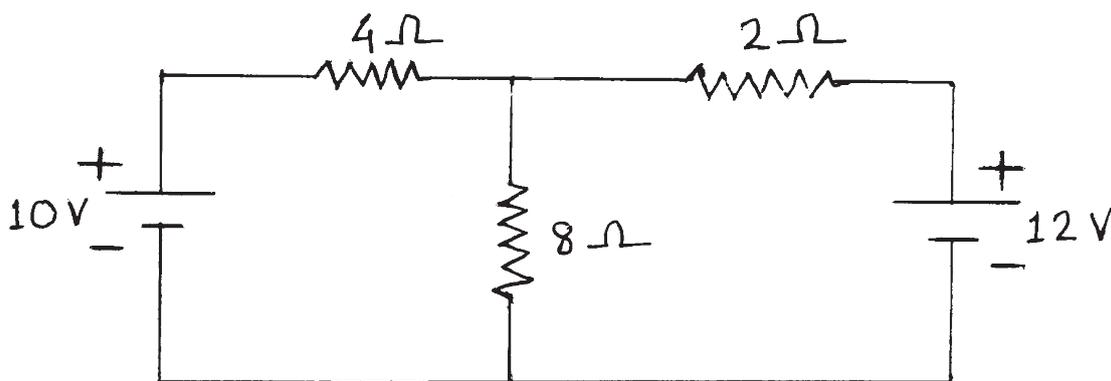


Fig. No. 1

4. Attempt any THREE of the following :

12

- Describe the effect of temperature on Resistance.
- Draw hysteresis loop for hard steel, cast steel and sheet steel, also write applications for each material.
- Derive the equation for Energy stored in Magnetic Field.
- Compare between Electric and Magnetic Circuits.
(Any four points)
- State different types of effects of electric current and explain any one.

5. Attempt any TWO of the following :

12

- Calculate the equivalent resistance between terminal A and B shown in Figure No. 2.

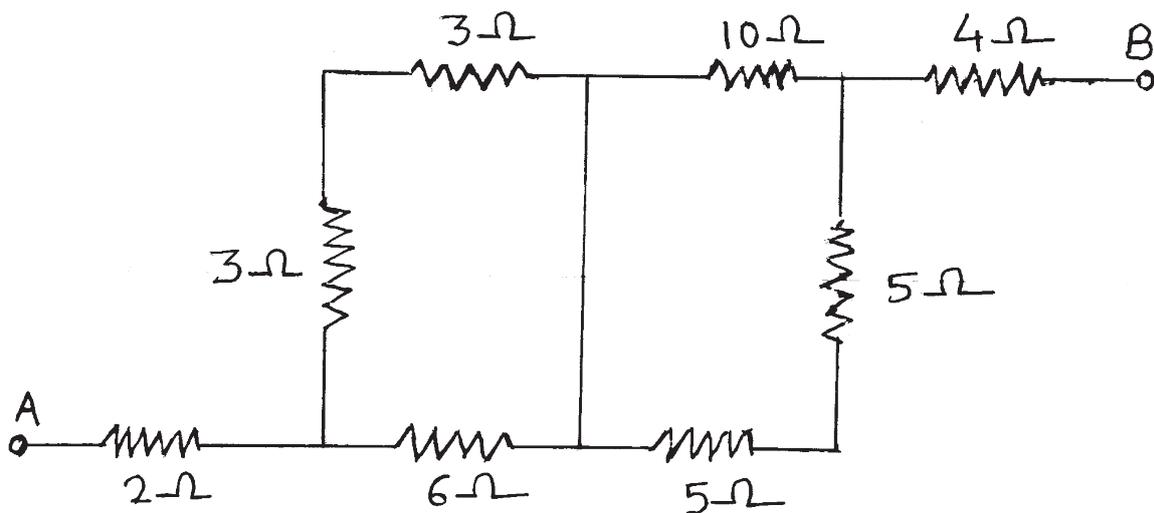


Fig. No. 2

- An iron ring of mean circumference of 70 cm and cross sectional area of 50 mm^2 is uniformly wound by wire of 1000 turns carrying 1.6 A current. Calculate the value of flux and flux density. (Assume $\mu_r = 1000$). Also calculate mmf and field intensity.

312310

[4]

Marks

- c) Define the following terms :
- i) Active and Passive Network
 - ii) Linear and Non-Linear Circuit
 - iii) Unilateral and Bilateral Circuit

6. Attempt any TWO of the following :

12

- a) Derive the equation of Coefficient of Coupling in Magnetic Circuits.
 - b) State and explain Breakdown Voltage and Di-electric strength of capacitor. Also state the factors affecting Breakdown Voltage.
 - c) Draw a neat sketch of series magnetic circuit. State value of reluctance (S) for both series and parallel magnetic circuit. Name each term used in them.
-