

313318

12526

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

-
- Instructions* – (1) All Questions are *Compulsory*.
(2) Answer each next main Question on a new page.
(3) Illustrate your answer with neat sketches wherever necessary.
(4) Figures to the right indicate full marks.
(5) Assume suitable data, if necessary.
(6) Use of Non-programmable Electronic Pocket Calculator is permissible.
(7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

- 1. Attempt any FIVE of the following: **10****
- a) Draw the symbol of zener diode and LED.
 - b) Define α and β of a transistor.
 - c) List types of rectifier.
 - d) Convert following:
 $(25)_{10} = (?)_2 = (?)_{16}$.
 - e) Write specifications of IC 0808. (Any two points)
 - f) Draw symbol and write the truth table of D-flip-flop.
 - g) Write the base or Radix of following number system.
 - i) Binary
 - ii) Octal
 - iii) Decimal
 - iv) Hexadecimal.

P.T.O.

2. Attempt any THREE of the following: 12
- a) Draw and explain V-I characteristics of zener diode.
 - b) Describe the construction and working of NPN transistor with diagram.
 - c) Draw symbols and write truth table of NOT, AND, OR and NAND gate.
 - d) Explain the operation of SISO shift register with circuit diagram.
3. Attempt any THREE of the following: 12
- a) Draw the circuit of zener diode as a voltage regulator and explain its working.
 - b) Draw the circuit diagram of 4-bit R-2R ladder DAC and state its output voltage expression.
 - c) Compare CB, CE and CC configuration on the basis of –
 - i) Input impedance
 - ii) Output impedance
 - iii) Voltage gain
 - iv) Current gain.
 - d) Subtract using 2'S complement method :-
 - i) $(0101)_2 - 1001_2$
 - ii) $(1110)_2 - (1001)_2$
4. Attempt any THREE of the following: 12
- a) With circuit diagram explain transistor as a switch.
 - b) Draw logic diagram of Half Adder and write its truth table.
 - c) Draw block diagram of DC regulated power supply. State the function of each block.
 - d) Draw and explain the working of single slope ADC.
 - e) State and prove Demorgan's first and second Theorem.

5. Attempt any TWO of the following:**12**

- a) Compare half wave, centre tapped full wave and bridge type rectifier on the basis of :-
- i) Number of diodes used
 - ii) Ripple factor
 - iii) Rectification efficiency
 - iv) Output dc voltage (Vdc)
 - v) Peak inverse voltage
 - vi) Transformer utilisation factor.
- b) Draw and explain single stage RC coupled CE amplifier and state the function of each component.
- c) Draw circuit diagram and output waveforms of 3-bit synchronous counter.

6. Attempt any TWO of the following:**12**

- a) Describe successive approximation (SAR) Register ADC with diagram.
- b) Draw and explain 8:1 multiplexer with truth table.
- c) Draw input and output characteristics of CE configuration and show different regions on it.
-