

# 313332

**12526**

**3 Hours / 70 Marks**

Seat No. 

--	--	--	--	--	--	--	--

- 
- Instructions* – (1) All Questions are *Compulsory*.
- (2) Answer each next main Question on a new page.
- (3) Illustrate your answer with neat sketches wherever necessary.
- (4) Figures to the right indicate full marks.
- (5) Assume suitable data, if necessary.
- (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
- (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

- 1. Attempt any FIVE of the following: **10****
- a) Define frequency and time period related to a.c. waveform.
- b) Draw impedance triangle and phasor diagram for R-C series circuit.
- c) Define Admittance related to AC circuit. State its SI Unit.
- d) Draw phasor diagram for three-phase voltages. Express these voltages in polar form.
- e) Draw an ideal and a practical current source. Write difference between them.
- f) State the maximum power transfer theorem for DC circuits.
- g) State Reciprocity theorem.

P.T.O.

2. Attempt any THREE of the following:

12

- a) For series R-L-C circuit, draw neat circuit diagram. State the three conditions for R-L-C series circuit. Draw voltage triangle and impedance triangle for  $X_L > X_C$ .
- b) A coil having resistance of  $5\Omega$  and an inductance of  $0.2\text{ H}$  is connected in parallel with a series combination of  $10\Omega$  resistor and  $80\ \mu\text{F}$  capacitor. If supply voltage is  $230\text{ V}$ ,  $50\text{ Hz}$ , determine :-
- Total circuit impedance
  - Total current taken by the circuit
  - Power factor of the circuit.
- c) Three equal impedances having  $R = 20\Omega$  in series with  $C = 50\ \mu\text{F}$  are connected in delta across  $415\text{ V}$ , 3 phase,  $50\text{ Hz}$  AC supply. Determine :-
- Impedance per phase
  - Phase and line currents
  - Total power consumed by load.
- d) State the equivalent delta  $R_{12}$ ,  $R_{23}$  and  $R_{31}$  for star connection of three resistances  $R_1$ ,  $R_2$  and  $R_3$  with proper equations for network shown in Figure No. 1 :

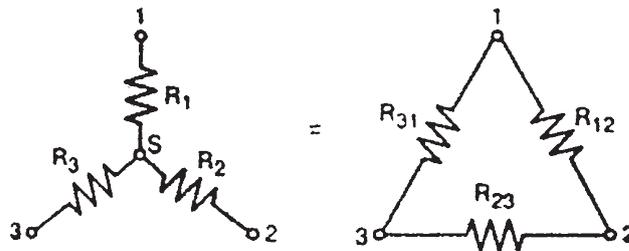


Fig. No. 1

3. Attempt any THREE of the following:

12

- a) A series R-L-C circuit has  $R = 5\Omega$ ,  $L = 10\text{ mH}$  and  $C = 15\ \mu\text{F}$ . Calculate :-
- Resonant frequency
  - Q-factor of the circuit
  - Bandwidth
  - Voltage Magnification.

- b) Explain the “Current Magnification” in parallel resonant circuit consisting of inductive branch (R-L) in parallel with a pure capacitor (C). Derive equation for it.
- c) Using mesh analysis, find current in  $5\Omega$  resistor in the network shown in Figure No. 2.

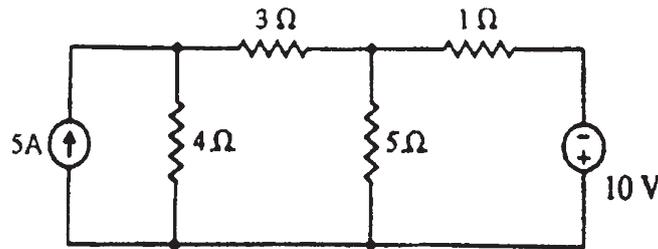


Fig. No. 2

- d) Using Node analysis, find current  $I$  in the circuit shown in Figure No. 3.

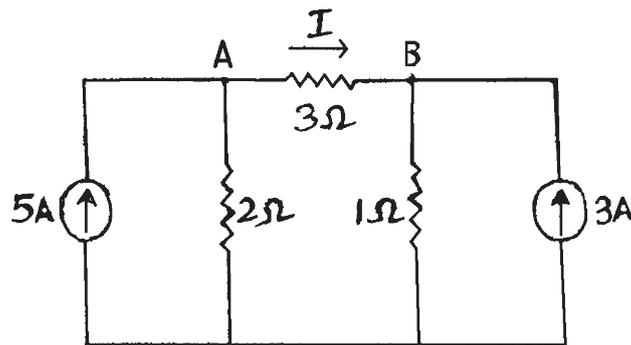


Fig. No. 3

4. Attempt any THREE of the following:

12

- a) Two circuits the impedance of which are given by  $Z_1 = (6 + j8)$  ohm and  $Z_2 = (8 - j6)$  ohm are connected in parallel. If the applied voltage to the combination is 100 V, Find by impedance method :-
- Current at each branch
  - Overall current
  - Power factor of the combination.

- b) Compare parallel resonance with series resonance on the basis of :-
- Impedance
  - Current
  - Magnification
  - Resonant frequency.
- c) With neat circuit diagram, explain how to convert a practical voltage source into an equivalent practical current source.
- d) Write stepwise procedure for applying Thevenin's theorem to simple circuits. (Assume simple circuit)
- e) Calculate the value of R which will absorb maximum power from the circuit of Figure No. 4.

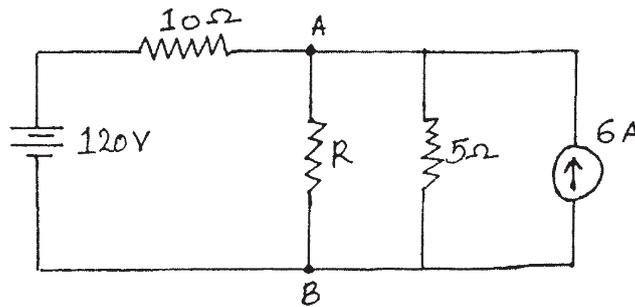


Fig. No. 4

5. Attempt any TWO of the following:

12

- a) For a series R-L-C circuit consisting of  $R = 5\Omega$ ,  $L = 0.01$  H and  $C = 10 \mu\text{F}$  supplied with 230 V, 50 Hz supply, Determine :-
- Circuit impedance
  - Circuit current
  - Circuit power factor
  - Active power
  - Reactive power
  - Apparent power.

- b) In a 3 phase star connected system, derive the relationship  $V_L = \sqrt{3} V_{ph}$ .
- c) Apply superposition theorem to compute current  $I$  in the network shown in Figure No. 5.

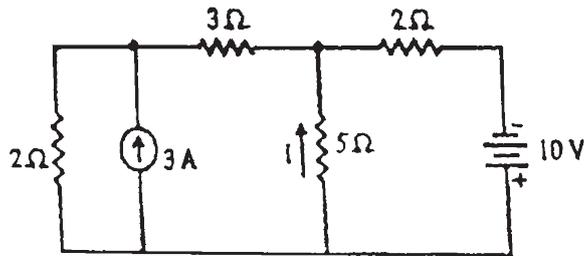


Fig. No. 5

6. Attempt any TWO of the following: 12

- a) Explain Graphical Representation of Resonance in R-L-C series circuit.
- b) A balanced delta connected load, consists of per phase impedance of  $(5 + j7)\Omega$ . It is supplied with 415 V, 50 Hz, 3 phase AC supply. Calculate :-
- Line current
  - Phase current
  - Phase voltage
  - Total power absorbed
  - Power factor of the combination.

Also draw vector diagram.

- c) By Norton's theorem, find the current in  $4\Omega$  resistor in the network shown in Figure No. 6.

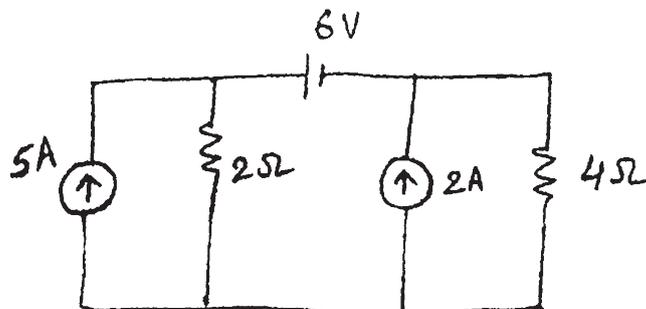


Fig. No. 6