

# 314363

**12526**

**3 Hours / 70 Marks**

Seat No. 

--	--	--	--	--	--	--	--

- 
- Instructions* – (1) All Questions are *Compulsory*.  
(2) Illustrate your answers with neat sketches wherever necessary.  
(3) Figures to the right indicate full marks.  
(4) Assume suitable data, if necessary.  
(5) Use of Non-programmable Electronic Pocket Calculator is permissible.  
(6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

- 1. Attempt any FIVE of the following :** **10**
- a) Draw labelled symbol of LASCR and TRIAC.
  - b) State the relation between firing angle and conduction angle with waveform.
  - c) Write four turn ON methods of SCR.
  - d) Draw the basic block diagram of SMPS.
  - e) List two applications of inverter.
  - f) Define latching current and holding current of SCR.
  - g) A single phase full wave controlled rectifier is supplied with a voltage  $V = 230 \sin 314 t$ . If firing angle is 30 degrees, find average dc output voltage.

P.T.O.

- 2. Attempt any THREE of the following : 12**
- a) Explain the working of class C commutation with neat circuit diagram and waveforms.
  - b) Draw and explain proximity detector using SCR.
  - c) Interpret the VI characteristics of PUT.
  - d) Draw the circuit diagram of a semi-converter with R load and explain its working.
- 3. Attempt any THREE of the following : 12**
- a) Draw VI characteristics of SCR. State the effect of gate current on operation of SCR.
  - b) Give classification of cyclo-converter. State and explain working principle of single phase cyclo-converter with R load.
  - c) Explain the effect of freewheeling diode with respect to single phase centre tapped full wave controlled rectifier with RL load.
  - d) Define performance parameters for the inverter.
- 4. Attempt any THREE of the following : 12**
- a) Draw the constructional diagram of GTO and explain it's working.
  - b) Explain with circuit diagram the operation of battery charger using SCR.
  - c) Explain operation with circuit diagram a suitable type of triggering circuit to control the firing angle from  $0^\circ$  to  $180^\circ$ .
  - d) Explain with a neat circuit diagram the operation of series inverter.
  - e) Explain the operation of three phase half wave controlled rectifier with circuit diagram and also sketch it's input and output waveforms.

**5. Attempt any TWO of the following : 12**

- a) Draw circuit diagram and explain the operation of emergency lighting system.
- b) Draw and explain the circuit diagram of UJT relaxation oscillator and write the expression for frequency.
- c) What is the need of polyphase rectifier ? Draw and explain 3- $\phi$  rectifier (uncontrolled) with R load.

**6. Attempt any TWO of the following : 12**

- a) Name a suitable chopper to increase the output voltage and also explain its operation with neat circuit diagram using IGBT with R load.
  - b) State the need of snubber circuit. Draw  $di/dt$  and  $dv/dt$  protection circuit.
  - c) Explain two transistor analogy of SCR. Write relation between anode current and gate current.
-