



**Q.4) Attempt any Three of the following. 12 Marks**

- a. Describe full bridge inverter with neat sketch.
- b. Describe six pulse half wave controlled rectifier with neat sketch.
- c. Compare morgan's chopper with jones's chopper with respect of i) operation ii) application.
- d. Explain the necessity of getting synchronized firing pulses for the gate trigger of thyristor in fully controlled converter.
- e. List any four applications of phase controlled rectifier explain any one in brief.

**Q.5) Attempt any Two of the following. 12 Marks**

- a. Explain the function of DC chopper using MOSFET with circuit diagram and waveform.
- b. State the types of heatsink used in power electronics application and explain any one
- c. A Mc-Murray inverter uses a commutation circuit consisting of  $C=25\mu\text{F}$  and  $L=25\mu\text{H}$  the source voltage  $E_{\text{DC}}=230\text{ V dc}$ . The load current varies from 50 to 150A at the instant of commutation. Find the value of turn off time.  $E_{\text{dc}}$  minimum is 10% of  $E_{\text{dc}}$

**Q.6) Attempt any Two of the following. 12 Marks**

- a. Three phase fully controlled rectifier is connected to three phase ac supply of 230V, 50Hz. load current is continuous and has a negligible ripple. If the average load current  $I_{\text{dc}}=150\text{ A}$  and the commutating inductance  $L_c = 0.1\text{ mH}$ . Determine the overlap angle when  $\alpha = 10^\circ$ .
- b. Explain the functioning of four quadrant chopper with respect to output waveform
- c. Draw the circuit of single phase to single phase Cycloconverter explain its operation with waveforms.

**Scheme - I**  
**Sample Test Paper - I**

**Program Name** : Diploma in Industrial Electronics  
**Program Code** : IE  
**Semester** : Fourth  
**Course Title** : Applied Power Electronics  
**Max. Marks** : 20

22430

**Time : 1 Hour**

---

**Instructions:**

- (1) All questions are compulsory.
- (2) Illustrate your answers with neat sketches wherever necessary.
- (3) Figures to the right indicate full marks.
- (4) Assume suitable data if necessary.
- (5) Preferably, write the answers in sequential order.

**Q.1 Attempt any FOUR.**

**08 Marks**

- a. Differentiate between UJT and DIAC
- b. Define intrinsic stand of ratio with respect to UJT
- c. State merits of Jones's Chopper
- d. List different power semiconductor devices
- e. Sketch the Symbol of TRIAC with characteristics
- f. Differentiate between step up chopper and step down chopper

**Q.2 Attempt any THREE.**

**12 Marks**

- a. Interpret the output wave forms of the four Quadrant choppers.
- b. Explain with neat diagram the working of single phase controlled rectifier
- c. State the function of freewheeling diode in controlled rectifier and its merit.
- d. Describe with neat labelled sketch working of UJT triggering circuit for SCR
- e. Explain with neat sketch the function of step up chopper
- f. A single phase half wave converter is operated from a 230V, 50Hz supply. If the load is resistive of value 10 ohms and firing angle  $\alpha$  is 60 degree. Determine i) the efficiency ii) ripple factor v) peak inverse voltage of thyristor.

**Scheme -I**  
**Sample Test Paper - II**

**Program Name** : Diploma in Industrial Electronics  
**Program Code** : IE  
**Semester** : Fourth  
**Course Title** : Applied Power Electronics  
**Max. Marks** : 20

**22430**

**Time : 1 Hour**

---

**Instructions:**

- (1) All questions are compulsory.
- (2) Illustrate your answers with neat sketches wherever necessary.
- (3) Figures to the right indicate full marks.
- (4) Assume suitable data if necessary.
- (5) Preferably, write the answers in sequential order.

**Q.1 Attempt any FOUR.**

**08 Marks**

- a. State the limitations of SCR series inverter
- b. List the applications of Dual Converter
- c. Give classification of cycloconverters
- d. Sketch the neat diagram of snubber circuit
- e. Differentiate between half bridge inverter and full bridge inverter.
- f. State  $I^2R$  rating of thyristor

**Q.2 Attempt any THREE.**

**12 Marks**

- a. Draw the circuit diagram of three phase to single phase cycloconverter and discuss briefly.
- b. Differentiate between single phase inverter and three phase inverter
- c. List different type of scheme of thyristor protection.
- d. Explain with sketches the working of the circulatory current free dual converters.  
of dual converters Compare CSI and VSI.
- a. A single phase full bridge inverter has a resistive load of 2.4 ohms and the DC input voltage of 48 V. Determine the RMS output voltage at the fundamental frequency and the output power.