



17214

16172

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) *All questions are compulsory.*
 - (2) *Answer each next main question on a new page.*
 - (3) *Illustrate your answers with neat sketches wherever necessary.*
 - (4) *Figures to the right indicate full marks.*

Marks

I. Attempt any ten of the following :

(10×2=20)

- 1) Define resistance. Also mention the factors upon which it depends.
- 2) What is internal voltage drop and terminal voltage ?
- 3) State any two features of carbon composition resistors.
- 4) State Ohm's law. Also express it in the form of equation.
- 5) What is dielectric strength of an insulating material ? What is its unit ?
- 6) State any two applications of electromagnet.
- 7) Define magnetic line of force. Also draw and show magnetic lines of force of a bar type magnet.
- 8) State Lenz's law.
- 9) Classify electrical materials.
- 10) State Faraday's laws of electromagnetic induction.
- 11) What is Amorphous metal ? Give one application of this metal.
- 12) State the factors affecting hysteresis loss.

II. Attempt any four of the following :

(4×4=16)

- 1) Why is source conversion needed ? Also explain how voltage source can be converted into an equivalent current source. Explain with suitable figures.
- 2) A potential difference of 200 V is applied to copper field coil at a temperature of 15° C and the current is 10 A. What will be the mean temperature of the coil when the current has fallen to 5 A, the applied voltage being the same as before ? $\alpha_{15} = \frac{1}{534.5} / ^\circ\text{C}$.

P.T.O.



- 3) Prove that $I_1 = \frac{IR_2}{R_1 + R_2}$ in the parallel combination of two resistances R_1 and R_2 .
- 4) State and explain Kirchoff's current law and voltage law.
- 5) Two batteries A and B are connected in parallel and a load of 10Ω is connected across their terminals. A has an e.m.f. of $12V$ and an internal resistance of 2Ω ; B has an e.m.f. of $8V$ and an internal resistance of 1Ω . Use Kirchoff's laws to determine the values and direction of the currents flowing in each of the batteries and in the external resistance. Refer Fig. 1.

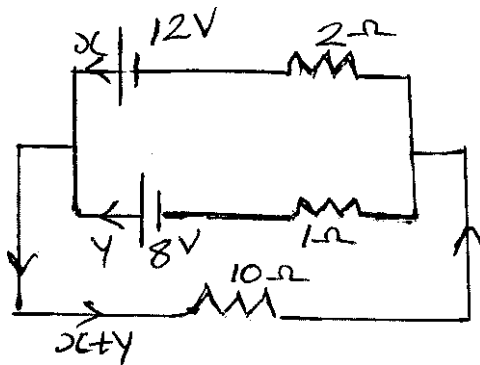


Fig. 1

- 6) Define the following terms of a magnetic circuit :
- MME
 - Ampere turns
 - Reluctance
 - Permeance.

III. Attempt any four of the following :

(4×4=16)

- Derive the equation to find capacitance of a capacitor having medium partly air.
- Draw the arrangement by which a capacitor C may be charged through a resistance R and explain it in brief.
- Three capacitors A, B, C have capacitances 10 , 50 and $25 \mu F$ respectively. Calculate (a) charge on each when connected in parallel to a $250 V$ supply (b) total capacitance.
- A $50 \mu F$ capacitor is charged from a $200 V$ supply. After being disconnected, it is immediately connected in parallel with a $30 \mu F$ capacitor. Find (a) p.d. across the combination (b) the electrostatic energies before and after the capacitors are connected in parallel.



- 5) What is magnetic hysteresis ? What is the cause of hysteresis ?
- 6) Define the following terms as referred to battery :
 - a) E.M.F.
 - b) Internal resistance
 - c) Ah efficiency and
 - d) WAh efficiency.

IV. Attempt any four of the following :

(4×4=16)

- 1) State any two harmful effects of hysteresis loss. Also draw hysteresis loop for (a) non-magnetic material (b) hard steel.
- 2) With the help of diagram, explain the concept of leakage flux, useful flux and fringing.
- 3) A mild steel ring having a cross-sectional area of 5 cm^2 and a mean circumference of 40 cm has a coil of 200 turns wound informly around it. Calculate :
 - a) Reluctance of the ring
 - b) Current required to produce a flux of $800 \mu \text{ Wb}$ in the ring.

Assume relative permeability of mild steel as 380.

- 4) In the network of resistances shown in Fig. 2. Calculate the network resistance measured between B and C.

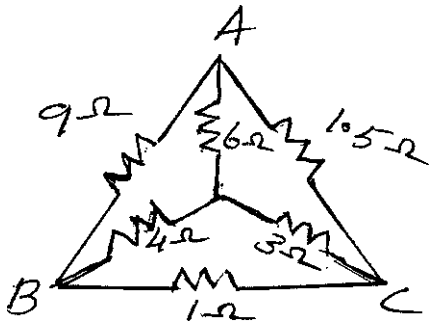


Fig. 2

- 5) Write down any three similarities between electric and magnetic circuits. Also give one important dissimilarity.
- 6) Classify insulating materials on the basis of state of material. Give two examples of each.

V. Attempt any four of the following :

(4×4=16)

- 1) Define self inductance and mutual inductance. Also write one equation for each.
- 2) Compare statically induced e.m.f. with dynamically induced e.m.f. on any four points.
- 3) Derive an expression for energy stored in a magnetic field.



Marks

- 4) Calculate the inductance of a solenoid of 2000 turns wound uniformly over a length of 50 cm on a cylindrical paper tube 4 cm in diameter. The medium is air.
- 5) State any four advantages of A.C. over D.C.
- 6) Compare series resistive circuit with parallel circuit on any four points.

VI. Attempt **any four** of the following :

(4×4=16)

- 1) Describe current charging method of batteries in brief.
- 2) Compare dry cell with liquid cell on any four points.
- 3) Define the following terms in connection with A.C. generator :
 - a) Cycle
 - b) Frequency
 - c) Time
 - d) Amplitude
- 4) Write down any two electrical and any two mechanical properties of high conductivity materials.
- 5) Classify magnetic material. Explain each type in brief.
- 6) Find the resistance between the points P and Q in the series parallel network shown in Fig. 3.

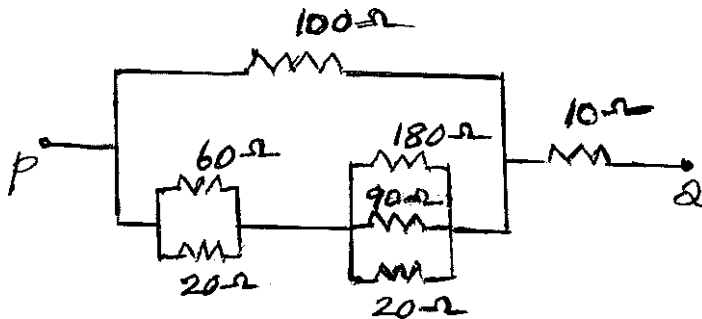


Fig. 3