

22421

21222

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

15 minutes extra for each hour

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Illustrate your answers with neat sketches wherever necessary.
 - (3) Figures to the right indicate full marks.
 - (4) Assume suitable data, if necessary.

Marks

1. Attempt any FIVE of the following :

10

- (a) State :
 - (i) Duality Theorem
 - (ii) De-Morgan's Theorem
- (b) Draw symbol and truth table of Universal Gates.
- (c) State race around condition in J-K flip flop.
- (d) Draw symbol and truth table of T-type flip flop.
- (e) Explain assemble directives
 - (i) DB
 - (ii) EQU
- (f) Explain PUSH instruction with one example.
- (g) State the function of LCD display pins.
 - (i) R/W
 - (ii) RS

2. Attempt any THREE of the following :

12

- (a) Compare between TTL and CMOS. (Any four points)
- (b) Draw OR gate and AND gate using Universal Gates.
- (c) Design 8:1 MUX using 4:1 & 2:1 MUX. Draw Truth table.
- (d) Minimise the following Boolean expression using K-map and realize it using the basic logic gates.

3. Attempt any THREE of the following : 12

- (a) Explain any four addressing modes of 8051 microcontroller with one example each.
- (b) Interface stepper motor to 8051 microcontroller and write an ALP to rotate stepper motor in Anti-clockwise direction continuously.
- (c) Compare between combinational and sequential circuit (Any four points)
- (d) Draw memory organization for $E\bar{A} = 0$ and $E\bar{A} = 1$ and explain the same.

4. Attempt any THREE of the following : 12

- (a) Explain the following instruction :
 - (i) DAA
 - (ii) DIV AB
 - (iii) CJNE A, data, rel
 - (iv) SWAP A
- (b) Compare between Harvard and Von-Neuman architecture (Any four points).
- (c) Design Half-adder using K-map and implement using basic logic gates.
- (d) Realize the following equations using NAND Gates only :
 - (i) $Y = (A + B) \cdot (B + C)$
 - (ii) $Y = AB + C$
- (e) What are the alternate function of port 3 of 8051 micro-controller ?

5. Attempt any TWO of the following : 12

- (a) Interface 8 LED's with port 1 of 8051 micro-controller. Write ALP to make LED's ON and OFF after 10 msec. delays. Assume suitable data.
- (b) Develop an ALP to arrange ten numbers stored in internal memory locations starting from 40H location in descending order.
- (c) Draw Architecture of 8051 micro-controller.

6. Attempt any TWO of the following :

12

- (a) Explain power saving options
 - (i) Idle mode
 - (ii) Power down mode
 - (b) Draw interfacing diagram of $8K \times 8$ program ROM with 8051 and also write memory map for the same.
 - (c) Construct 3 bit asynchronous up-counter using flip-flop. Draw its timing diagram.
-

