

22212

21222

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--	--

15 minutes extra for each hour

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE of the following :

10

- (a) Define the term resistance and state its unit.
- (b) State Ohm's law applied to an electrical circuit and express it in the form of equation.
- (c) Define dielectric strength and breakdown voltage.
- (d) State the values of permeability of free space and permeability of air.
- (e) Define the following terms :
 - (i) MMF
 - (ii) Reluctance
- (f) List two types of induced emf.
- (g) State Faraday's law of Electromagnetic induction.

2. Attempt any **THREE** of the following :

12

- (a) List any four types of resistors. Give one application of each.
- (b) Find the equivalent resistance between terminals A and B shown in Figure No. 1 given below :

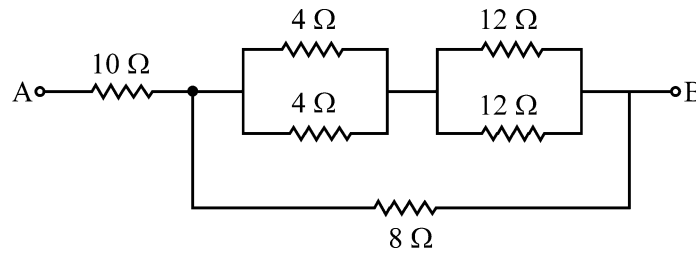


Figure No. 1

- (c) (i) State the equation for energy stored in capacitor.
- (ii) If 200 V source is applied to parallel combination of 3 capacitors of 4 μf, 8 μf and 12 μf. Calculate energy stored in each capacitor.
- (d) Compare statically induced emf with dynamically induced emf on following four points :
- (i) Movement of coil or magnet
 - (ii) Current
 - (iii) Expression of induced emf
 - (iv) Application

3. Attempt any **THREE** of the following :

12

- (a) State and explain Kirchhoff's voltage law.
- (b) A furnace takes a current of 10 ampere from 200V DC supply for 8 hours. Calculate energy consumed in kWh.

- (c) Find the current flowing through 8Ω resistor using KVL. Refer Figure No. 2.

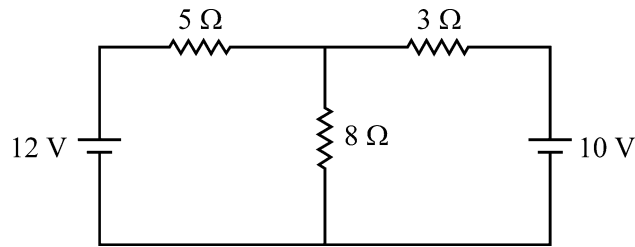


Figure No. 2

- (d) List four factors affecting capacitance of capacitor.

4. Attempt any THREE of the following :

12

- (a) Define electrical work & electrical energy. Give SI units of each.
- (b) Calculate resistance between terminals A and B, using star-delta conversion. Refer Figure No. 3.

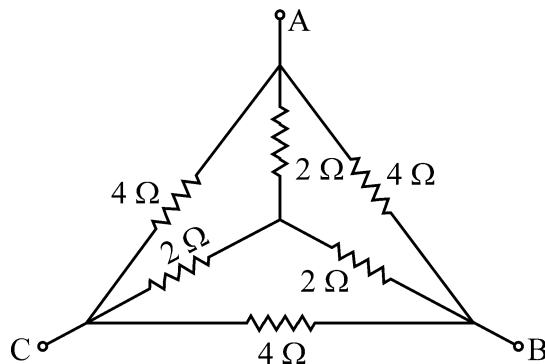


Figure No. 3

- (c) The resistance of copper coil increases from 70Ω at 12°C to 95.5Ω at 60°C . Find temperature coefficient of material at 0°C .
- (d) Three capacitors have capacitances $2\mu\text{f}$, $3\mu\text{f}$, $5\mu\text{f}$. What is the effective capacitance when connected in :
- Series
 - Parallel
- (e) Derive an expression for capacitance of the parallel plate capacitor with medium partly air.

5. Attempt any TWO of the following :**12**

- (a) Compare magnetic circuit and electric circuit stating three similarities & three dissimilarities.
- (b) An iron ring of 20 cm diameter and 5 cm^2 cross-section area is wound with 300 turns. Flux density of iron is 1 Wb/m^2 and permeability of 500. Find :
 - (i) Reluctance
 - (ii) Flux
 - (iii) MMF
 - (iv) Current
- (c) Calculate the inductance and energy stored in magnetic field of air cored coil of 300 cm long, 60 cm diameter and wound with 5000 turns and carrying 8 A current.

6. Attempt any TWO of the following :**12**

- (a) Draw hysteresis loop for hard steel, cast steel, sheet steel and non-magnetic material. Also write application of each material.
 - (b) Two coils, A of 1500 turns and B of 1200 turns are such that 70% of flux produced by coil A links with coil B. A current of 5 Ampere in coil A produces flux of 0.04 Wb in coil A and 0.085 Wb in coil B. Find :
 - (i) L_1
 - (ii) L_2
 - (iii) M
 - (iv) K
 - (c) Related to electromagnetic induction :
 - (i) Define Self-inductance & Mutual inductance.
 - (ii) Write one equation of each of the above.
 - (iii) State the Values of Coupling Factor for tight coupling and loose coupling.
-