

# 22430

**21222**

**3 Hours / 70 Marks**

Seat No. 

--	--	--	--	--	--	--	--

15 minutes extra for each hour

---

- Instructions* – (1) All Questions are *Compulsory*.
- (2) Illustrate your answers with neat sketches wherever necessary.
- (3) Figures to the right indicate full marks.
- (4) Assume suitable data, if necessary.
- (5) Use of Non-programmable Electronic Pocket Calculator is permissible.
- (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

- 1. Attempt any FIVE of the following: **10****
- a) Give classification of three phase controlled rectifier.
- b) List any four different triggering circuits used for phase controlled rectifiers.
- c) Define chopper. List it's any two applications.
- d) Differentiate voltage driven inverter and current driven inverter. (any two)
- e) State the working principle of 'Dual Converter'
- f) List any four Thyristor Mounting techniques.
- g) Enlist any two open source simulation softwares used for power electronic circuits.

P.T.O.

- 2. Attempt any THREE of the following:** **12**
- a) Draw a schematic of step-up chopper. Also draw voltage and current waveforms for it.
  - b) Compare single phase and three phase bridge controlled rectifier on the basis of No. of supply phases, power, no. of SCRs, ripple factor.
  - c) Draw the neat diagram of single phase inverse cosine firing circuit. State any two advantages.
  - d) Explain parallel capacitor inverter, with a neat schematic diagram.
- 3. Attempt any THREE of the following:** **12**
- a) Explain 'Firing circuits with logic gates' with neat sketch and waveforms.
  - b) Explain the working of Single phase half bridge inverter, with neat sketch. Draw associated waveforms.
  - c) Describe the working of circulatory current mode dual converter, with neat labelled circuit diagram.
  - d) Draw a neat labelled sketch of single phase to single phase mid-point cycloconverter. Also draw the output waveforms for  $f/3$  frequency.
- 4. Attempt any THREE of the following:** **12**
- a) Explain with neat sketch, the working of Three phase half wave controlled rectifier.
  - b) For a three phase full controlled bridge rectifier answer the following :
    - (i) Draw circuit diagram
    - (ii) Draw output voltage waveform for  $\alpha = 60$ .
  - c) Draw the neat sketch of Three phase pulse output firing circuit using phase locked oscillator.
  - d) Describe six pulse half wave controlled rectifier with neat sketch.
  - e) Explain three phase full bridge inverter, with neat sketch.

**5. Attempt any TWO of the following:****12**

- a) For class C chopper answer the following
  - (i) Draw circuit diagram.
  - (ii) Interpret associated waveforms.
- b) State the types of Heat sinks used in power electronics applications and explain any one.
- c) Compare series and parallel inverter based on
  - (i) Circuit diagram
  - (ii) Position of commutating components
  - (iii) Type of commutation
  - (iv) Nature of output voltage waveform.
  - (v) Transformer
  - (vi) RLC circuit.

**6. Attempt any TWO of the following:****12**

- a) Explain the function of four-quadrant chopper with the help of quadrant diagram.
  - b) Describe Mc. Murry Bedford half bridge inverter with the help of associated waveforms.
  - c) Identify the circuit to get three phase output voltage waveform at load from a DC source. Draw circuit diagram and explain with the help of waveforms.
-