

22529

21222

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

15 minutes extra for each hour

- Instructions :**
- (1) Answer each next main Question on a new page.
 - (2) Illustrate your answers with neat sketches wherever necessary.
 - (3) Figures to the right indicate full marks.
 - (4) Assume suitable data, if necessary.
 - (5) Use of Non-programmable Electronic Pocket Calculator is permissible.

Marks

1. Attempt any FIVE :

10

- (a) List out the role of power system engineer in analysis of given power system.
- (b) Draw neat labelled equivalent circuit of alternator.
- (c) State the impact of resistance and capacitance on performance of transmission line.
- (d) State the four factors that governs the skin effect in transmission line conductors.
- (e) Define the generalised constant $A \times B$ refer to transmission line.
- (f) Define the generalised circuit applicable to transmission line.
- (g) List out any two reactive power compensating equipment used in the power system.

2. Attempt any THREE :

12

- (a) Summarise the advantages of per-unit system in power system analysis.
 (b) Calculate the Self GMD and Mutual GMD for following conductors configuration.

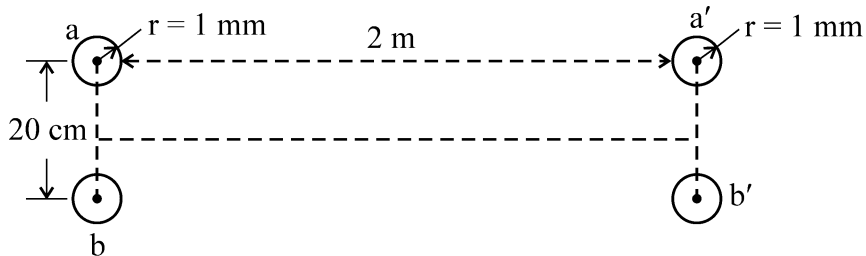


Fig. 1

- (c) Determine the GCC for medium transmission line represented by 'T' network. Assume $Y = \text{total admittance / ph.}$ & $Z = \text{total impedance / ph.}$
 (d) Describe the benefits of generalised circuit representation of transmission line.

3. Attempt any THREE :

12

- (a) Develop reactance diagram of following power system considering generator rating as base values.

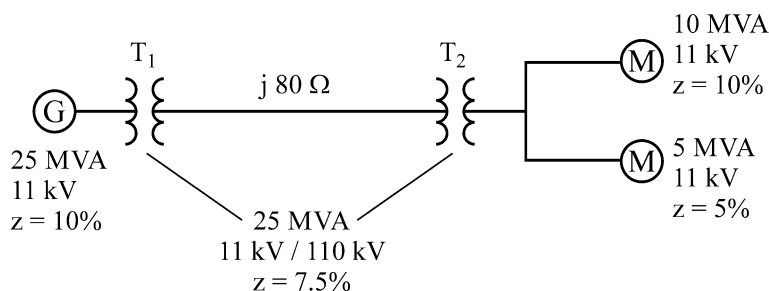


Fig. 2

- (b) Develop the equation for inductance of single phase line composed of solid conductors.
 (c) A three phase transmission line have total impedance $(10 + j 32) \text{ ohms/ph}$ and admittance $2.8 \times 10^{-4} \text{ s/ph}$. Calculate the GCC considering ' π ' network.
 (d) A 220 kV transmission line has GCC as $A = 0.75 \angle 0.2^\circ$, $B = 110 \angle 85^\circ \Omega$. Calculate real power at unity power factor that can be delivered when voltages at both ends of the tr. line maintained constant.

4. Attempt any THREE :

12

- (a) Explain the different aspects of power system analysis.
- (b) Determine the GCC – $A \times B$ for the resultant network when two generalised circuits are connected in parallel.
- (c) Determine the Self GMD of following configured conductors.

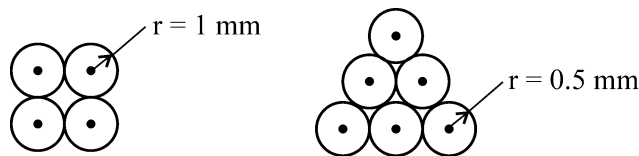


Fig. 3

- (d) Develop the condition for maximum real power flow at receiving end of the transmission line.
- (e) Evaluate the co-ordinates of the centre and radius of sending end circle diagram for a power system having following data :

$$A = 0.96 \angle 3^\circ, B = 50 \angle 73^\circ \Omega/\text{ph.}, V_{S_{l-l}} = 120 \text{ kV} \angle 2^\circ, V_{R_{l-l}} = 100 \text{ kV} \angle 0^\circ.$$

5. Attempt any TWO :

12

- (a) Calculate the total capacitance of each conductor of 3.3 kV, 3 phase 50 Hz, 50 km long transmission line composed of solid conductors of 20 mm diameter and are spaced at the corners of a triangle with 3 m, 5 m, 4 m sides.
- (b) Write the procedure to draw receiving end circle diagram.
- (c) A three phase 220 kV transmission line has $A = D = 0.9 \angle 0.2^\circ$, $B = 100 \angle 72^\circ \Omega$. Determine the max. power supplied at sending end when sending end voltage is maintained at 230 kV.

6. Attempt any TWO :

- (a) For a generalised circuit representation of transmission line prove that :

$$V_R = AV_S - BI_S$$

$$I_R = -CV_S + DI_S$$

- (b) Explain the need of reactive power compensation in power system. Suggest the suitable compensating equipment for following area :

- Load Center
- 300 km long transmission line
- Distribution substation

- (c) Evaluate the real power at the sending end 3-phase transmission line having GCC – $A = 0.98 \angle 3^\circ$ and $B = 105 \angle 72^\circ \Omega$, Power delivered is 50,000 kVA, 132 kV, 0.85 lag p.f. Load angle is 11° .
-