

312310

23242

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
  - (2) Answer each next main Question on a new page.
  - (3) Illustrate your answers with neat sketches wherever necessary.
  - (4) Figures to the right indicate full marks.
  - (5) Assume suitable data, if necessary.
  - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

1. Attempt any FIVE of the following :

10

- (a) Define EMF and state its unit.
- (b) State the meaning of linear and non-linear networks.
- (c) Define capacitance and state its unit.
- (d) State the values of permeability of free space and permeability of air.
- (e) Define reluctance and reluctivity.
- (f) State the expression to determine energy stored in a magnetic field.
- (g) State Fleming's right hand rule.

2. Attempt any THREE of the following :

12

- (a) State heating effect of electric current and write any two applications of it.
- (b) With a neat sketch explain the working of capacitor.



312310

[2 of 4]

- (c) Three capacitors having capacitances of  $3 \mu\text{F}$ ,  $5 \mu\text{F}$  and  $7 \mu\text{F}$ . Find total capacitance when they are connected in (i) Series (ii) Parallel.
- (d) State and explain statically and dynamically induced emfs.

**3. Attempt any THREE of the following : 12**

- (a) Draw the symbol and characteristics of ideal voltage source and practical voltage source.
- (b) State and explain Kirchhoff's current law.
- (c) Explain the construction of a lead acid battery with neat diagram.
- (d) Distinguish between electric and magnetic circuits (any four points).

**4. Attempt any THREE of the following : 12**

- (a) Calculate current, resistance and energy consumed by an electric iron rated  $230 \text{ V}$ ,  $2 \text{ kW}$  when used for 12 hours.
- (b) The resistance of copper coil increases from  $70 \Omega$  at  $12^\circ\text{C}$  to  $95.5 \Omega$  at  $60^\circ\text{C}$ . Find temperature coefficient of material at  $0^\circ\text{C}$ .
- (c) If  $200 \text{ V}$  source is applied to parallel combination of 3 capacitors of  $4 \mu\text{F}$ ,  $8 \mu\text{F}$  and  $12 \mu\text{F}$ . Calculate energy stored in each capacitor.
- (d) State and explain Faraday's law of electromagnetic induction.
- (e) List the different types of inductor with their applications.

**5. Attempt any TWO of the following : 12**

- (a)
  - (i) State Ohm's law and express it in the form of equation.
  - (ii) Compare series and parallel circuits of resistance (any four points).
- (b) Draw hysteresis loop for following materials :
  - (i) Permanent magnet
  - (ii) Steel alloy
  - (iii) Plastic

312310


[3 of 4]

- (c) An air cored coil 1.5 meter long, 8 cms. in diameter has 5000 turns then calculate :
- The inductance of the coil.
  - The magnetic energy stored when the current of 12 Amp passes through it.

6. Attempt any TWO of the following :

12

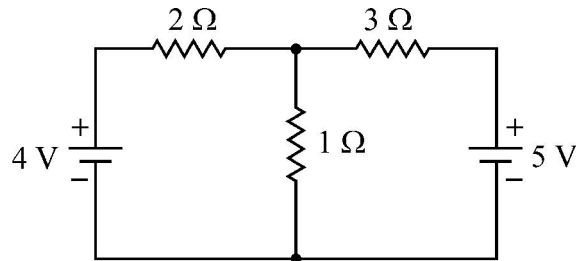- (a) Find current through  $1 \Omega$  resistance using Kirchoff's voltage law.



- (b) An iron ring of mean circumference 100 cm is uniformly wound with 500 turns of wire. Calculate the value of flux density to produce a current of 1.1 Amp in the ring. Assume  $\mu_r = 1200$ .
- (c) Derive the expression for the energy stored in magnetic field.

---

