

22346

22232

3 Hours / 70 Marks

Seat No.

| | | | | | | | |
|--|--|--|--|--|--|--|--|
| | | | | | | | |
|--|--|--|--|--|--|--|--|

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.
 - (8) Use of steam tables, logarithmic, Mollier's chart is permitted.

Marks

1. Attempt any FIVE of the following :

10

- (a) List the types of biasing of BJT. Which type of biasing is used mostly ?
- (b) Define thermal runaway.
- (c) Draw neat symbol of E-MOSFET and D-MOSFET.
- (d) What is coupling ? List the types of amplifier coupling ?
- (e) State Barkhausen's criteria for sustained oscillations.
- (f) List four applications of wave shaping circuits.
- (g) Define Line regulation and Load regulation.




- 2. Attempt any THREE of the following :** **12**
- (a) Draw the input and output characteristics of BJT in CE configuration and define the parameters input resistance and output resistance.
 - (b) Compare BJT and FET (any four points).
 - (c) Single transistor is operating as an ideal class B amplifier with $1\text{ k}\Omega$ load. A dc meter in the collector reads 10 mA . How much signal power is delivered to the load ?
 - (d) Draw and explain the working of UJT relaxation oscillator with neat diagram.
- 3. Attempt any THREE of the following :** **12**
- (a) Derive the relation between current amplification factor in CE and CB transistor configuration.
 - (b) Describe the working principle of E-MOSFET with neat diagram.
 - (c) Explain the operation of class-B push pull amplifier with neat diagram.
 - (d) The negative half cycles are to be clipped from the given input signal $v_i = 10 \sin \omega t$, name and draw the circuit with input-output waveform.
- 4. Attempt any THREE of the following :** **12**
- (a) Define the terms with respect to JFET :
 - (i) Pinch-off voltage
 - (ii) DC drain resistance
 - (iii) Transconductance
 - (iv) Amplification factor
 - (b) Explain the working principle of PNP transistor with suitable diagram.
 - (c) Draw the neat sketch of single stage BJT CE amplifier and explain the concept of phase reversal in this amplifier.

22346

[3 of 4]

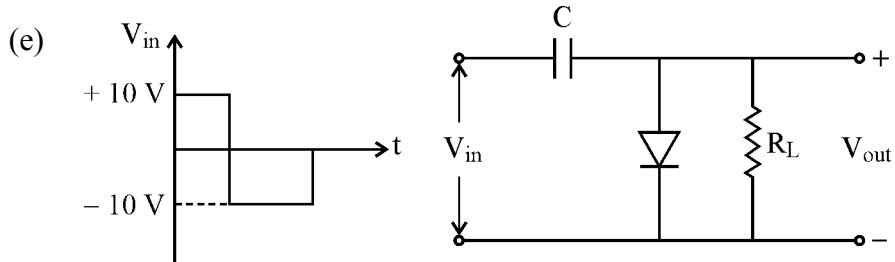- (d) The ac equivalent circuit of a crystal has these values : $L = 1\text{H}$, $C = 0.01\text{ pF}$.
 $R = 1000\ \Omega$ and $C_{in} = 20\text{pF}$. Calculate F_s and F_p of the crystal.



Sketch the wave shape of clamped output and name the above clamping circuit.

5. Attempt any TWO of the following :

12

- (a) Design a complete regulated power supply to give -12 V regulated output using IC 79XX. Write the function of rectifier and filter circuit used in the circuit.
- (b) State the need of biasing of the transistor. Draw circuit diagram of voltage divider bias and write the function of each component.
- (c) Calculate voltage gain A_F and input resistance R_{iF} in voltage series negative feedback amplifier. The voltage gain without feedback $A = 500$, input resistance without feedback $R_i = 3\text{ k}\Omega$ and feed back factor $\beta = 0.01$. Draw the block diagram of voltage series feedback connection.

P.T.O.

6. Attempt any TWO of the following :

12

- (a) Draw circuit diagram and frequency response of RC coupled amplifier. Write its drawbacks.
 - (b) Draw circuit diagram of RC integrator for a sinusoidal input. Derive the expression for output voltage. Draw the output waveform if the same circuit is connected to a rectangular wave generator.
 - (c) Draw the circuit of transistorised shunt voltage regulator and explain its working. Write any two drawbacks of this regulator.
-