

22526

22232

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Figures to the right indicate full marks.

Marks

1. Attempt any FIVE of the following : 10

- (a) State the use of proximity switch & pressure switch.
- (b) State any two benefits of automation.
- (c) State any two PICs available in market with no. of IO's.
- (d) Draw ladder diagram for AND gate.
- (e) Draw ladder diagram for XOR gate.
- (f) State the function of seal in circuit w.r.t. PLC.
- (g) Define SCADA.

2. Attempt any THREE of the following : 12

- (a) Explain the working of FWD-STOP-REV control circuit of an Induction motor.
- (b) Explain Digital output module of PLC.
- (c) Develop ladder diagram & wiring diagram of DOL starter.
- (d) Explain latching relay using PLC.



- 3. Attempt any THREE of the following : 12**
- (a) Explain down counter module with example.
 - (b) Explain the instruction T_{ON} and T_{OFF} .
 - (c) Develop Bottle filling system using Ladder diagram.
 - (d) Explain SCADA architecture with neat sketch diagram.
- 4. Attempt any THREE of the following : 12**
- (a) Explain solenoid valve with neat sketch diagram.
 - (b) Explain function of different parts of PLC.
 - (c) Explain any two input and output devices of automation.
 - (d) Develop ladder diagram & wiring diagram of DOL starter with OLR.
 - (e) Explain :
 - (i) Stepper motor control module
 - (ii) Communication module in PLC.
- 5. Attempt any TWO of the following : 12**
- (a) Draw control & power circuit diagram of conveyor control.
 - (b) Develop Traffic light control using ladder diagram.
 - (c) Compare the salient features of SCADA, PLC & DCS system.
- 6. Attempt any TWO of the following : 12**
- (a) Draw a ladder diagram for 3 motor operation for following condition :
 - (i) Start push button starts motor M_1 . After 15 seconds M_2 & M_3 starts.
 - (ii) Stop push button stops M_3 and after 15 seconds motor M_2 and M_1 .
 - (b) Explain IF-CLOSED, IF-OPEN & internal relay instructions.
 - (c) Explain PLC based water level controller with neat ladder diagram.
-