

17664

11920

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each Section on same / separate answer sheet.
 - (3) Answer each next main Question on a new page.
 - (4) Illustrate your answers with neat sketches wherever necessary.
 - (5) Figures to the right indicate full marks.
 - (6) Assume suitable data, if necessary.
 - (7) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (8) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. (A) Attempt any THREE : 12
- (a) List any four benefits of automation.
 - (b) Draw block diagram of PLC. List any two programming devices used for PLC.
 - (c) Define following terms related to PLC :
 - (i) Operating cycle of PLC
 - (ii) Speed of execution
 - (d) List any four precautions taken while placing PLC in an enclosure.
- (B) Attempt any ONE : 6
- (a)
 - (i) Give classification of PLC.
 - (ii) Compare fixed and modular PLC (any four points)
 - (b) Draw block diagram of analog input module. Describe function of each block.

- 2. Attempt any TWO :** **16**
- (a) Describe the following speciality input modules :
 - (i) Stepper motor control module
 - (ii) Thermocouple module
 - (b) Draw ladder diagram for blinking of LED with delay of 10 seconds.
 - (c)
 - (i) Draw block diagram of AC output module.
 - (ii) Draw wiring diagram to connect AC load to PLC. Specify which type of O/P module can be used.
- 3. Attempt any FOUR :** **16**
- (a) List any four specifications of AC input module.
 - (b) List any four automation tools. Describe DCS.
 - (c) Give truth table and draw ladder diagram for NAND and EX-OR Gate.
 - (d) Give classification of PLC programming languages.
 - (e) Describe how noise suppression is done during PLC installation.
- 4. (A) Attempt any THREE :** **12**
- (a) Describe why grounding is necessary for PLC during installation.
 - (b) Draw instruction format of Up-counter. Describe function of each bit.
 - (c) Give details of trouble shooting in PLC system.
 - (d) Describe the term redundancy in PLC with diagram.
- (B) Attempt any ONE :** **6**
- (a) Draw and describe PLC as sinking and sourcing input device.
 - (b) Draw logic diagram and ladder diagram for 4 : 1 multiplexer.

5. Attempt any TWO :**16**

- (a) Draw block diagram of DC input module. Describe function of each block.
- (b)
 - (i) Describe the function and organization of RAM and ROM in PLC.
 - (ii) List any four data handling instructions used in PLC. Describe any one instruction in details.
- (c) Draw ladder diagram for traffic control system. (Assume suitable data)

6. Attempt any FOUR :**16**

- (a) Draw ladder diagram for given Boolean equation :
 - (i) $Y = \bar{A} BC + \bar{A} \bar{B} \bar{C} + A B C$
 - (ii) $Y = A \bar{B} C (C + D)$
 - (b) Draw ladder diagram for following conditions :
 - if $Y > N7$: 3 switch ON motor 1.
 - if $Y \leq N7$: 3 switch ON motor 2.
 - (c) Write general format for PID instruction.
 - (d) Describe I/O addressing in PLC.
 - (e) Draw format of ON Delay timer with waveforms.
-

