

22213

11920

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* –
- (1) All Questions are *Compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

- 1. Attempt any FIVE of the following: **10****
- a) Draw symbols of zener diode and LED
 - b) List the types of filters.
 - c) Draw symbol of NPN and PNP transistor
 - d) Define the term line regulation and load regulation.
 - e) Suggest the diode material suitable to rectify 0.5V AC signal.
 - f) Draw circuit of zener diode as a voltage regulator.
 - g) Draw truth table for logic gates represented by following IC's:
 - (i) IC 7400
 - (ii) IC 7402

P.T.O.

- 2. Attempt any THREE of the following:** **12**
- a) Draw and explain V-I characteristics of a PN Junction diode.
 - b) Explain shunt capacitor filter with the help of circuit diagram and waveform.
 - c) Compare CB, CE, CC configuration of BJT with respect to following points.
 - (i) Input Impedance
 - (ii) Output Impedance
 - (iii) Current gain
 - (iv) Voltage gain
 - d) Draw the functional block diagram of IC 723. State any two features of IC 723.
- 3. Attempt any THREE of the following:** **12**
- a) Draw block diagram of DC regulated power supply and explain function of each block with waveforms.
 - b) State and explain Barkhausen's criteria required for Oscillations.
 - c) State the need of biasing of BJT. List types of biasing.
 - d) A half wave rectifier is used to supply 50V DC to a resistive load of $1K\Omega$. The diode has a resistance of 10Ω . Calculate required input AC voltage.
- 4. Attempt any THREE of the following:** **12**
- a) Draw the circuit diagram of crystal oscillator and give the basic principle of piezoelectric crystal.
 - b) Compare half wave rectifier and full wave rectifier with respect to:
 - (i) PIV
 - (ii) Ripple Frequency
 - (iii) TUF
 - (iv) Efficiency

- c) In a common base configuration, current amplification factor is 0.8. If emitter current is 2mA, determine the value of base current.
- d) Describe the operating principle of LASER diode with constructional diagram.
- e) List out advantages and disadvantages of bridge rectifier.

5. Attempt any TWO of the following: 12

- a) Draw frequency response of two stage RC coupled amplifier. Write procedure to calculate bandwidth and state any two methods to improve bandwidth.
- b) State the need of regulator. Draw circuit diagram of DC regulated dual power supply for $\pm 12V$ using IC's 78XX and 79XX
- c) State race around condition. Draw the circuit diagram of master slave JK flipflop using NAND gates and explain it's operation.

6. Attempt any TWO of the following: 12

- a) List two applications of oscillator. Calculate the frequency of oscillation for RC phase shift oscillator for the components values $R = 8.2K\Omega$, $C = 0.01\mu F$, $R_1 = 1.2K\Omega$, $R_F = 39K\Omega$.
 - b) Define transistor. Explain how transistor works as a switch with input and output waveforms.
 - c) Draw implementation of EX-OR and EX-NOR logic gate using NAND and NOR gate.
-