

# 22433

11920

3 Hours / 70 Marks


Seat No.

|  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|

- Instructions* –
- (1) All Questions are *Compulsory*.
  - (2) Answer each next main Question on a new page.
  - (3) Illustrate your answers with neat sketches wherever necessary.
  - (4) Figures to the right indicate full marks.
  - (5) Assume suitable data, if necessary.
  - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
  - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

1. Attempt any FIVE of the following: 10
- a) Draw dual input unbalanced output configuration of differential amplifier.
  - b) Draw ideal and practical transfer characteristics of op-amp.
  - c) Draw circuit diagram of op-amp based filter which provides the following response. Name the circuit. Refer Figure No 1.

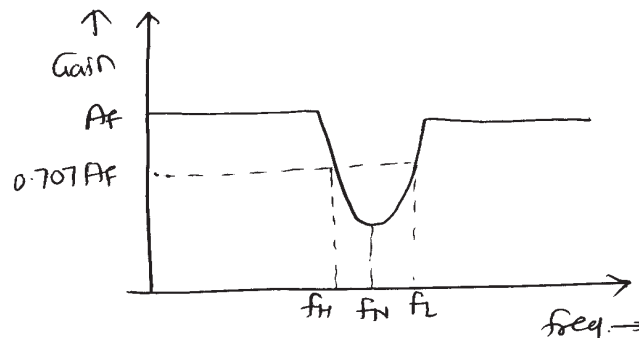

**Fig. No. 1**

P.T.O.

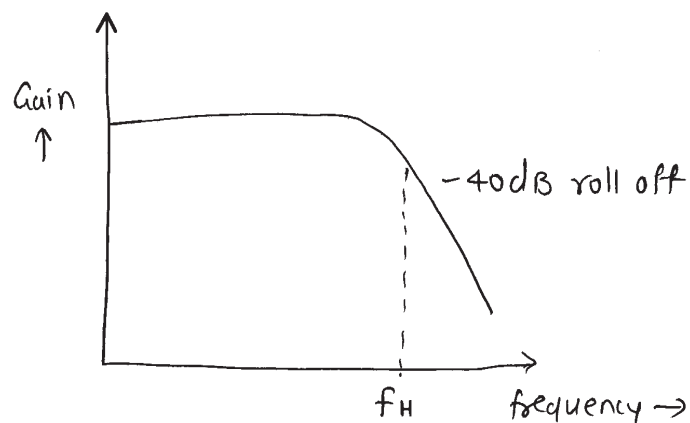
- d) Draw Astable multivibrator circuit using IC555.
- e) Define cut off frequency and Q factor with respect to filter circuit.
- f) Draw circuit diagram of practical op-amp differentiator.
- g) Draw circuit diagram of V to I converter.

**2. Attempt any THREE of the following: 12**

- a) Draw neat diagram of antilog amplifire and explain its working.
- b) Derive an expression for output voltage of inverting amplifier. Also draw circuit diagram.
- c) Design first order Low pass filter with 1 KHz cut off frequency and pass band gain 3.
- d) Describe the operation of instrumentation amplifier using three op-amp.

**3. Attempt any THREE of the following: 12**

- a) Explain virtual ground and virtual short.
- b) Using op-Amp draw the circuit to show the out-put  $V_o = 3(V_1 - 2V_2)$  where  $V_1$  and  $V_2$  are input voltages.
- c) Design and draw op-amp based phase shift oscillator for frequency 200Hz.
- d) Suggest and draw op-amp based circuit using butter worth filter to fulfill following response. Refer Figure No2.

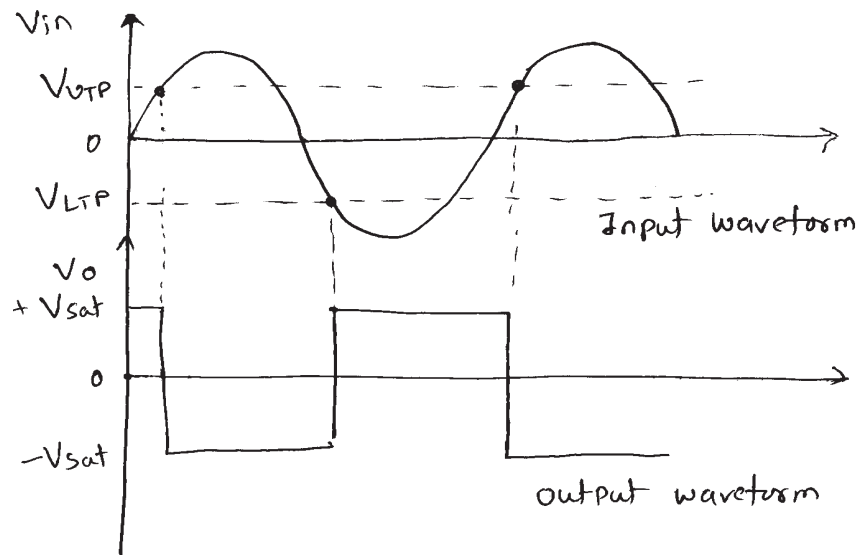


**Fig. No. 2**

4. Attempt any THREE of the following:

12

- Draw and explain precision rectifier using op-amp.
- If  $R_1=2\text{ k}\Omega$ ,  $R_f=100\text{ k}\Omega$ ,  $V_{cc}=\pm 15\text{ V}$  and RMS input voltage,  $V_i=20\text{ mV}$ . Calculate output voltage in inverting and non-inverting mode.
- Identify the following waveforms. Label the circuit name and draw the circuit diagram for the same. Refer Figure No 4.

Fig. No. 3

- Draw band pass and band stop filter using op-amp.
- Draw and describe the circuit diagram of Wien Bridge Oscillator using IC 741.

**5. Attempt any TWO of the following: 12**

- a) Draw single input unbalanced output differential amplifier and describe its operation. Draw ideal differential amplifier.
- b) Draw circuit diagram of bistable multi vibrator using IC555. Explain its working with neat waveforms.
- c) For a schmitt trigger with op-amp find threshold voltage  $V_{UTP}$  and  $V_{LTP}$  when  $R_2=150\text{k}\Omega$ ,  $R_1=100\text{k}$   $V_{in}=500\text{mv}$ . Sine wave saturation voltage= $\pm 15\text{V}$ . Draw diagram and waveform.

**6. Attempt any TWO of the following: 12**

- a) Draw the circuit diagram and output waveform for sine and square wave input for output voltage

$$V_o = \frac{-1}{Rc} \int_0^t V_{in} dt + c$$

- b) Draw and derive the expression for gain of open loop and closed loop configuration of op-amp in inverting mode.
  - c) Explain the operation of Notch filter with neat circuit diagram and waveform.
-