

17302

11920

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
  - (2) Answer each next main Question on a new page.
  - (3) Illustrate your answers with neat sketches wherever necessary.
  - (4) Figures to the right indicate full marks.
  - (5) Assume suitable data, if necessary.
  - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
  - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

1. (A) Attempt any SIX :

12

- (a) Give the speciality of zener diode. State its 2-3 applications.
- (b) Why NAND and NOR gates are called as universal gate ? Draw AND gate using NAND gates only.
- (c) Draw symbol of NPN transistor and state three configurations of transistor. (BJT)
- (d) Define counter. State four applications of counter.
- (e) Draw pin diagram of Op-Amp IC-741.
- (f) Give two examples of :
  - (i) Electrical Transducer
  - (ii) Mechanical Transducer

- (g) State important specification parameters of ADC. (any two)
- (h) List various types of CNC machines.

**(B) Attempt any TWO :****8**

- (a) Define rectifier. Draw circuit diagram and input-output waveforms of bridge type full-wave rectifier.
- (b) Describe how Op-Amp is used as adder using circuit diagram and output voltage equation.
- (c) Draw simple block diagram of CNC machine and describe in short.

**2. Attempt any FOUR :****16**

- (a) Name the circuit used in rectifier to minimize ripple. List the types of this circuit with simple circuit diagram.
- (b) Compare LED and photo diode with four points.
- (c) Draw circuit diagram of two stage RC coupled amplifier using BJT and state function of each component in short.
- (d) Draw a labelled pin diagram of IC 555 and state function of each pin in short.
- (e) Compare microprocessor and microcontroller with help of four points. Give two applications of each.
- (f) Describe ADC and DAC w.r.t. their needs and list two applications of each.

**3. Attempt any FOUR :****16**

- (a) Compare intrinsic and extrinsic semiconductors with the help of four important points.
- (b) State the need of multi-stage amplifier. List the types of multistage amplifier and give two advantages of each type.
- (c) State Barkhausen criteria for oscillations. List types of oscillator.

- (d) Define multiplexer. Draw logical symbol of 4 : 1 multiplexer with truth table and output logical equation.
- (e) Define transducer. State factors which are considered while selecting transducer for a particular application.
- (f) List various elements of mechatronic system and state 4-5 applications.

**4. Attempt any FOUR :****16**

- (a) Draw block diagram of regulated power supply and state function of each block in short.
- (b) Draw circuit diagram of CE configuration for NPN transistor and its output characteristics.
- (c) List the function of OR gate. Draw its logical symbol and write the truth table.
- (d) Define Data Acquisition System (DAS). Draw simple block diagram of single channel DAS and state function of each block in short.
- (e) List any four criteria for selection of PLC for an application and explain any one in short.
- (f) Define bistable multivibrator. Draw its circuit diagram using timer IC555.

**5. Attempt any FOUR :****16**

- (a) Draw block diagram of PLC and state which input/output devices are used in it.
- (b) Explain with diagram how BJT acts as an amplifier.
- (c) Draw circuit diagram of an inverting amplifier using Op-Amp. Calculate gain of  $R_f = 12 \text{ k}\Omega$  and  $R_i = 3 \text{ k}\Omega$ .
- (d) Describe basic SR flip-flop using NAND gates and truth table.
- (e) Compare BJT and FET with four key points.
- (f) Explain active and passive transducer with example.

**P.T.O.**

**6. Attempt any FOUR :****16**

- (a) Develop a ladder diagram for output Q to be ON when button A is ON or either button B or C are ON.
  - (b) Define Shift Register. State its types with simple diagram.
  - (c) State Piezo-electric effect used in crystal oscillator and write four features of crystal oscillator.
  - (d) State the function of half adder. Draw its logic circuit and truth table.
  - (e) Explain FMS in short with simple block diagram.
  - (f) Compare three configurations of BJT with four points.
-