

17329

11920

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each Section on same / separate answer sheet.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.

Marks

SECTION-I

1. Attempt any NINE of the following :

18

- (a) Define current and voltage with their units.
- (b) Define frequency and phase.
- (c) Give any two advantages of polyphase supply.
- (d) Define kVA rating of single phase transformer.
- (e) Write types of 3 ϕ Induction motor based on construction of rotor.
- (f) State the factors for selection of motor for different drives.
- (g) State the types of tariff.
- (h) State expression for active power, reactive power and apparent power for three phase circuit.
- (i) Define voltage ratio and current ratio of transformer.

[1 of 4]

P.T.O.

- (j) State the working principle of A.C. motor.
- (k) State two advantages of ELCB.
- (l) Name different types of safety tools.

2. Attempt any FOUR of the following :

16

- (a) Define the following terms and its relation with amplitude :
 - (i) RMS value
 - (ii) Average value
- (b) Three resistance of 30Ω each are connected in delta across a 3ϕ 400 V AC supply. Draw the circuit. Find phase current, line current, line voltage and phase voltage.
- (c) Explain construction and working principle of transformer with diagram.
- (d) Define slip and slip-speed. Draw speed torque characteristics of 3 phase I.M.
- (e) State applications of following lamps :
 - (i) CFL lamps
 - (ii) Sodium vapour lamps
- (f) What is earthing ? Why it is necessary ?

3. Attempt any FOUR of the following :

16

- (a) State first aid measure to be given to person who has received electric shock.
- (b) Draw and explain working principle of Direct on-line starter.
- (c) With neat sketch explain working of Auto transformer. List two specification of it.
- (d) Describe two different types of enclosures.
- (e) Derive emf equation expression of the transformer.

SECTION-II

4. Attempt any FOUR of the following : 16

- (a) Explain the working principle of UJT. State its applications.
- (b) Explain Zener diode as a voltage regulator.
- (c) Explain with diagram Op-Amp as an non-inverting amplifier.
- (d) Draw circuit diagram of full wave bridge type rectifier. Explain its operation with waveform.
- (e) Draw the circuit diagram of RC coupled amplifier and also draw its frequency response.
- (f) Convert the following :
 - (i) $(416)_{10} \rightarrow ()_2$
 - (ii) $(3000.45)_{10} = ()_8$

5. Attempt any THREE of the following : 18

- (a)
 - (i) Compare between conductor and insulator. (Any three point)
 - (ii) Explain working of P-N junction diode.
- (b) Draw and explain circuit of centre tapped full wave rectifier with π filter and draw its input and output waveforms.
- (c) Explain op-amp used as an adder with expression.
- (d) Design all basic gates using NOR gate only.

6. Attempt any FOUR of the following : $4 \times 4 = 16$

- (a) Draw symbol of
 - (i) Photo-diode
 - (ii) LED
 - (iii) BJT
 - (iv) UJT

P.T.O.

- (b) Define line and load regulation.
 - (c) Explain transistor as a switch with suitable circuit diagram.
 - (d) Draw symbol and truth table of
 - (i) EX-OR gate
 - (ii) NAND gate
 - (iii) OR gate
 - (iv) AND gate
 - (e) Define Oscillator. State the conditions for sustained oscillations.
 - (f) Give comparison between CB, CC and CE configuration.
-