

SUMMER – 2022 EXAMINATION

Subject Name: Automotive Electrical & Electronics Systems

Subject Code:

22651

Model Answer

Important Instructions to examiners:

- 1) The answers should be examined by key words and not as word-to-word as given in the model answer scheme.
- 2) The model answer and the answer written by candidate may vary but the examiner may try to assess the understanding level of the candidate.
- 3) The language errors such as grammatical, spelling errors should not be given more Importance (Not applicable for subject English and Communication Skills.)
- 4) While assessing figures, examiner may give credit for principal components indicated in the figure. The figures drawn by candidate and model answer may vary. The examiner may give credit for any equivalent figure drawn.
- 5) Credits may be given step wise for numerical problems. In some cases, the assumed constant values may vary and there may be some difference in the candidate's answers and model answer.
- 6) In case of some questions credit may be given by judgement on part of examiner of relevant answer based on candidate's understanding.
- 7) For programming language papers, credit may be given to any other program based on equivalent concept.
- 8) As per the policy decision of Maharashtra State Government, teaching in English/Marathi and Bilingual (English + Marathi) medium is introduced at first year of AICTE diploma Programme from academic year 2021-2022. Hence if the students in first year (first and second semesters) write answers in Marathi or bilingual language (English +Marathi), the Examiner shall consider the same and assess the answer based on matching of concepts with model answer.

Q.	Sub	Answer	Marking		
No.	Q.		Scheme		
	Ν.				
1		Attempt any FIVE of the following	10		
	a	List four types of circuit defects	02		
		Answer:- (¹ / ₂ mark for each type)			
		i) Open circuit			
		ii) Short circuit	¹ ⁄2 mark for		
		iii) Short to ground	each type		
		iv) Voltage drop (Undesired Resistance in connection)			
	b	Interpret the function of a buzzer in automotive electrical system	02		
		Answer:- (2 marks for interpretation)			
		Function of buzzer in an automobile is to warn the driver about possible safety hazard by	02		
		an audio signal. Seat belt, Speed limit and similar safety provisions are made to avoid			
		possibility of hazard to passengers. If these are not followed, the driver is warned through			
		an audio signal. Driver is supposed to take relevant corrective action. Buzzer buzzes till			



	corrective action is taken.	
c	State four parameter of battery specification	02
	Answer: (Any four parameters, ¹ / ₂ mark each)	
	1. Voltage	
	2. Capacity	
	3. Dimension	¹ /2 mark
	4. Battery rating/s	each
	5. Dimension	
	6. Cycle life	
	7. Fast Charge Time	
	8. Energy Density	
	9. Polarity	
	10. Acid volume	
	11. Operating Temperature	
d	Defines and list types of battery ratings	02
	Answer: (¹ / ₂ mark for each rating, any four)	
	• Ampere-Hour Rating- Describes how much current the battery is able to supply for	
	10 or 20 hours	
	• Watt-Hour Rating- A Watt-hour is the voltage (V) that the battery provides	1/
	multiplied by how much current (Amps) the battery can provide for some amount of	¹ /2 mark for each rating,
	time (generally in hours).	any four
	• Reserve capacity - The reserve capacity rating measures the amount of time (in	
	minutes) a fully charged battery can - discharge at 25 amperes, while maintaining a	
	voltage of at least 1.75 volts per cell.	
	• Cold Cranking Amperes- It is the number of amperes that a battery delivers for 30	
	seconds at 0°F without the cell voltage falling below 1.2 volts	
	• Twenty Minutes Rating: it is the amount of current a battery can deliver - for 20	
	minutes, without dropping the cell voltage below 1.75 volts and temperature of 26°C	
	is maintained at the start of the test.	
e	List types of methods of triggering primary circuit	02
	Answer: (2 marks for correct types)	
	• Magnetic Pick up	2 marks for
		correct



		Hall effect generator	types
		Optical Pulse generator	
	f	Explain reasons for providing time delay in automatic headlight system	02
		Answer: (2 marks for correct explanation)	
		Time delay in automatic headlight system enables a vehicle to illuminate the way on a	2
		street /car parking garage, where there may be no lighting. It keeps the headlights turned	
		ON for a pre-set measure of time after the ignition is turned OFF.	
	g	Discuss functions of mass air flow sensor	02
		Answer: Mass air flow sensor is used to calculate the amount of air volume delivered to the engine. If the mass air flow sensor (MAF) doesn't work properly, it will cause ECU to miscalculate the fuel to be injected, causing additional damage to the engine.	2 marks
2		Attempt any three of the following	12
	a	Draw a neat labeled wiring diagram of windshield wiper in automobile	04
	h	V V	Correct Sketch – 3 marks Correct Labels – 1 mark
	b	Describe working of following switches in the vehiclei)Ganged switchii)Mercury Switch	04
		Answer: (2 mark each) Ganged switch:	
		Ganged switches allow one movement to move multiple contacts at the same time. A	
		headlight switch turns on parking lights and head lights even though these two circuits are	
		separated and do not come in contact. The movement is usually indicated by a dotted line	
		connecting the contacts of the switch.	









Mercury Switch:

Mercury is very good Conductor of Electricity. In mercury switch, Capsule is partially filled with mercury. One end of the capsule is two electrical contact points. The switch is attached to the hood or Luggage compartment lid. Normally mercury is in end opposite to contacts. When the lid is open the mercury flows to contact end and provides close circuit between the electrical contacts.



2

2



 C	Illustrate with simple circuit diagram the testing of open circuit defect using voltmeter	02
	Answer: (2 marks for explanation, 2 marks for circuit diagram)	
	The easiest method of testing a circuit is to start at the most accessible place and work	
	from there if the load components is easy accessible, test for voltage at the input to the	
	load	
	Remember, to get reliable test results, the load component must remain in the circuit.do	2
	not do any open circuit testing unless directed to in the service information. Use the	
	following procedure for locating the open:	
	1. With the switch in on position measure the voltage at point A, if the voltage is 10.5V	
	or higher check the ground side (point B) .if the voltage at point B is less than 10.5V	
	there is excessive resistance or an open in the ground circuit. If the voltage at point A	
	is less than 10.5V continue testing.	
	2. work towards the battery the test on connection for voltage. If the voltage is present at	
	a connection then the open ids between that connection and the previously tested	
	location. Used afused jumper wire to bypass that section to confirm the location of the open	
	3. If the battery voltage is present at point B the open is in the ground circuit. The used	
	fused jumper wire to connect the ground circuit then retest the components	
	Circuit diagram the testing of open circuit defect using voltmeter	
	12 V	2
	Fuse Light Switch Ignition Switch Batery Eig. Open Circuit Text	(Note: Circuit dia. Can vary and should be considered if caters to the procedure of test.)
	Fig- Open Circuit Test	



d	Describe the procedure of battery terminal test with help of schematic diagram	04
	Answer:- (2 marks for test procedure, 2 marks for circuit diagram)	
	 Procedure Checks for poor electrical connection between the terminals and the battery cables. 	
	• A voltmeter is used to measure voltage drop across terminals and cables.	
	• To perform a battery terminal test, connect the negative voltmeter lead to the	
	battery cable end. Touch the positive lead to the battery terminal.	
	• Keep the ignition or injection system disabled so that the engine will not start	2 marks for
	• Crank the engine while watching the voltmeter reading.	test
	• If the voltmeter reading is 0.5 volts or above, there is high resistance at the battery	procedure
	cable connection.	
	• This indicates that the battery connections need to be cleaned.	
	• A good, clean battery will have less than a 0.5 volt drop	2 marks for circuit diagram
	Figure: Battery Terminal Test	(Note:
	Voltmeter (Range 0 to 2 volts, DC)	Circuit dia. Can vary and should be considered if caters to the procedure of test.)
e	Illustrate with sketch current output test of an alternator. Predict the possible test results and their inference.	04
	Answer: (2 marks for test procedure & inference, 2 marks for circuit diagram)	
	• Start the engine and let it idle at about 1200 rpm while all other electrical	
	equipment's are off	2 marks for
	• Connect an amperage meter (or multi meter) across the battery terminals (or	test procedure
	positive terminal of alternator and negative terminal of battery)	& inference
	• Turn on all electrical equipment in the vehicle	
	• Check amp reading on the meter	



		• The reading should be near the maximum rated output of alternator (Find this					
		value in manufacturers catalogue)					
		• If the reading is too low (approx. about 10%), alternator is not functioning					
		properly					
		• If ammeter read $\pm 10\%$ of rated output current, then alternator is working well.					
		• If the reading is far below the rated value, then alternator is faulty and not					
		producing the required current. Replacement is the general recommendation.					
		Fig. Current output test of an alternator	2 marks for circuit diagram and (Note: Circuit dia. Can vary and should be considered if caters to the				
			procedure				
			of test.)				
Q3		Attempt any Three of the following	of test.) 12				
Q3	a	Attempt any Three of the following List any four components of starting system and state their functions.	of test.) 12 04				
Q3	a	Attempt any Three of the following List any four components of starting system and state their functions. Answer:	of test.) 12 04				
Q3	a	Attempt any Three of the following List any four components of starting system and state their functions. Answer: The components of starting system and their functions are as follows:(<i>any Four</i>)	of test.) 12 04				
Q3	a	Attempt any Three of the following List any four components of starting system and state their functions. Answer: The components of starting system and their functions are as follows:(<i>any Four</i>) 1. Battery: A starter battery supplies the current to starter motor, needed for engine	of test.) 12 04				
Q3	a	Attempt any Three of the following List any four components of starting system and state their functions. Answer: The components of starting system and their functions are as follows:(<i>any Four</i>) 1. Battery: A starter battery supplies the current to starter motor, needed for engine cranking.	of test.) 12 04 1 mark for				
Q3	a	Attempt any Three of the following List any four components of starting system and state their functions. Answer: The components of starting system and their functions are as follows:(any Four) 1. Battery: A starter battery supplies the current to starter motor, needed for engine cranking. 2. Ignition switch: It controls the current supplied to the solenoid and to the starter	of test.) 12 04 1 mark for each				
Q3	a	Attempt any Three of the following List any four components of starting system and state their functions. Answer: The components of starting system and their functions are as follows:(<i>any Four</i>) 1. Battery: A starter battery supplies the current to starter motor, needed for engine cranking. 2. Ignition switch: It controls the current supplied to the solenoid and to the starter motor for cranking. In starter mode, the switch provides current to solenoid and	of test.) 12 04 1 mark for each component				
Q3	a	Attempt any Three of the following List any four components of starting system and state their functions. Answer: The components of starting system and their functions are as follows:(<i>any Four</i>) 1. Battery: A starter battery supplies the current to starter motor, needed for engine cranking. 2. Ignition switch: It controls the current supplied to the solenoid and to the starter motor for cranking. In starter mode, the switch provides current to solenoid and the starter motor gets supply.	of test.) 12 04 1 mark for each component				
Q3	a	Attempt any Three of the following List any four components of starting system and state their functions. Answer: The components of starting system and their functions are as follows:(<i>any Four</i>) 1. Battery: A starter battery supplies the current to starter motor, needed for engine cranking. 2. Ignition switch: It controls the current supplied to the solenoid and to the starter motor for cranking. In starter mode, the switch provides current to solenoid and the starter motor gets supply. 3. Neutral safety switch: The switch provides continuity in starter circuit if the	of test.) 12 04 1 mark for each component				
Q3	a	Attempt any Three of the following List any four components of starting system and state their functions. Answer: The components of starting system and their functions are as follows:(any Four) 1. Battery: A starter battery supplies the current to starter motor, needed for engine cranking. 2. Ignition switch: It controls the current supplied to the solenoid and to the starter motor for cranking. In starter mode, the switch provides current to solenoid and the starter motor gets supply. 3. Neutral safety switch: The switch provides continuity in starter circuit if the transmission is in neutral or clutch is disengaged.	of test.) 12 04 1 mark for each component				
Q3	a	Attempt any Three of the following List any four components of starting system and state their functions. Answer: The components of starting system and their functions are as follows:(any Four) 1. Battery: A starter battery supplies the current to starter motor, needed for engine cranking. 2. Ignition switch: It controls the current supplied to the solenoid and to the starter motor for cranking. In starter mode, the switch provides current to solenoid and the starter motor gets supply. 3. Neutral safety switch: The switch provides continuity in starter circuit if the transmission is in neutral or clutch is disengaged. 4. Solenoid: Solenoid controls a larger cranking current with use of small current	of test.) 12 04 1 mark for each component				
Q3	a	Attempt any Three of the following List any four components of starting system and state their functions. Answer: The components of starting system and their functions are as follows:(any Four) 1. Battery: A starter battery supplies the current to starter motor, needed for engine cranking. 2. Ignition switch: It controls the current supplied to the solenoid and to the starter motor for cranking. In starter mode, the switch provides current to solenoid and the starter motor gets supply. 3. Neutral safety switch: The switch provides continuity in starter circuit if the transmission is in neutral or clutch is disengaged. 4. Solenoid: Solenoid controls a larger cranking current with use of small current carrying circuit that uses a movable core. The core is mechanically linked to the	of test.) 12 04 1 mark for each component				
Q3	a	Attempt any Three of the following List any four components of starting system and state their functions. Answer: The components of starting system and their functions are as follows:(<i>any Four</i>) 1. Battery: A starter battery supplies the current to starter motor, needed for engine cranking. 2. Ignition switch: It controls the current supplied to the solenoid and to the starter motor for cranking. In starter mode, the switch provides current to solenoid and the starter motor gets supply. 3. Neutral safety switch: The switch provides continuity in starter circuit if the transmission is in neutral or clutch is disengaged. 4. Solenoid: Solenoid controls a larger cranking current with use of small current carrying circuit that uses a movable core. The core is mechanically linked to the electrical contacts through some form of mechanical linkage.	of test.) 12 04 1 mark for each component				
Q3	a	Attempt any Three of the following List any four components of starting system and state their functions. Answer: The components of starting system and their functions are as follows:(any Four) 1. Battery: A starter battery supplies the current to starter motor, needed for engine cranking. 2. Ignition switch: It controls the current supplied to the solenoid and to the starter motor for cranking. In starter mode, the switch provides current to solenoid and the starter motor gets supply. 3. Neutral safety switch: The switch provides continuity in starter circuit if the transmission is in neutral or clutch is disengaged. 4. Solenoid: Solenoid controls a larger cranking current with use of small current carrying circuit that uses a movable core. The core is mechanically linked to the electrical contacts through some form of mechanical linkage. 5. Starter motor: Upon receiving current, motor initially provides adequately high	of test.) 12 04 1 mark for each component				



 	6. Starter drive: It ensures the starter motor engagement while cranking, and immediate disengagement upon engine starting	
b	Explain working of bendix drive with sketch	04
	<u>Answer: (</u> Diagram – 2 marks, Working – 2 mark)	
	Bendix Drive :	
	Working: Bendix Drive	
	1. When the motor starts, the armature shaft rotates causing the sleeve to rotate and	
	because the pinion cannot rotate due to unbalance weight, it moves axially towards	
	the motor till it is engaged with flywheel.	
	2. Further movement of the pinion is prevented by the collar attached on the sleeve	Working – 2 mark
	and because of this pinion has to start rotating.	2 mark
	3. As it is also mesh with engine flywheel, the flywheel is rotated and the engine	
	starts.	
	4. When the engine starts, it is flywheel that rotates the pinion and because of its	
	bigger size, the flywheel rotates the pinion much faster than the armature with the	
	result that the pinion backed out of mesh with the flywheel.	
	ARMATURE STARTING MOTOR COLLER FLY WHEEL	Diagram – 2 marks,
	Fig. Bendix Drive	
c	Explain working of computer controlled ignition system.	04
 	Answer: (Working - 2 marks, Equivalent diagram- 2 Marks) Working :- i. An ECU	Working - 2marks
	ii. Crankshaft speed and crankshaft position sensor.	211101185
	iii. Ignition coils	
	1. The system is generally used for four cylinder or six cylinder engines. The basic	
	principle is that of the "Lost Spark".	
	2. The distribution of the spark is achieved by using two double ended coils, which are	
	fired alternately by using ECU.	



The timing is determined by using information from a crank shaft speed and 3. crankshaft position sensors as well as some other sensors such as engine load, coolant temperature and detonation sensor etc. Other ensors DIS coil Equivalent ECU diagram- 2 Marks) DIS coil Crankshaft speed and position sensor Fig. Computer controlled ignition system 4. The coil pack (2 ignition coils for four cylinder engine) gets triggered twice in each cycle of operation by using ECU, so that flow of current through one of the two primary windings is stopped. 5. When the flow of current is stopped, the magnetic field in the primary winding collapses suddenly and a high voltage is produced in the secondary winding. 6. When one of the coils is fired, a spark is delivered to two companion cylinders, either 1 and 4 or 2 and 3 for four cylinder engine, at the end of compression and exhaust respectively. 7. The spark delivered to the cylinder on the compression stroke will ignite the mixture. The spark produced in the other cylinder will have no effect, as this cylinder will be 8. completing its exhaust stroke. d Justify the precautions in handling of ignition system using Hall effect sensor. 04 Answer: 4 In electronic ignition system using Hall effect sensor, ignition voltage up to 30 KV may be encountered. Under adverse conditions, such as moisture in the engine compartment, voltage spike can penetrate the insulation. If technician's bare hand comes in contact with it will cause severe electric shock. In order to avoid injury and damage to the electronic ignition system, it is necessary



		when working on engines equipped with an electronic ignition system, following	
		precautions should be taken.	
		1. When the engine is running, or getting cranked by the starter motor, do not touch	
		the high voltage line.	
		2. Disconnect /connect the wiring of the ignition system only when the ignition is	
		switched off.	
		3. A Hall switch gets triggered (and causes high voltage in the secondary circuit)	
		when the distributor shutter is pulled out of the gap between the permanent magnet	
		and Hall IC. So, the ignition switch should be turned off during assembly/	
		dismantling of system components.	
04		Attempt any three of the following	12
	a)	List the navigation system in automobile .Explain any one	04
		Answer: The Navigation system in Automobile	
		GPS - Global Positioning System	
		GPRS – General Pocket Radio Services	
		Clobal Positioning System (CPS)	1 for list
		Technology fulfills goals of accurate location navigation and asset tracking. It	
		makes automotive commute safer and easier	
		Working	
		1 A CPS receiver must be locked on to the signal of 4 or more satellites to calculate	3 mark for
		a 3-D position of user (latitude longitude and altitude) and track movement	Explanation
		2 The GPS satellites transmit signals to a GPS receiver. These receivers passively	
		receive satellite signals: they do not transmit and require an unobstructed view of	
		the sky so they can only be used affectively outdoors	
		3 CPS operations depend on a very accurate time reference, which is provided by	
		3. Of 5 operations depend on a very accurate time reference, which is provided by	
		4 Each GPS satellite transmits data that indicates its location and the current time	
		5. All GPS satellites synchronize operations so that these repeating signals are	
		5. All OLS satellites synchronize operations so that these repeating signals are	
		6 The signals moving at the speed of light arrive at a CDS receiver at elightly	
		different times because some setallites are further every then others	
		The distance to the CDS satellites are he determined by estimating the encoder	
		7. The distance to the GPS satellites can be determined by estimating the amount of	
		time it takes for their signals to reach the receiver.	









- 6. Remote controlled keyless entry systems are also available. They use a hand held transmitter attached as a key chain.
- 7. It can be operated within a range of 25 to 50 feet and from any direction. The operating is done by a button press, then driver door is unlocked, theft security is disarmed. During exit, lock button locks all doors.



Fig: Keyless Entry System Keypad



Fig: Remote Keyless Entry System Transponder



Describe working of an Electric two wheeler with layout. С **Answer:** (Working: 02 marks, Sketch=02marks) Power Battery Motor Batters onverter 02 Mechanical Link 0 al Electrical Link Unidirectional Electric User Throttle Demand Wheels Controller Iransu Pedal OR



	Working of Electric two wheeler	
	1. An electric two wheeler consist of a battery that provides energy, an electric motor	
	that drive the wheels, and a controller that regulates the energy flow to the motor.	
	2. Electric two wheeler is simple, high reliable, have lifetimes measured in millions	
	of kilometers, need no periodic maintenance, and cost significantly less per km to	
	operate. They are highly flexible as well, using electrical energy readily available	
	anywhere as input fuel.	
	3. The direct drive-train layout is used most widely to drive small electric scooters.	02
	4. In case of indirect drive. Mostly used on electric motorcycles,transmission,a chain or belt drive, or maybe a shaft drive unit are conventionally used on high capacity electric vehicles	
d	Explain with sketch throttle position sensor	04
	Answer: (Explaination-2, sketch=02)	
	<u>Throttle position sensor :</u>	
	1. This sensor is usually mounted on the throttle body.	02
	2. It senses the position of the throttle valve or butterfly valve and transmits the	
	information to the Engine control unit.	
	3. This sensor monitors how far down the accelerometer pedal is pushed and gives	
	the output current determining the position of the pedal.	
	4. The position of the pedal controls the airflow of the engine.	
	5. If the valve is wide opened, a large amount of air is supplied to the engine and	
	vice-versa.	
	6. The output given by this sensor, along with other sensors is transmitted to the	
	engine control unit, which decides the amount of fuel to be injected into the engine	
	accordingly.	
	Accelerator linkage V V Resistance material	02



5	a	Explain with neat sketch construction and working of	6 Marks
		i) Maxi Fuse ii) Relays	
		Answer: (Construction & working of maxi fuse and relay - 3 marks each)Maxi Fuse: (Sketch - 1 mark & description - 2 marks)	
		Maxifuse	Sketch – 1 mark & 2 marks for description of constructio n & working of maxi-fuse
		Figure: Typical Maxi Fuse	
		• A fuse is the most common circuit protection device in the electrical systems of vehicle.	
		• A fuse is placed in an automotive electrical circuit so that, when current flow	
		exceeds the rating of the fuse, it blows or blows out i.e. it are designed to turn off the	
		circuit that it protects.	
		• The size of the metal fuse element determines the rating. Excessive current cause's	
		excessive heat and that causes the circuit protector to open. Once a fuse blows, it must be replaced with a new one.	
		• The element in the fuse melts, opening the circuit and preventing the other	
		components of the circuit from being damaged by the over current. A fuse also	
		separates a number of circuits like starting circuit, ignition circuit, charging circuit	
		etc. thus failure of a fuse doesn't affect the other circuit.	
		• Maxi-Fuse is a fast-acting blade fuse, standard for vehicle circuit protection. These are also designed to provide predictable time delay and low heat dissipation	Sketch – 1
		 These fuses are color-coded for easy identification of fuse ratings. 	mark & 2 marks for
		• Maxi fuses are a large version of blade fuses and are used to replace fusible links in	description of
		many vehicles.	constructio
		• Max1 Tuses are rated up to 80 amperes or more.	working of relay



			Г
		Relay: (Sketch – 1 mark & description – 2 marks)	
		Operation	
		POWER CIRCUIT TO LOAD SOURCE CONTROL CIRCUIT	
		Figure: Schematic of Typical Relay	
		• A Relay is an electric switch that allows a small amount of current to control a high- current circuit.	
		• When the control circuit switch is open, no current flows to the coil of the relay, so the windings are de-energized.	
		• When the switch is closed, the current flows through the control coil, which is	
		wrapped around an iron core. The iron core intensifies the magnetic field, the coil is	
		energized, turning the soft iron core into an electromagnet.	
		• The magnetic field attracts the upper contact arm and pulls the armature down,	
		closing the contacts and allowing power from the power source to go to the load.	
		• This closes the power circuit contacts, connecting power to the load circuit.	
		• When the control switch is opened, current stops' flowing in the coil and the electromagnet disappears.	
		• This releases the armature, which breaks the power circuit contacts.	
		• The purpose of relay is to control a load circuit with the use of small current carrying control circuit.	
		• It saves the size of wiring connected to the switches and reduces weight.	
5	b	Explain with neat sketch construction of Lead Acid Battery	6 Marks
		Answer: (Construction – 4 marks, Equivalent Fig/ Diagram - 2 marks)	
		Construction of lead acid battery:	
		A battery consists of number of cells, generally six for 12V battery. Each cell consists of	
		positive and negative plates separated by a separator and connected in series with	



positive and negative terminals of battery respectively. The plates are immersed in a solution of sulfuric acid, which acts as electrolyte. Each plate consists of a grid upon which is attached. The active material, lead dioxide on the negative plates, pure lead on the positive plates.



 $\begin{array}{c} Descriptio\\ n \ of\\ constructio\\ n-4\\ marks. \end{array}$

Equivalent

Diagram -2 marks

Fig/

Figure: Typical construction of Lead Acid Battery

The lead acid batteries are made of five basic components:

- 1. **Positive and negative internal plates:** The positive and negative plates are made up of lead material. The grid has horizontal and vertical grid bars that intersect at right angles. An active material made from ground lead alloys (usually Antimony) oxide, acid, and material expanders is pressed into the grid in paste form. About 5% to 6% antimony is added to increase the strength of the grid.
- 2. **Plate separators:** Plate separators are made of micro porous synthetic material. Many batteries have envelope type separators that retain active materials near the plate.
- 3. **Electrolyte:** Electrolyte is a dilute solution of sulfuric acid and water, better known as battery acid. Electrolyte solution consists of 64% water and 36% sulphuric acid, by weight. Electrolyte is both conductive and reactive.
- 4. A resilient plastic container: The battery case is made of polypropylene, hard rubber and plastic base materials. Battery case must be capable of withstanding temperature extremes, vibration and acid absorption. Provision in container for cell elements sit on raised supports in the bottom of the case.
- 5. Lead terminals: The connection point between the battery and whatever it powers.



		Some batteries a	re top terminal batteries they	have the two main terminals or posts	
		Some batteries a	re top-terminal batteries – tiley	have the two main terminals of posts	
		in the cover. Th	ne positive terminal post is lar	ger than the negative terminal post.	
		Other batteries a	re side-terminal batteries. They	have the terminals on the side of the	
		battery.			
5	С	Give probable caus i) corroded battery ii) reading of voltag	e & remedies for following tro bracket ge on individual cell differ	bubles	6 Marks
		Answer: (Causes &	remedies for troubles/defect –	3 marks for each defect)	
		Defect	Cause	Remedy	
		Corroded battery bracket	Over filling of battery electrolyte	Avoid overfilling of battery electrolyte	The marks should be awarded to
			• Over charging of battery than the specified limit of the battery.	 Regularly clean battery brackets Apply anti rust or anti 	causes & remedies
			• More Moisture content around battery bracket	 To avoid overcharging of battery adjust voltage 	other than mentioned here in the answer.
				regulator of an alternator	
		Reading of voltage on individual cell	• The battery plates may be defective because of loss of active material	• Defective battery should be replaced by one of the same rating.	
		differ	 Short circuiting of battery cells 	• Visually inspect the condition of battery plates.	
			 Open circuit cells 	• If the battery is in poor state, it may be replaced.	
6	a	"Computer contro ignition system." Ju	olled Ignition system is bett ustify your answer.	ter as compared to conventional	6 Marks
		Answer: (Any six ju	ustification points – 1 marks ea	uch)	
		Sl. Parameters	s Computer Controlled Ig System	nition Conventional Ignition System	
		1 Construction	 The computer corrignition system general not reduce the performative engine because it do use mechanical device works electrically works electrically works from crankshaft. Breaker point has 	 The conventional ignition system uses a distributor device to drive the breaker point, and to distribute the secondary coil voltage to each spark plug. This distributor 	Any other suitable justificatio n or points may be awarded with 1 mark for each



			replaced using a transistor while the distributor is replaced with an ignition coil module.	the crankshaft engine, so it can be said that conventional ignition systems somewhat reduces the engine's performance.	justificatio n.
	2	Servicing and Maintenance:	The Computer controlled ignition system does not require adjustment as in conventional ignition. There is no moving part in computer controlled ignition. So it only relies on the quality of electronic component materials. Therefore less wear and tear of parts.	The conventional ignition systems use breaker points to trigger induction on the coil. In some time, the opening angle of the breaker point will shift because this is one of the moving parts and there is definitely a wear usage. So it needs an adjustment called dwell angle adjustment. Due to maintenance problems, carbon deposits on spark plug reduce the fuel efficiency.	
	3	Operation:/Co mbustion quality:	 The higher the engine RPM, the faster the sparking interval. The faster the sparking interval. The faster the induction interval on the coil. In computer controlled ignition, it has at least two ignition coil and has transistor according to the number of spark plugs. So that the induction interval for each ignition coil is not too fast even at high RPMs. it keeps the fire produced stable. Noiseless operation at higher speed optimum ignition timing can be achieved as per ignition module. Detonation can be avoided using detonation sensor 	 The conventional ignition only has one ignition coil and one breaker point that will work at intervals according to the induction interval on the coil. So, when the RPM is high, the induction of the ignition coil is less than the maximum so that the voltage produced is also relatively lower. It creates some noise at higher speed. Ignition timing can be varied as per engine speed and and engine load. But is not efficient.Detonation can not be avoided. 	



		4	Power Output: Fuel Efficiency: Service life of components	 It does not use mechanical distributors to distribute secondary voltage, but use a single coil/ coil pack where each coil /coil pack will be connected directly to each spark plug. It makes the connection shorter and no voltage is wasted, so the secondary voltage is completely used to ignite air fuel mixture. It is very effective and saves electricity because no voltage is wasted. More power output The above factors results in higher efficiency. 	 It does use mechanical distributors to distribute secondary voltage which results in longer path and there are chances of waste of secondary voltage. It is not effective and do not saves electricity because of waste of voltage at the various places in the ignition system such as breaker plate, breaker points etc. Low power output The above factors reduces the efficiency. 	
			components	more.	components of system is less	
6	b	List & explain any one electronic fuel injector testing types.		6 Marks		
		Answ	er: (List of electr	ronic fuel inject test- 2 marks & ex	planation of any one test of	
		electr	onic fuel injector	- 4 marks)		
		Follow	wing is the list tes	ts of Electronic Fuel Injector: (2 mar	rks)	Marks
			1. Sound test			should be awarded to
			2. Spray test			any other
			3. Voltage drop	p test		fuel
			4. Fuel Flow te	est		injector testing
			5. Ohmmeter t	est.		other than
		• So	ound test for test	ing electronic fuel injector:		specified in this
	The use of electronic fuel injectors is a sophisticated way to provide the right fuel and ai			provide the right fuel and air	model	
		mix to	o an engine for a v	vehicle. The small cylindrical fuel in	jectors play a specific role in	allswei
		a larg	er fuel intake sys	stem, along with other elements like	e the fuel pump and the fuel	
		tank.	Over time, fuel	injectors may need to be mainta	ined or checked for proper	



The following is the test Procedure for sound test for electronic fuel injector:		
0	The electronic fuel injection system relies on electronic signals that control how	
	these items operate	
0	Along with checking a fuel injector electronically, you can listen for certain kinds	
	of sounds that will tell you when a fuel injector might not be working correctly	
0	A clunking sound or similar warning sound may show that the fuel injector is not	
	functioning the way it should be	
0	If the injector electrical leads are difficult to access, an injector power balance test	
	is hard to perform. As an alternative, start the engine and use a technician	
	stethoscope to listen for correct injector operation	
0	A good injector makes a rhythmic clicking sound as the solenoid is energized and	
	de-energized several times each second	
0	If clunk- clunk instead of steady click-click is heard, chances are the problem	
	injector has been found	
0	Cleaning or replacement is in order	
0	If an injector does not produce any clicking noise, the injector, connecting wires or	
	PCM may be defective	
0	When the injector clicking noise is erratic, the injector plunger may be sticking	
0	If there is no injector clicking noise, proceed with the injector resistance test and	
	light to locate the cause of problem	
0	If a stethoscope is not handy, use a thin steel rod, wooden dowel, or fingers to feel	
	for a steady on/off pulsing of the injector solenoid.	
	OR	
	Obmunistan taati	
• (Jnmmeter test:	



	Injector Ohm Meter		
	 An ohmmeter/multimeter is connected across the injector terminals to check the injector windings after the injector wires are disconnected. If the ohmmeter/multimeter reading is infinite, the injector winding is open. 		
	 All ommeter reading below the spectfied value indicates that the injector winding is shorted. A satisfied injector winding should have resistance between 0.3 to 0.4 ohms. Replace the injector if the results do not have the resistance as specified by manufacturer. 		
6 C	State the purpose of OBD II. Define the terms. i) Drive cycle ii) trip iii) worm up cycle		
	 Answer: (Purpose of OBD-II-3 marks- 1 marks each point & Defining terms - 1 mark each) Purpose of OBD-II (Any three- 3 marks): To enable the computer systems to monitor the ability of systems and components to maintain low emission The standardized data link connector, that allows for these tools to communicate with the PCM Identifying faults in the computer-controlled systems and to notify the driver by means of a malfunction indicator light if the emission related fault causes an increase in emission up to 1.5 times the allowable standard In addition a diagnostic trouble code (DTC) was stored in the computer's memory For easier diagnosis of a problem by a technician by using added information stored in the PCM It brings standardization in components and systems used by various automobile manufacturers. e.g. Data link connectors, data circuits, diagnostic tests and diagnostic trouble codes It provides almost complete engine control and also monitors parts of the chassis, body and accessory devices, as well as the diagnostic control network of a vehicle. i) Drive cycle 	03	



engine is then run until the system goes into closed loop. The drive cycle continues to	
include whatever specific operating conditions are necessary either to initiate and	
complete a specific monitoring sequence or to verify a symptom or verify a repair.	
OR	
A drive cycle may be defined as an engine startup and vehicle operation that allows the	
PCM to enter closed loop and allows all the monitors to complete their function.	
ii) Trip	
A trip is defined as an engine operating drive cycle that contains all of the necessary conditions for a particular test to be performed.	
OR	
A trip for a particular diagnostic test is defined as a key on and key off cycle in which all the enabling criteria for a given diagnostic test have been met.	
iii) Warm up cycle	
A warm-up cycle consists of engine start -up and vehicle operation such that the coolant temperature has risen greater than 40°C from the start-up temperature and reached at least 71°C. If this condition is not met, during the ignition cycle, the diagnostic tests may not run.	