



17213

21718

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) *All questions are **compulsory**.*
 - (2) *Answer **each** next main question on a **new** page.*
 - (3) *Illustrate your answers with neat sketches **wherever** necessary.*
 - (4) *Figures to the **right** indicate **full** marks.*
 - (5) *Assume suitable data, if **necessary**.*
 - (6) *Use of Non-programmable Electronic Pocket Calculator is **permissible**.*
 - (7) *Mobile Phone, Pager and any other Electronic Communication devices are **not** permissible in Examination Hall..*

Marks

1. Attempt **any ten** of the following :

20

- a) Define electronics. Give examples of active components.
- b) Draw the symbol of MOSFET.
- c) Write the application of Varactor Diode.
- d) State the need of multistage amplifier.
- e) Define static and dynamic resistance.
- f) Give the classification of I-C.
- g) Define filter. State its types.
- h) State the meaning of I_{dss} and $V_{gs(off)}$.
- i) Draw the symbol of Tunnel Diode and Schottky Diode.
- j) Name the examples of analog and digital IC. (Write any 1 of each).
- k) State the value of knee voltage for Si and Ge.
- l) Define variable capacitor. State its types.

2. Attempt **any four** of the following :

16

- a) Describe the working of Zener breakdown of Zener Diode.
- b) State the application of electronics (any 8).
- c) State the working of NPN transistor.

P.T.O.



- d) Draw the circuit diagram of single stage amplifier ? State the function of each components.
- e) State the working of Tunnel diode.
- f) Describe the working of crystal oscillator.
- 3. Attempt any four of the following : 16**
- a) Draw and explain the construction of LDR. Explain its working principle.
- b) Explain Zener diode as voltage regulator.
- c) Explain the FET parameters.
- d) Draw the block diagram of CE configuration with input and output characteristics.
- e) Draw DC load line on output characteristics of BJT and show different operating point on DC load line.
- f) State Barkhausen criteria for oscillator and describe its use.
- 4. Attempt any four of the following : 16**
- a) Draw constructional diagram of Schottky diode and explain it.
- b) Explain center type F.W.R. with input output waveform.
- c) Compare BJT and FET, (any 4 points)
- d) Draw block diagram of R-C coupled amplifier.
- e) Explain the working of II filter with its waveform generation.
- f) Define the following :
- 1) Bandwidth
 - 2) Power gain
 - 3) Current gain
 - 4) Voltage gain.
- 5. Attempt any four of the following : 16**
- a) Define the following :
- 1) Knee voltage
 - 2) Peak inverse voltage
 - 3) Reverse saturation current
 - 4) Maximum forward current.
- b) Compare H.W.R. and bridge type F.W.R. (Four points).
- c) Explain transistor as a switch.



[3]

17213

Marks

- d) Explain Reverse Bias of P-N junction.
- e) State the working of direct coupled amplifier with the help of its circuit diagram.
- f) Name the materials which are used for LED making. State LED's applications.

6. Attempt **any four** of the following :

16

- a) Compare PN Junction and Zener Diode. (4 points)
 - b) Describe Regulated power supply with block diagram.
 - c) State the relation between α and β . Define Q point.
 - d) Explain Astable multivibrator with its circuit diagram.
 - e) Draw the transfer characteristics of JFET and explain its significance.
 - f) An A.C. supply of 230 V is applied for F.W.R. through a transformer of turn's ratio 2 : 1 calculate
 - i) Direct current output voltage
 - ii) PIV of diode.
-