



17302

21718

3 Hours / 100 Marks

Seat No.

| | | | | | | | |
|--|--|--|--|--|--|--|--|
| | | | | | | | |
|--|--|--|--|--|--|--|--|

- Instructions :** (1) *All questions are compulsory.*
(2) *Illustrate your answers with neat sketches wherever necessary.*
(3) *Figures to the right indicate full marks.*
(4) *Assume suitable data, if necessary.*
(5) *Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.*

Marks

1. a) Attempt **any six** of the following :

12

- i) Draw symbols and label the terminal of :
 - 1) Photodiode
 - 2) UJT
- ii) Define intrinsic and extrinsic semiconductor.
- iii) List types of BJT and draw symbols of the same with neat labels.
- iv) Sketch pin diagram of IC 555 and label all pins.
- v) Draw logical symbol of 2 : 1 mux. and write its truth table.
- vi) What is transducer ? How they are classified ?
- vii) What is mechatronics ? Write its applications.
- viii) State types of real time mechatronics system.

b) Attempt **any two** of the following :

8

- i) Compare microprocessor and microcontroller (any four points).
- ii) Sketch circuit diagram of non-inverting op-amp. Calculate gain if $R_f = 25 \text{ K } \Omega$, $R_i = 5 \text{ K } \Omega$.
- iii) List any four advantages and applications of CNC system.

2. Attempt **any four** of the following :

16

- a) What is thermal runaway ? How it is avoided ?
- b) Draw instrumentation amplifier and write its output voltage equation.
- c) What is Barkhausen criteria ? Which type of feedback is used in an oscillator ? State types of oscillator.
- d) Define load regulation and line regulation.

P.T.O.



- e) Sketch symbol and write truth table of :
 - I) AND gate
 - II) NAND gate
- f) State function and application of robotic system.

3. Attempt any four of the following :

16

- a) Sketch pin out diagram of IC741, label all pins and state function of each pin.
- b) Compare RC coupling and transformer coupling w.r.t. following points.
 - I) Coupling element
 - II) Distortion
 - III) Voltage gain
 - IV) Applications.
- c) Draw circuit diagram input and output waveform of full wave bridge rectifier.
- d) Draw circuit diagram and waveform of bistable multivibrator using IC 555.
- e) Sketch block diagram for PLC and state functions of each block.
- f) Compare Active and Passive transducers on the basis of any four points.

4. Attempt any four of the following :

16

- a) State the principle of R-2R type DAC and write two applications of DAC.
- b) What is advance vehicle condition system ? Explain briefly.
- c) Write features of 8085 microprocessor.
- d) What is data logger ? State its applications.
- e) Draw ladder diagram for start stop logic with one input push button for start and one push button for stop and one output for motor to activate solenoid valve.
- f) Draw block diagram of regulated power supply and write function of each block.

5. Attempt any four of the following :

16

- a) What is AC signal conditioning ? State types of circuit used for AC signal conditioning.
- b) How transistor works as a switch ? Also draw a necessary circuit and waveform for it.
- c) Sketch circuit diagram for integrator using op-amp, also draw output waveform for square wave and sine wave input.
- d) Draw single channel data acquisition system and write function of each block.
- e) What is opto coupler ? Draw its circuit, also write its advantages.
- f) Draw decade counter using T Flip-flop and write its truth table.



[3]

17302

Marks

16

6. Attempt any four of the following :

- a) What is decoder ? Draw logical diagram of 3 : 8 decoder and its truth table.
 - b) Write the selection factors for PLC.
 - c) Draw CB and CE configuration for BJT.
 - d) Draw JK Flip-flop using NAND gate and what is the race around condition ?
 - e) Compare HWR and FWR with
 - 1) Diode use
 - 2) Output voltage
 - 3) Ripple factor
 - 4) Efficiency
 - f) What is triggering mechanism ? Give types of triggering with waveform.
-