



# 17329

21718

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :** (1) *All questions are compulsory.*  
(2) *Answer each Section on separate answer sheet.*  
(3) *Illustrate your answers with neat sketches wherever necessary.*  
(4) *Figures to the right indicate full marks.*  
(5) *Assume suitable data, if necessary.*  
(6) *Use of Non-programmable Electronic Pocket Calculator is permissible.*  
(7) *Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.*

**Marks**

SECTION – I

1. Attempt **any five** of the following :

**20**

- Define the following terms related with an AC quantity :
  - RMS value
  - Cycle
  - Phase
  - Frequency
- A balanced star connected load is supplied from 400 volt, 3-phase, 50 Hz supply. The resistance per phase is 25 ohm. Calculate
  - line voltage
  - phase voltage
  - line current
  - power consumed
- Explain construction and working principle of transformer with diagram.
- Explain with diagram the working of universal motor and state its two application.
- What are the different types of lamps used for domestic application ? Explain any one.
- State applications of any four safety tools used in electrical workshop.
- List any four safety precautions to be taken while handling an electrical equipments.

2. Attempt **any three** of the following :

**18**

- Explain construction and working of auto-transformer with diagram. List its four application.
- Draw and explain speed-torque characteristics of 3-phase I.M. List its two application.
- Explain any six factors to be considered while selection of motors for different drives.
- Draw delta connected 3-phase supply system, mark line, phase voltage, line current and phase current. Write power equation.

**P.T.O.**



3. Attempt **any three** of the following :
- Define power and energy with their units.
  - Define transformation ratio and turn ratio of the transformer.
  - Draw circuit diagram of direct on-line starter. List its two applications.
  - Compare between MCCB and ELCB (any four point).
  - Why earthing is required ? Write necessity of earthing.

## SECTION – II

4. Attempt **any five** of the following : 20
- With the help of a neat diagram explain construction and working of LED.
  - Explain zener diode as a voltage regulator.
  - Draw circuit diagram of phase shift oscillator. List its two application.
  - Draw symbol and truth table of
    - OR gate
    - NOR gate
    - NAND gate
    - AND gate
  - Compare between intrinsic and extrinsic semiconductor (any four point).
  - Explain half wave rectifier with circuit diagram and wave form diagram.
5. Attempt **any three** of the following : 18
- Write the comparison between CE, CB and CC configuration (any six points).
  - Convert following binary number to decimal, Hexadecimal and octal form  $(10011.1101)_2$ .
  - Draw and explain block diagram of regulated power supply in detail.
  - Compare between conductor and insulator (any three point).
    - Explain working of PN junction diode.
6. Attempt **any three** of the following : 12
- Explain the working of full wave bridge type rectifier with help of circuit diagram.
  - Explain block diagram of OP-AMP.
  - Explain with diagram OP-AMP as a non inverting amplifier.
  - Convert the following :
    - $(64)_{10} \rightarrow ( )_2$
    - $(3000.45)_{10} \rightarrow ( )_8$
  - Explain crystal oscillator with diagram.
  - State Barkhausen's criteria for oscillation.
-